

EMI and AC

SOLUTIONS

EXERCISE - O

1. **Ans. (C)**

$$\phi = B \cdot A = BA \cos \theta \quad (\theta = 90^\circ)$$

2. **Ans. (A)**

According to size law, current in both will decrease.

3. **Ans. (D)**Flux will be zero as $\vec{B}$ will be perpendicular to area vector.4. **Ans. (C)**

Lenz law.

5. **Ans. (C)**

Lenz's Law

6. **Ans. (B)**

Len's Law.

7. **Ans. (C)**

$$E = -\frac{d\phi}{dt} = \frac{dBA}{dt} = \frac{Bd}{dt} \pi (R_0 + t)^2$$

$$E = 2\pi B (R_0 + t) \text{ Anticlockwise.}$$

8. **Ans. (B)**

$$\phi = B \cdot A$$

$$E = \frac{d\phi}{dt} = A \times \frac{dB}{dt} = \pi R^2 \frac{dB}{dt} = \frac{\pi \times (0.1)^2}{2} \times 0.1 = 1.57 \times 10^{-3} V$$

$$i = \frac{\mathcal{E}}{R} = 3.92 \times 10^{-5} A.$$

9. **Ans. (B)**

(A) Inc dot will induced cross (upper half)

Inc dot will induced cross (lower half)

(B) Inc dot $\rightarrow$ cross (upper half)Dec dot $\rightarrow$ dot (lower half)(C) Dec dot $\rightarrow$ dot (upper half)Inc cross $\rightarrow$ dot (lower half)Hence $I_A = I_C > I_B$ 10. **Ans. (D)**

Concept - Mutual induction

$$\phi_{21} = M_{21} I_1$$


$$E_{21} = -\frac{d\phi_{21}}{dt} = -M_{21} \frac{dI_1}{dt}$$

$$I_2 = \left(\frac{e_{21}}{R_2} \right) = -\frac{M_{21}}{R_2} \frac{dI_1}{dt}$$

According to graph $I_2 = \text{constant}$

$$\int dI_1 = \int -\left(\frac{I_2 R_2}{M_{21}} \right) dt$$

$$I_1 = -(\text{constant}) \times t$$

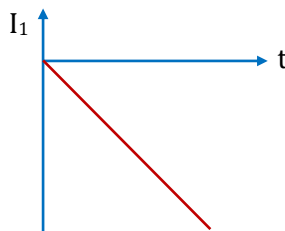

11. **Ans. (A)**

Induced EMF is such that it opposes the cause of flux change.

12. **Ans. (C)**

$$\phi = BS = B\pi R^2 = B\pi(R_0 + t)^2$$

$$e_{ind} = -\frac{d\phi}{dt} = -2\pi(R_0 + t)B$$

Since flux is increasing e_{in} is anticlockwise

13. **Ans. (D)**

$$V_1 = Bv(4r)$$

$$V_2 = -B(2v)(2r)$$

$$V_1 - V_2 = \Delta V = 8Bvr$$

14. **Ans. (D)**

No flux change.

15. **Ans. (C)**

$$\varepsilon_{in} = (\vec{V} \times \vec{B}) \cdot \vec{\ell}$$

$$\varepsilon = \frac{B\omega(PQ)^2}{2} = \frac{B\omega(L^2 + l^2)}{2}$$

$$= \pm(-Bv_x j + Bv_y i) (\ell_1 i + \ell_2 j)$$

$$\varepsilon_{in} = \pm B(\ell_1 V_y - \ell_2 V_x)$$

$$\varepsilon_{in} \propto (\ell_2 V_x - \ell_1 V_y)$$

16. **Ans. (A)**

$$V_p - V_q = B\ell v$$

$$= 4 \times 1 \times 20$$

$$= 80 \text{ V}$$

$$q_A = +80 \times 10$$

$$= +800 \mu\text{C}$$

$$q_B = -800 \mu\text{C}$$

17. **Ans. (B)**

$$E = B\ell v$$

18. **Ans. (A)**

$$\Delta E = \frac{1}{2} B\omega\ell^2$$

$$V_P > V_Q$$

So current from $P \rightarrow Q$

19. **Ans. (C)**

$$m\omega^2 x = eE$$

$$\int E dx = \frac{m\omega^2 \ell^2}{2e}$$


20. **Ans. (B)**

$$B. (\text{at centre}) \quad \frac{\mu_0}{2R} \left(\frac{q\omega}{2\pi} \right)$$

$$B = \frac{\mu_0}{4\pi} \frac{q\omega}{R}$$

$$\phi = B \cdot \pi r^2; \varepsilon_{in} = \frac{d\phi}{dt} = \pi r^2 \frac{dB}{dt} = \frac{\mu_0}{4\pi} \pi r^2 \frac{q}{R} \frac{d\omega}{dt}$$

$$= \frac{\mu_0 e r^2}{4R} \alpha$$

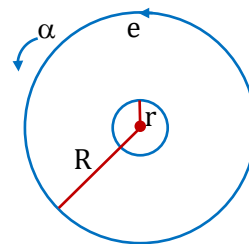

21. Ans. (A)

$$\phi = \pi r^2 [\cos \omega t \hat{j} + \sin \omega t (-\hat{i})] \cdot [B_y \hat{j} + B_z \hat{k}],$$

$$\phi_2 = B_y \pi r^2 \cos \omega t, E = \left| \frac{d\phi}{dt} \right| = B_y \omega \pi r^2 \sin \omega t$$

22. Ans. (A)

$$B \left(\frac{B \omega L^2}{2R} \right) \frac{L \times L}{2} = MgL$$

$$V = \omega L$$

23. Ans. (A)

$$B(x) = B_0 \left(1 + \frac{x}{a} \right)$$

$$\varepsilon_1 = (\varepsilon_{in})_{AB} = B \ell v_0$$

$$= B_0 \left(1 + \frac{x}{a} \right) d \cdot v_0$$


$$= B \cdot d v_0 \left(1 + \frac{x}{a} \right)$$

$$B(x+d) = B_0 \left(1 + \frac{x+d}{a} \right)$$

$$\varepsilon_{net} = \varepsilon_2 - \varepsilon_1$$

$$= B_0 d v_0 \left(\alpha + \frac{\alpha}{d} + \frac{d}{a} - 1 \frac{1}{a} \right)$$

$$= \frac{B_0 d^2 v_0}{a}$$

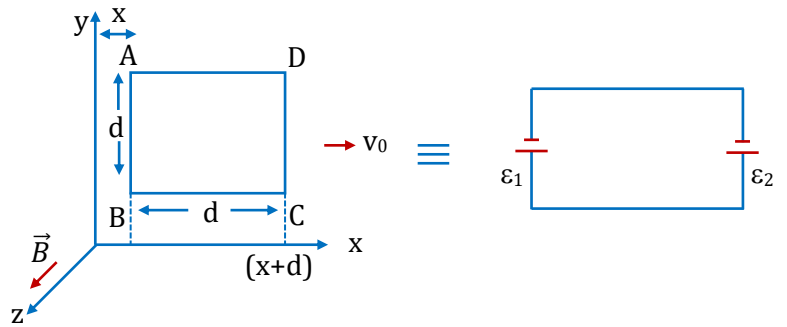

24. Ans. (C)

$$\varepsilon = \frac{B \omega (PQ)^2}{2} = \frac{B \omega (L^2 + l^2)}{2}$$

25. Ans. (C)

$$\text{For (A): } V_B - V_A = \frac{1}{2} B \omega \ell^2 \Rightarrow V_A - V_B = -\frac{1}{2} B \omega \ell^2$$

$$\text{For (B): } V_B - V_A = B v \ell = B \left(\frac{\omega \ell}{2} \right) \ell = \frac{1}{2} B \omega \ell^2 \Rightarrow V_A - V_B = -\frac{1}{2} B \omega \ell^2$$

$$\text{For (C): } V_A - V_B = 0$$

$$\text{For (D): } V_B - V_A = \frac{1}{2} B \omega \ell^2 - \frac{1}{2} B \omega \left(\frac{\ell}{2} \right)^2 = \frac{3}{8} B \omega \ell^2 \Rightarrow V_A - V_B = -\frac{3}{8} B \omega \ell^2$$

26. Ans. (C)


$$\frac{d\phi}{dt} = \varepsilon = B_v u d$$

$$R_{eq} = R + \frac{\rho d}{ab}$$

$$\Rightarrow I = \frac{\varepsilon}{R_{eq}} = \frac{B_v u d}{R + \frac{\rho d}{ab}}$$

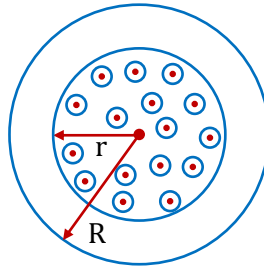27. Ans. (A)

$$\begin{aligned}
 E(2\pi R) &= -\frac{d}{dt}[B(\pi r^2)] \\
 \Rightarrow E &= -\frac{r^2}{2R} \frac{dB}{dt} \\
 \Rightarrow Edt &= -\frac{r^2}{2R} dB \\
 \Rightarrow \int qEdt &= -\frac{qr^2}{2R} \int_B^0 dB \\
 \Rightarrow mv &= \frac{qr^2 B}{2R} \\
 \Rightarrow v &= \frac{qr^2 B}{2mR}
 \end{aligned}$$



28. Ans. (A)

For cylindrical region

$$B \propto \ell \text{ for } \ell < R$$

$$= B \times \lambda \frac{1}{\alpha} \text{ for } \ell > R$$

29. Ans. (A)

$$\pi R^2 B_0 = E \times 2\pi r$$

$$E = \frac{\pi R^2}{2\pi r} B_0 = \frac{R^2 B_0}{2r}$$

$$a = \frac{qE}{m} = \frac{q}{m} \frac{R^2 B_0}{2r} = \frac{qB_0 R^2}{2mr}$$

30. Ans. (A)

$$B = Kt^2$$

$$\int \vec{E} \cdot d\vec{l} = \frac{d\phi}{dt} = \frac{AdB}{dt}$$

$$\Rightarrow E \cdot 2\pi r = \pi r^2 \cdot 2Kt$$


$$\Rightarrow E = Krt$$

Ring starts moving when torque due to electric field becomes greater than torque due to limiting friction

$$QEr = \mu Mgr$$

$$\Rightarrow Q \cdot Krt \cdot r = \mu Mgr$$

$$\Rightarrow t = \frac{\mu Mg}{QKr}$$

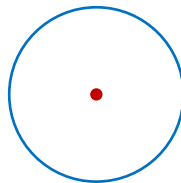

31. Ans. (D)

Induced electric field is non conservative in nature. Therefore work done by this field is path dependent.

32. Ans. (A)

$$\oint \vec{E} \cdot d\vec{\ell} = \frac{d}{dt} \vec{B} \cdot \vec{A}$$

$$\Rightarrow E \cdot 2\pi r = \pi r^2 \frac{d}{dt} Kt$$

$$\Rightarrow E = \frac{rK}{2}$$

$$\Rightarrow a = \frac{eE}{m} = \frac{erK}{2m}$$

Directed along tangent to the circle of radius r , whose centre lies on the axis of cylinder.

33. Ans. (A)

$$E = A \frac{dB}{dt}$$

$$10 = \frac{1}{100} \times \frac{20}{\Delta t}$$

$$\Delta t = 20 \times 10^{-3} \text{ sec} = 20 \text{ ms}$$

34. Ans. (C)

Magnetic field lines and induced electric field lines always form closed loop.

35. Ans. (A)

$$\phi = B\pi r^2 = (16 - 4t^2)\pi r^2$$

$$e_{ind} = -\frac{d\phi}{dt} = 8\pi r^2 t$$


$$e_{ind} = \int E \cdot d\ell$$

$$8\pi r^2 t = E 2\pi r$$

$$\Rightarrow E = \frac{8rt}{2} = 4rt$$

$$\text{At } t = 2 \text{ sec}$$

$$E = 8 \text{ Volt/m}$$

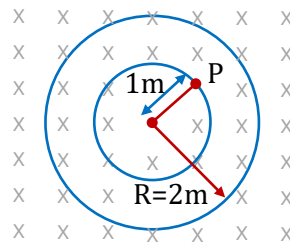

36. Ans. (C)

$$y = \frac{1}{2} Li^2$$

$$\frac{di}{dt} = \frac{2}{2} Li \frac{di}{dt}$$

$$= 2 \times 2 \times 4$$

$$= 16 \text{ J/s.}$$

37. Ans. (A)

$$e = -L \frac{di}{dt}$$

$$\frac{di}{dt} = \text{Slope}$$

$$|\text{Slope}|_1 > |\text{Slope}|_2$$

$$e_1 > e_2$$

38. Ans. (A)

$$B = \mu_0 n_i$$

$$= \left(\mu_0 \frac{N}{L} i \right)$$


$$\phi_T = B \cdot AN = Li \Rightarrow i = \frac{BAN}{L}$$

39. Ans. (B)

$$B_C = \frac{\mu_0 i}{2R}$$

$$\phi = \frac{\mu_0 i}{2R} \pi r^2$$

$$M = \frac{\mu_0 \pi r^2}{2R}$$

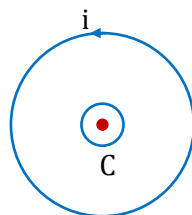

40. **Ans. (D)**

No flux linked, $M = 0$.

41. **Ans. (B)**

$$\text{Mutual inductance, } M = \frac{\phi_N}{I_M} = \frac{\phi_M}{I_N}$$

$$\Rightarrow \phi_M = \left(\frac{I_N}{I_M} \right) \phi_N = \frac{3}{2} \times 1.8 \times 10^{-3} \\ = 2.7 \times 10^{-3} \text{ Wb}$$

42. **Ans. (C)**

For figure (A)

$$L_{eq} = L + 2L + 2M$$

$$= 3L + 2 \frac{1}{\sqrt{2}} \sqrt{L \cdot 2L}$$

$$= 5L = L$$

$$\Delta L = 4L$$

For Figure (B)

$$L_{eq} = L + 2L - 2M$$

$$= 3L - 2 \frac{1}{\sqrt{2}} \sqrt{L \cdot 2L}$$

43. **Ans. (B)**

$$\varepsilon = \frac{d\phi}{dt} = M \frac{di}{dt}$$

$$\Rightarrow \frac{4}{10} = 2 \frac{\Delta i}{10}$$

$$\Rightarrow \Delta i = 2A$$

44. **Ans. (A)**

$$\phi = at(T - t) = aTt - at^2$$

$$e_{ind} = - \frac{d\phi}{dt}$$

$$e_{ind} = -a(T - 2t)$$

$$i_{ind} = \frac{e_{ind}}{R} = \frac{(2at - aT)}{R}$$

$$H = \int_0^T i^2 R dt = \int_0^T \frac{(2at - aT)^2}{R} dt$$

$$= \frac{\int_0^T (4a^2t^2 + a^2T^2 - 4a^2Tt) dt}{R} = \frac{1}{R} \left(\frac{4a^2T^3}{3} + a^2T^3 - \frac{4a^2T^3}{2} \right)$$

$$H = \frac{a^2T^3}{3R}$$


45. **Ans. (B)**

$$\frac{di}{dt} = -10^3 \text{ A/s}$$

$$V_A - iR + V + L \frac{di}{dt} = V_B$$

$$V_A - 5 \times 1 + 15 - 5 \times 10^{-3}(-10^3) = V_B$$

$$V_B - V_A = 15V$$

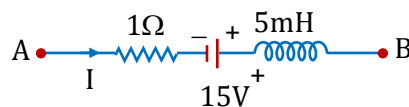

46. **Ans. (A)**

In L - R circuit,

$$V_L = V_0 e^{-Rt/s} \quad \dots(i)$$

$$i = i_0(1 - e^{-Rt/s})$$

47. **Ans. (B)**

Inductor opposes the introduction change of current due to which induced emf is generated in inductor.

48. **Ans. (A)**

At $t \rightarrow \infty$

$$i = i_0 = \left(\frac{V}{R}\right)$$

$$R_{eq} = R$$

$$L_{eq} = \frac{2L \times L}{3L} = \frac{2L}{3}$$

$$i(t) = i_0 \left(1 - e^{-\frac{Rt}{L_{eq}}}\right)$$

$$= \frac{V}{R} \left(1 - e^{-\frac{3Rt}{2L}}\right)$$

$$V_L(t) = V - iR$$


$$\Rightarrow \frac{L di}{dt} = V - iR \left(1 - e^{-\frac{3Rt}{2L}}\right)$$

$$i \frac{L di}{dt} = V e^{-\frac{3Rt}{2L}}$$

$$\int_0^i L di = \int_0^t V e^{-\frac{3Rt}{2L}} dt$$

$$Li = \frac{2LV}{-3R} \left| e^{-\frac{3Rt}{2L}} \right|_0^t$$

$$i = \frac{2V}{3R} [1 - e^{-3Rt/2L}]$$

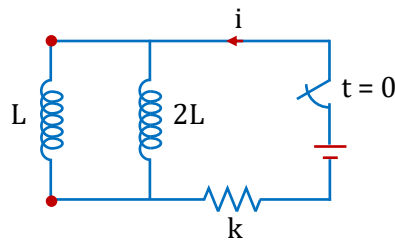

49. **Ans. (A)**

At $t = 0$ inductor is open circuit

$$i = \frac{V}{30} = \frac{2}{30} = \frac{1}{15} A$$

$t \rightarrow \infty$ inductor is short circuited


$$i = \frac{2}{20} = \frac{1}{10} A$$

50. **Ans. (A)**


$$\tau = \frac{L}{R} = \frac{2 \times \frac{1}{2} Li^2}{i^2 R} = \frac{L}{R}$$

51. **Ans. (B)**

Build up circuit

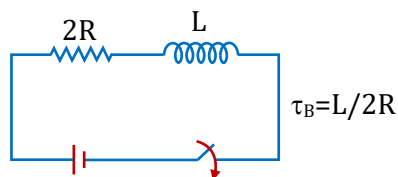

Decay

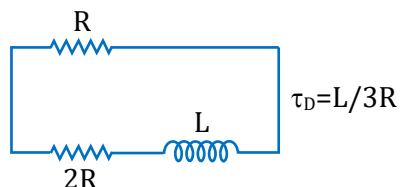

Ratio = 3 : 2

52. **Ans. (A)**

When $x \rightarrow y$

$$i = \frac{E}{R_1}$$

$$\text{Energy} = \frac{1}{2} L \times \left(\frac{E}{R_1} \right)^2$$

53. **Ans. (B)**

Energy of inductor is = $\frac{1}{4} th$ (initial value)

$$\Rightarrow \text{Current } i = \frac{I}{2}$$


$$Q = \frac{\Delta\phi}{R} = \frac{L \left(I - \frac{I}{2} \right)}{R}$$

54. **Ans. (C)**


$$U = \frac{1}{2} Li^2, P = i^2 R, \tau = \frac{L}{R}$$

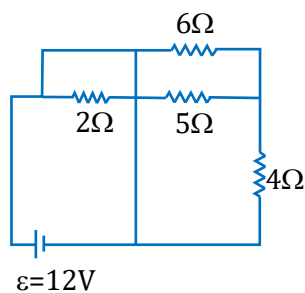55. **Ans. (A)**

Initially all capacitor behave like close circuit and all induction behave like open circuit



$\equiv$

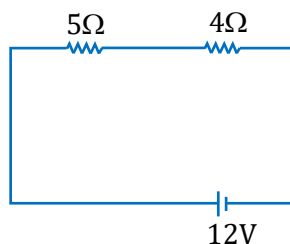

$$i = \frac{12}{9} = \frac{4}{3}$$

56. **Ans. (A)**

$$\frac{Q^2}{2C} = 640 \mu J \quad \dots(1)$$

$$\frac{Q}{C} = 16 V \quad \dots(2)$$

From (1) and (2)

$$\frac{Q}{2} = \frac{640 \times 10^{-6}}{16}$$

$$\Rightarrow Q = 80 \times 10^{-6} C$$

$$\therefore C = \frac{Q}{16} = \frac{80}{16} \mu F = 5 \mu F$$

57. **Ans. (A)**Let $q = q_0 \sin \omega t$

$$I = \frac{dq}{dt} = q_0 \omega \cos \omega t$$

$$\frac{dI}{dt} = \frac{d^2 q}{dt^2} = -q_0 \omega^2 \sin \omega t$$

$$\frac{dI}{dt} \text{ maximum at } \sin \omega t = -1$$

$$\left(\frac{dI}{dt} \right)_{\max} = q_0 \omega^2$$

$$\omega = \frac{1}{\sqrt{LC}}$$

58. **Ans. (B)**When the total energy stored in $300 \mu F$ goes into $1200 \mu F$ capacitor its voltage is maximum.

$$\frac{V_0}{\sqrt{3}}$$

$$V = 50$$

59. **Ans. (D)**

$$\text{Total energy} = \text{Initial energy on capacitor} = \frac{1}{2} CV^2, \text{ Magnetic field energy} = \frac{1}{2} LI^2$$

$$\therefore \frac{1}{2} LI^2 = \frac{1}{3} \times \frac{1}{2} CV^2$$

$$\Rightarrow I = \sqrt{\frac{CV^2}{3L}} = \sqrt{\frac{6 \times 10^{-6} \times 6 \times 6}{3 \times 2.0 \times 10^{-3}}} = 0.6 A$$

60. **Ans. (D)**

Net current through ammeter = zero.

61. Ans. (A)

$$\begin{aligned}
 i_3 &= i_1 + i_2 \\
 &= 5 \left(\frac{3}{5} \sin \omega t + \frac{4}{5} \cos \omega t \right) \\
 &= 5 (\sin \omega t \cdot \cos 53^\circ + \cos \omega t \cdot \sin 53^\circ) \\
 &= 5 \sin (\omega t + 53^\circ)
 \end{aligned}$$

62. Ans. (D)

$$\begin{aligned}
 \langle V \rangle &= \frac{\int_0^{T/2} V dt}{\int_0^{T/2} dt} = \frac{\text{Area under } V-t \text{ curve}}{\frac{T}{2}} \\
 &= \frac{V_0}{2} \\
 V_{\text{rms}} &= \sqrt{\frac{2 \int_0^{T/4} V^2 dt}{\int_0^{T/2} dt}} = \sqrt{\frac{4 \int_0^{T/4} \left(\frac{4V_0}{T} - t \right)^2 dt}{T}} \\
 &= \frac{V_0}{\sqrt{3}}
 \end{aligned}$$

63. Ans. (D)

$$\begin{aligned}
 e &= 10 \left[\sin \left(\omega t + \frac{\pi}{6} \right) \right] \\
 i &= 5 \sin \left(\omega t + \frac{\pi}{4} \right) \\
 \Delta \phi &= \frac{\pi}{4} - \frac{\pi}{6} = \frac{3\pi - 2\pi}{12} = \frac{\pi}{12}
 \end{aligned}$$

64. Ans. (B)

$$\begin{aligned}
 i_0 &= \frac{V_0}{X_c} = 300\sqrt{2} \times 100 \times 10^{-6} \\
 &= 30\sqrt{2} \text{ mA} \\
 i_{\text{rms}} &= \frac{i_0}{\sqrt{2}} \\
 i_{\text{rms}} &= 30 \text{ mA}
 \end{aligned}$$

65. **Ans. (A)**

$$\omega L = 90 \times 10^{-3} \times 2\pi \times 1000 = 180\pi$$

$$\frac{1}{\omega C} = \frac{1}{0.5 \times 10^{-6} \times 2\pi \times 1000} = \frac{1000}{\pi}$$

$\Rightarrow$ Circuit is inductive $V_L > V_R$

$\Rightarrow$ Voltage leads the current

$$\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R} = \frac{80\pi}{R}$$

$$R = \frac{80\pi}{\sqrt{3}}$$

At resonance,

$$\begin{aligned}\omega &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{90 \times 10^{-3} \times 0.5 \times 10^{-6}}} \\ &= \frac{1}{\sqrt{45 \times 10^{-9}}} = \frac{10^5}{15\sqrt{2}} = \frac{\sqrt{2}}{3} \times 10^4\end{aligned}$$

66. **Ans. (B)**

$$V_1 = V_L + V_C = 120V$$

$$V_{net} = \frac{200\sqrt{2}}{\sqrt{2}} = 200V$$

$$V_L^2 + V_R^2 = V_{net}^2$$

$$\Rightarrow 120^2 + V_R^2 = 200^2$$

$$V_R^2 = 40000 - 14400$$

$$V_R = \sqrt{25600}$$

$$V_R = 160$$

$$i = \frac{V_R}{R} = \frac{160}{40} = 4A$$

67. **Ans. (A)**

$$V_{eq} = \sqrt{V_0^2 + \left(\frac{V_0}{2}\right)^2}$$

$$R_{eq} = \sqrt{(\omega L)^2 + R^2}$$

68. **Ans. (D)**

$$\cos \phi = \frac{R}{Z}$$

$$\text{Ratio} = \frac{Z_1}{Z_2} = \frac{\sqrt{(3R)^2 + R^2}}{\sqrt{(2R)^2 + R^2}} = \sqrt{2}$$

69. **Ans. (A)**

$$z = 100 \left(= \frac{V}{I} \right) \cos \phi = \frac{R}{Z} = \frac{100}{\sqrt{(100)^2 + \left(\frac{1}{\omega C} \right)^2}}$$

$$z = R (\Rightarrow x_L = x_C) = \frac{1}{\sqrt{2}}$$

70. **Ans. (D)**

Current in circuit :

$$I = \frac{V}{X} = \frac{250}{(75-25)} = \frac{250}{50} = 5A$$

$$\therefore V_L = I X_L = 5 \times 25 = 125V$$

$$\text{and } V_C = I X_C = 5 \times 75 = 375V$$

voltage on capacitor is more than that of supply voltage because the phase difference between V_L and V_C is 180° (i.e. out of phase).

71. **Ans. (A)**

$$Q = \frac{\omega_0}{2Y} \text{ highest } Q \Rightarrow \text{lowest } Ys$$

72. **Ans. (C)**

$$\tan \phi = \omega L - \frac{1}{\omega C} \left(\frac{X_L - X_C}{R} \right)$$

$$\text{When } \frac{\omega}{\omega_0} = 1 \quad \text{i.e. } \omega = \frac{1}{\sqrt{LC}} = \omega_0$$

$$\tan \phi = 0 \text{ as in plot}$$

As R increases $\tan \phi$ decreases for a given ω .

(i) belong to smaller R . compared to (2) and (3) curves.

Hence, (a) - (1)

(b) - (2)

(c) - (3)

73. **Ans. (D)**

$$\frac{f_{\max}}{\Delta f_{\text{half of max power}}} = \text{Quality factor}$$

74. **Ans. (B)**

$$I_{rms} = \sqrt{\frac{\int_0^t i^2 dt}{\int_0^t dt}}$$

i^2 is maximum for III and equal for I and II and minimum for IV

$$\text{So, } I_3 > I_1 = I_2 > I_4$$

75. Ans. (C)

$$\cos \phi = \frac{R}{Z} = \frac{1}{\sqrt{2}} \Rightarrow \left| \omega L - \frac{1}{\omega C} \right| = R$$

$$\left| 100 \times 1 - \frac{1}{100C} \right| = 10$$


$$\frac{1}{100C} = 20 \quad C = 500 \mu F$$

76. Ans. (B)

$$\tan \theta_1 = \frac{X_L}{R}; \tan \theta_2 = \frac{X_C}{R}$$

$$\tan \theta = \frac{X_C - X_L}{R}$$
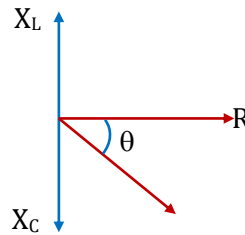
$$\tan \theta = \frac{X_C}{R} - \frac{X_L}{R} = \tan \theta_2 - \tan \theta_1$$



77. Ans. (C)

$$\langle P \rangle = i_{\text{rms}} V_{\text{rms}} \cos(\Delta\phi)$$

$$= \frac{2}{\sqrt{2}} \cdot \frac{200\sqrt{2}}{\sqrt{2}} \cdot \cos(45^\circ - 15^\circ)$$

$$= 100\sqrt{6} \text{ Watt}$$

78. Ans. (B)

$$\frac{i_p}{i_s} = \frac{N_s}{N_p} \Rightarrow i_p = \frac{1}{8} \times 25 = \frac{25}{8} A$$

$$P_{in} = i_p V_p \Rightarrow 10 \times 10^3 = \frac{25}{8} \times V$$

$$V = \frac{10^4 \times 8}{25}$$

79. Ans. (A)

$$A = \frac{F_0 / m}{\sqrt{\omega^2 - r^2}}$$

80. Ans. (D)

$$T' = \frac{2\pi}{\omega'}$$

$$\omega' = \sqrt{\omega_0^2 - y^2}$$

$$\omega' < \omega_0 \Rightarrow T' > T_0 \text{ and constant}$$

81. Ans. (D)

Amplitude of pendulum will vary as

$$A = A_0 e^{-\delta t}, \delta = \text{damping constant}$$

$$E = \frac{1}{2} k A^2 = \frac{1}{2} k A_0^2 e^{-2\delta t}$$

$$E = E_0 e^{-2\delta t}$$

$$\text{At } t = 0, E_0 = 45 \text{ J}$$

$$\text{At } t = 15 \text{ s}, E = 15 \text{ J}$$

$$\text{So } 15 = 45 e^{-2\delta \times 15} \Rightarrow \delta = \frac{1}{30} \ln 3$$

82. Ans. (A)

$$\text{Damping force, } F = -b \frac{dx}{dt}$$

$$= -bx_0 \left[\omega_0 e^{-\omega_0 t} - \omega_0 (1 + \omega_0 t) e^{-\omega_0 t} \right]$$

$$= bx_0 \omega_0^2 t e^{-\omega_0 t}$$

F is maximum when

$$\frac{dF}{dt} = 0$$

$$\Rightarrow bx_0 \omega_0^2 \left[e^{-\omega_0 t} - \omega_0 t e^{-\omega_0 t} \right] = 0$$

$$t = \frac{1}{\omega_0} = \frac{1}{100} \text{ sec} = 0.01 \text{ s}$$

83. Ans. (B)

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{25 \times 10^{-3} \times 12 \times 10^{-6}}}$$

$$= 1.825 \times 10^3 \text{ rad}$$

$$\lambda = \frac{I^2}{2L} = \frac{60}{2 \times 25} \times 10^3 = 1.2 \times 10^3$$

$$\omega' = \sqrt{\omega_0^2 - \gamma^2} = \sqrt{(1.825 \times 10^3)^2 - (1.2 \times 10^3)^2} = 1.4 \times 10^3$$

84. Ans. (A)

Charge decays exponentially means oscillation is overdamped:

$$\gamma \geq \omega_0 \Rightarrow \frac{R}{2L} \geq \frac{1}{\sqrt{LC}}$$

$$R \geq 2\sqrt{\frac{L}{C}}$$

$$R \geq 100\sqrt{2}\Omega$$

85. **Ans. (D)**

$$\omega_1 = \sqrt{\omega_0^2 - 2\gamma^2} \quad \text{Maximum amplitude}$$

$$\omega_2 = \omega_0 \quad \text{for power maximum}$$

$$* \omega_2 > \omega_1$$

86. **Ans. (C)**

$$\omega = \sqrt{\frac{k}{m}} \sqrt{1 - \frac{r^2}{4mk}} \quad \frac{r^2}{mk} = \frac{8}{100}$$

$$\omega = \sqrt{\frac{k}{m}} \sqrt{1 - \frac{8}{4mk}} = \sqrt{0.98 \frac{k}{m}}$$

For undamped

$$T_1 = \frac{2\pi}{\omega} = 2\pi \sqrt{\frac{m}{k}}$$


For damped

$$T_2 = \frac{2\pi}{\omega} = 2\pi \sqrt{\frac{m}{0.98k}}$$

$$\text{Change} = \frac{T_2 - T_1}{T_1} \times 100 = \frac{\sqrt{\frac{1}{0.98}} - 1}{1} \times 100 \approx 1\% \text{ increases}$$

87. **Ans. (AC)**

Since flux of wire on the loop is zero therefore emf will not be induced.

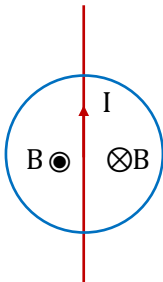88. **Ans. (ABCD)**Let velocity of wire at time t is v , then

$$\varepsilon = Bv\ell$$

$$q = C\varepsilon, i = \frac{dq}{dt} = CB\ell \frac{dv}{dt}$$

$$F_m = i\ell B$$

$$F - F_m = ma$$

89. **Ans. (AC)**At $t = 0$, Inductor behaves as open circuit.

$$\text{So } A_1 = A_3 = \frac{50}{100 + 50} = \frac{1}{3} \text{ and } A_2 = 0$$

$$V_1 = 100 \left(\frac{1}{3} \right)$$

$$V_2 = V_4 = 50 \left(\frac{1}{3} \right)$$

90. **Ans. (AB)**

At an instant at $t = t$ sec

Initially $J = mu$ (U = initial velocity)

$$U = \frac{J}{M}$$

Motional EMF = $BV\ell$

...(i)

Induced EMF in inductor = $L \frac{di}{dt}$

...(ii)

$$BV\ell = L \frac{di}{dt}$$

$$\int_0^i L di = B\ell \int_0^t V di$$

$$Li = B\ell x$$

...(iii)

Force on rod = $iB\ell$

By NLM

$$-iB\ell = ma$$

$$-\frac{B^2 \ell^2 x}{L} = ma$$

$$a = -\frac{B^2 \ell^2 x}{mL} \text{ (SHM)}$$

$$\omega = \frac{B\ell}{\sqrt{mL}}$$

We know in SHM

$$U = \frac{J}{m} = \omega A \Rightarrow A = \frac{J}{m\omega}$$

$$v = \omega \sqrt{A^2 - x^2}$$


$$\frac{\omega A}{2} = \omega \sqrt{A^2 - x^2}$$

$$\frac{A^2}{4} = A^2 - x^2$$

$$x^2 = \frac{3A^2}{4}$$

$$x = \pm \frac{\sqrt{3}}{2} A$$
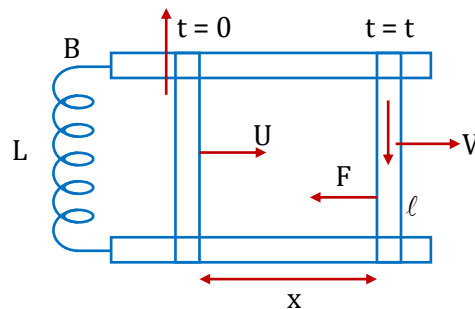
$$x = \pm \frac{\sqrt{3}}{2} \times \frac{J}{m\omega}$$



$$x = \pm \frac{\sqrt{3}}{2} \times \frac{J}{m} \times \frac{\sqrt{mL}}{b\ell}$$

$$x = \pm \sqrt{\frac{3J^2L}{4B^2\ell^2m}}$$

From equation (iii)

$$i = \frac{B\ell x}{L}$$

$$i = \sqrt{\frac{3}{4} \frac{J^2}{Lm}}$$

91. **Ans. (ABC)**

At $t = 0$

$$\text{Resistance of } ckt = \left(\frac{40 + 40 + 20}{100} \right) m \times 1r / m$$

$$R = 1r$$

$$\phi = \vec{B} \cdot \vec{A} = (2t) \left(\frac{40 \times 20}{100 \times 100} \right) = \frac{16t}{100}$$

$$|\varepsilon| = \frac{\partial \phi}{\partial t} = \frac{16}{100} = 0.16V, \text{ So, current } I = \frac{|\varepsilon|}{R} = 0.16A$$

$\therefore B = 2t$ (outer)

According to lenz low, induced emf will be opposite to it.

$\Rightarrow$ clockwise sense current.

(B) At $t = t$

$$\phi = \vec{B} \cdot \vec{A} = (2t) \left(\frac{20 \times (40 - 5t)}{100 \times 100} \right)$$

$$\phi = \frac{40t - 5t^2}{250}$$

$$|\varepsilon| = \frac{\partial \phi}{\partial t} = \frac{40 - 10t}{250}$$

$$\text{At } t = 2, |\varepsilon| = \frac{40 - 20}{250} = 0.08V$$

(C) At $t = 2$

$$R = \left(\frac{20 + 30 + 30}{100} \right) m \times 1\Omega / m = 0.8\Omega$$



$$\varepsilon = 0.08V, B = 2t = 4, \ell = 20 \text{ cm} = 0.2 \text{ m}$$

$$i = \frac{\varepsilon}{R} = \frac{0.08}{0.8} = 0.1A$$

For constant velocity

$$F = iB\ell = (0.1)(4)(0.2)$$


$$F = 0.08 \text{ N}$$

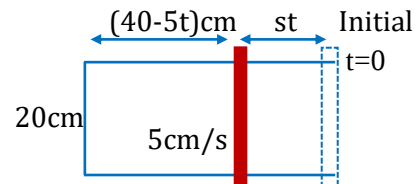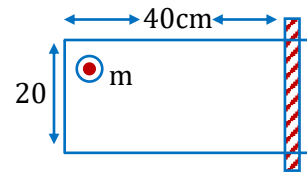

92. **Ans. (BD)**

(B) When Q is brought towards P , north and south poles, will be induced at P as shown in the figure which is as a result of current in P is opposite direction as current in Q .

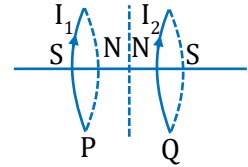(D) Not due to induction effect but because of magnetic force between them, if the currents are in opposite direction in the loops, the loops will repel each other.



93. **Ans. (AD)**

$$u = v \cot \theta$$


$$\omega = \frac{v}{l \sin \theta} = \frac{2v}{\sqrt{3}l}$$

Consider an imaginary conducting loop ABC .

e.m.f. in this loop = motional e.m.f. in the rod

$$= -\frac{B}{2} \frac{d(xy)}{dt} = -\frac{B}{2} [yv - xu] \left[\because \frac{dy}{dt} = -u \right]$$
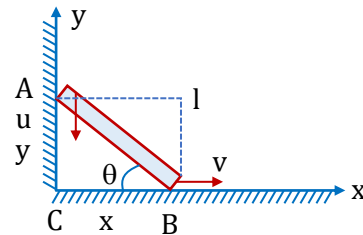
$$= \frac{Blv \cos 2\theta}{2 \sin \theta}$$



94. **Ans. (AB)**


Current must flow from E to F

In equilibrium

$$F_B \cos \theta = mg \sin \theta$$

$$ilB = mg \frac{\sin \theta}{\cos \theta}$$

$$ilB = mg \tan \theta$$

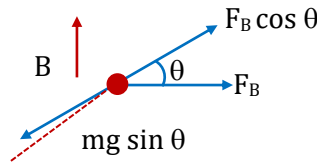

95. **Ans. (BC)**

$$\text{By using } e = \frac{1}{2} Bl^2 \omega$$

$$\text{For part } AO; e_{OA} = e_o - e_A = \frac{1}{2} Bl^2 \omega$$


$$\text{For part } OC; e_{OC} = e_o - e_C = \frac{1}{2} B(3l)^2 \omega = \frac{9}{2} B\omega l^2$$

$$\therefore e_A - e_C = 4Bl^2 \omega$$

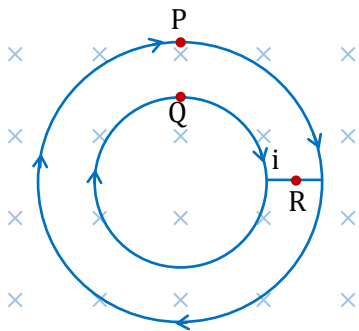96. **Ans. (ACD)**

Since inside flux is decreasing.

$\Rightarrow$ To increase flux (lenz law) current in loops must be clockwise.



Current cannot flow in a single wire connecting two independent loop.

Minimum two wires are required.

97. **Ans. (AB)**

Conceptual

98. **Ans. (ABD)**

$$emf = \varepsilon = \frac{d\phi}{dt} = \frac{d}{dt}(B.A) = \pi R^2 \frac{dB}{dt}$$

$$\varepsilon = \int E \cdot dr = \pi R^2 \frac{dB}{dt} \left\{ \frac{dB}{dt} \text{ is -ve} \right\}$$

$$\text{For wooden ring } E_w(2R) = \pi R^2 \frac{dB}{dt}$$

$$\Rightarrow E_w = \frac{1}{2} \left(\pi R \frac{dB}{dt} \right)$$

$$\text{For copper ring } E_c = \frac{1}{3} \left(\pi R \frac{dB}{dt} \right)$$

$$E_w > E_c$$

Resistance of wooden ring = ∞

$$\text{Current induced in wooden ring} = \frac{\varepsilon}{R} = 0$$

Electric field which is induced on wooden ring will be in tangential direction, so there will be torque acting on charge Q on the same ring i.e. the ring will rotate.


99. **Ans. (ABCD)**

$$\int \vec{E} \cdot d\vec{l} = A \cdot \frac{dB}{dt}$$

$$E \cdot 2\pi\sqrt{x^2 + d^2} = \pi R^2 k, \text{ where } \left(\frac{dB}{dt} = k \right)$$

$$E = \frac{R^2 k}{2\sqrt{x^2 + d^2}}; W = \int_0^\infty q \vec{E} \cdot d\vec{x}$$

$$= \int_0^\infty q E \cos \theta \cdot dx = \int_0^\infty \frac{q R^2 k}{2\sqrt{x^2 + d^2}} \frac{d}{\sqrt{d^2 + x^2}} dx = \frac{q R^2 k \pi}{4}$$

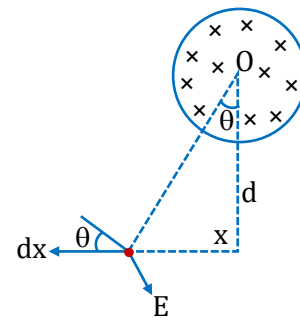100. **Ans. (ACD)**From faraday's law $V \propto L$

$$\text{Rate of change of current is constant } \left(v = -L \frac{\partial i}{\partial t} \right)$$

$$\therefore \frac{V_2}{V_1} = \frac{L_2}{L_1} = \frac{2}{8} = \frac{1}{4}$$

Power delivers to the two coils is same i.e.,

$$v_1 i_1 = v_2 i_2 \Rightarrow \frac{i_1}{i_2} = \frac{v_2}{v_1} = \frac{1}{4}$$

$$\text{Energy stores } W = \frac{1}{2} L i^2$$

$$\frac{W_2}{W_1} = \left(\frac{L_2}{L_1} \right) \left(\frac{i_2}{i_1} \right)^2 = \left(\frac{1}{4} \right) (4)^2 = 4$$

101. Ans. (AC)

For given situation $\frac{q}{C} + L \frac{di}{dt} = 0$

$$\Rightarrow \frac{d^2 q}{dt^2} + \frac{q}{LC} = 0 \quad \Rightarrow \frac{d^2 q}{dt^2} + \omega^2 q = 0$$

$$\Rightarrow q = q_0 \cos \omega t \text{ and } i = -q_0 \omega \sin \omega t$$

According to given conditions $\frac{q^2}{2C} = \frac{1}{2} Li^2$

$$\Rightarrow \frac{q_0^2 \cos^2 \omega t}{2C} = \frac{1}{2} L q_0^2 \omega^2 \sin^2 \omega t$$

$$\Rightarrow \cot^2 \omega t = \tan^2 \omega t$$

$$\Rightarrow \omega t = \frac{\pi}{4}, \frac{3\pi}{4}, \frac{5\pi}{4}, \frac{7\pi}{4}, \dots$$

$$\Rightarrow t = \frac{\pi\sqrt{LC}}{4}, \frac{3\pi\sqrt{LC}}{4}, \frac{5\pi\sqrt{LC}}{4}, \frac{7\pi\sqrt{LC}}{4}, \dots$$

102. Ans. (AD)

Conceptual

103. Ans. (BC)

$$L = 100 \times 10^{-3} \text{ H}$$

$$C = 10 \times 10^{-6} \text{ F}$$

$$R = 100 \Omega$$

$$V = 5 \sin 500 t$$

$$\omega = 500$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

$$= 500 \times 100 \times 10^{-3} = 50 \Omega$$

$$X_C = \frac{1}{500 \times 10 \times 10^{-6}} = 200 \Omega$$

When turns is doubled

$$L \propto n^2$$

$\Rightarrow X_L$ becomes 4 times

$$C = \frac{Ak\epsilon_0}{d}$$

When $k = 4$

C becomes 4 times

$\Rightarrow X_C$ becomes $\frac{1}{4}^{\text{th}}$ times

104. Ans. (ACD)

$$V_R^2 + V_L^2 = 100^2$$

$$|V_C - V_L| = 120$$

$$130^2 = V_R^2 + (V_C - V_L)^2$$

$\therefore V_C > V_L$ so circuit is capacitive.

105. Ans. (CD)

$$e = e_1 + e_2 = 200 \sin \left(\omega t + \frac{\pi}{2} \right)$$

$$e_0 = 200 \text{ volt}$$

$$V_5 = \frac{200}{\sqrt{2}} = 100\sqrt{2}$$

$$z = \sqrt{(500)^2 + (500)^2} = 500\sqrt{2}$$

$$i_{rms} = \frac{100\sqrt{2}}{500\sqrt{2}} = \frac{1}{5}$$


$$V_1 = 500 \times \frac{1}{5} = 100 \text{ volt}$$

$$V_2 = 900 \times \frac{1}{5} = 180 \text{ volt}$$

$$V_3 = 400 \times \frac{1}{5} = 80 \text{ volt}$$

$$V_4 = V_2 - V_3 = 100 \text{ volt}$$
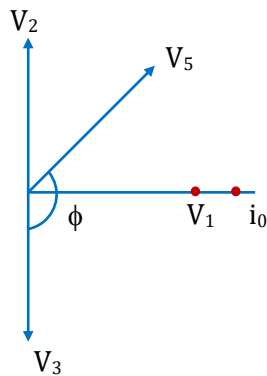
$$\Rightarrow \phi = \frac{\pi}{2} + \tan^{-1} \left(\frac{9}{5} \right)$$



106. Ans. (ACD)

$$X_L = X_C$$

$$2\pi f \cdot L = \frac{1}{2\pi f C}$$

$$2\pi f \cdot \frac{2}{\pi} = \frac{10^6}{2\pi f \cdot \frac{8}{\pi}}$$

$$f^2 = \frac{10^6}{4 \times 16}$$

$$f = \frac{10^3}{8} = \frac{1000}{8} = 125 \text{ Hz}$$

$$V_L = I X_L = 2 \times 2\pi \times \frac{1000}{8} \times \frac{2}{\pi} = 1000 \text{ V}$$

107. Ans. (BC)

Magnetic flux through the smaller loop due to current in the bigger loop

$$= \left(\frac{\mu_0 I}{2\pi d} - \frac{\mu_0 I}{2\pi(2d)} \right) \ell^2 = \frac{\mu_0 I \ell^2}{4\pi d}$$

$$\text{So mutual inductance} = \frac{\mu_0 \ell^2}{4\pi d}$$

$$\therefore \text{ So emf induced in the bigger loop} = \frac{d}{dt} \left[\frac{\mu_0 \ell^2}{4\pi d} k t \right] = \frac{\mu_0 \ell^2 k}{4\pi d}$$

108. Ans. (BD)

$$\varepsilon = \pi R^2 \sin^2 \theta \alpha$$

$$\text{So current } di = \frac{\varepsilon}{dr} = \frac{1}{2\rho} dR^2 \alpha \sin \theta d\theta$$

$$\text{So } \int d\mu = \int_0^\pi \frac{\pi dR^4 \alpha \sin^3 \theta d\theta}{2\rho} = \frac{2\pi}{3\rho} dR^4 \alpha$$

109. Ans. (ABD)

Loop equation gives

$$L \frac{di}{dt} + iR = \frac{\mu_0 N a^2 \omega}{2\ell} i$$

$$\text{So, } \frac{di}{dt} = \frac{1}{L} \left(\frac{\mu_0 N a^2 \omega}{2\ell} - R \right) i$$

$$\text{So to grow current always, } \frac{\mu_0 N a^2 \omega}{2\ell} - R > 0$$

$$\Rightarrow \omega > \frac{2\ell R}{\mu_0 N a^2}$$

110. Ans. (C)

$$T - F_B - (T + dT) = dm\omega^2 x \quad - F_B - dT = dm\omega^2 x$$

$$\int_{\ell/2}^x \lambda dx \cdot \omega x B - \int_0^T dT = \int_{\ell/2}^x \frac{m}{\ell} \omega^2 x dx$$

$$-\frac{\lambda \omega B}{2} \left(x^2 - \frac{\ell^2}{4} \right) - T = \frac{M\omega^2}{2\ell} \left(x^2 - \frac{\ell^2}{4} \right)$$

$$T = -\frac{\lambda \omega B}{2} \left(x^2 - \frac{\ell^2}{4} \right) - \frac{m\omega^2}{2\ell} \left(x^2 - \frac{\ell^2}{4} \right)$$

$$T = -\left(\frac{\lambda \omega B}{2} + \frac{m\omega^2}{2\ell} \right) x^2 + \frac{\lambda \ell^2 \omega B}{8} + \frac{m\omega^2 \ell}{8}$$



It is an equation of parabola concave in downward direction.

111. Ans. (B)

$$T_{(x=0)} = \frac{\ell^3 \omega B}{8} + \frac{m\omega^2 \ell}{8},$$

$$T_{(\alpha=\ell/4)} = \frac{3}{32} (B\omega \ell^3 + m\omega^2 \ell)$$
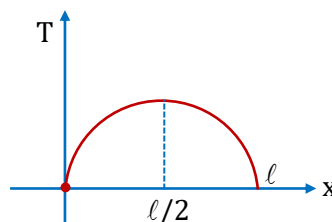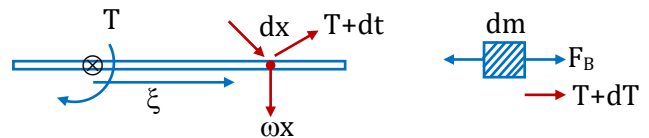
$$\frac{T_{(x=0)}}{T_{(x=\ell/4)}} = \frac{4}{3}$$



112. Ans. (D)

$$V_B - V_A = \frac{1}{2} B \omega (r_2^2 - r_1^2)$$

$$(A) V_P - V_0 = \frac{1}{2} (r_p^2 - r_u^2) > U_2 \quad \dots(1)$$

$$V_R - V_0 = \frac{1}{2} B \omega (r_R^2 - r_0^2)$$


$$V_R - V_0 = \frac{1}{2} B \omega ((\sqrt{2}a)^2 - 0^2) > 0 \quad \dots(2)$$

(B) from (1) and (2)

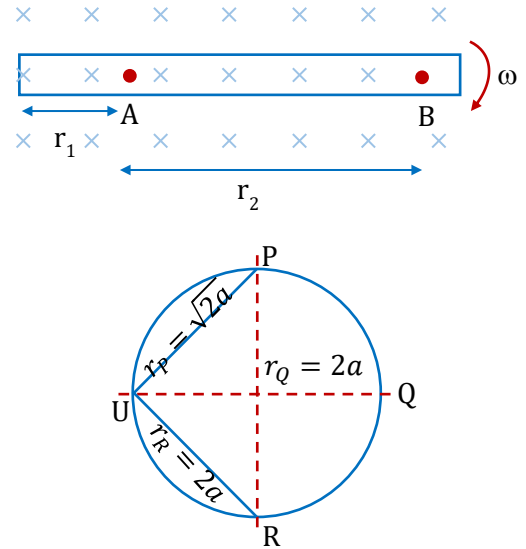(C) From (1), $V_0 < V_P$, $V_Q \neq V_P$

$$(D) V_Q - V_P = \frac{1}{2} B \omega (r_Q^2 - r_P^2) = \frac{1}{2} B \omega ((2a)^2 - (\sqrt{2}a)^2)$$

$$V_Q - V_P = \frac{1}{2} B \omega (2a^2) = V_P - V_0$$



113. Ans. (C)

$$(A) V_P - V_0 = \frac{1}{2} B \omega (2a^2) = B \omega a^2$$

$$(B) V_P - V_Q = \frac{1}{2} B \omega (r_P^2 - r_Q^2) = -B \omega a^2$$

$$(C) V_Q - V_0 = \frac{1}{2} B \omega (r_Q^2 - r_0^2) = 2B \omega a^2$$

$$(D) V_P - V_R = \frac{1}{2} B \omega (r_P^2 - r_R^2) = 0$$

114. Ans. (D)

$$V_Q - V_P = V_Q - V_R = V_1$$

$$V_P - V_0 = V_R - V_0 = V_2$$

No current flows in the circuit.

115. Ans. (A)

$$R_{eq} = \frac{R}{2} \parallel \frac{R}{2} = \frac{R}{4} = \frac{6}{4} = 1.5 \Omega$$

$$L_{eq} = \frac{L}{2} \parallel \frac{L}{2} = \frac{L}{4} = \frac{1.8 \times 10^{-4}}{4} = 4.5 \times 10^{-5} H$$


116. Ans. (C)

$$\tau = \frac{L/4}{R/4} = \frac{L}{R} = \frac{1.8 \times 10^{-4}}{6} = 3 \times 10^{-5} s = 30 \mu s$$

117. Ans. (B)

$$\text{Steady state current, } I = \frac{E}{R/4} = \frac{12}{1.5} = 8 A$$

118. Ans. (A)

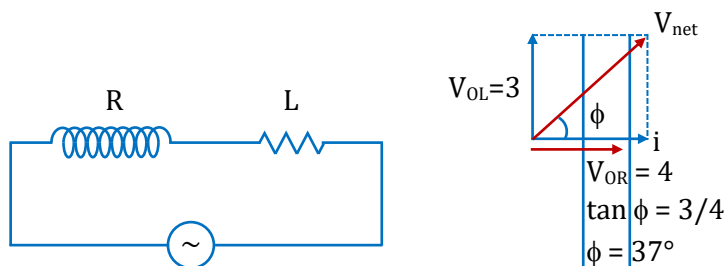

$$V_R = V_{OR} \sin \omega t$$

$$V_L = V_{OL} \sin \left(\omega t + \frac{\pi}{2} \right) \text{ when } V_R = 2$$

$$\frac{V_R}{V_L} = \frac{V_{OR}}{V_{OL}} (\tan \omega t) \Rightarrow V_{OR} \sin \omega t = 2 \quad \sin \omega t = \frac{2}{4} = \frac{1}{2} \text{ or } \omega t = 30^\circ$$

$$\frac{V_R}{V_L} = \frac{4}{3} \times \frac{1}{\sqrt{3}} \Rightarrow V_L \left(\frac{2 \times 3 \times \sqrt{3}}{42} \right) = 3 \cos \theta$$

119. Ans. (B)

$$\begin{aligned} V_{\text{net}} &= V_L + V_R \\ &= 3 \cos 30^\circ + 2 \\ &= \left(\frac{3\sqrt{3} + 4}{2} \right) V \end{aligned}$$

120. Ans. (A)

$$\text{Since } V_L = -L \frac{di}{dt}$$

If $\frac{di}{dt}$ is decreasing then V_L is increases.

$$\text{and } V_{\text{source}} = \sqrt{V_R^2 + V_L^2}$$

So, V_{source} also increases

EXERCISE - S

1. Ans. 6.5 V

$$B = \frac{\mu_0 NI}{\ell}$$

(Inside the solenoid away from the ends)

$$\phi = \frac{\mu_0 NI}{\ell} A$$

$$\text{Total flux linkage} = N\phi = \frac{\mu_0 N^2 A}{\ell} I$$

(Ignoring end variations in B)

$$|\varepsilon| = \frac{d}{dt}(N\phi)$$

$$|\varepsilon|_{av} = \frac{\text{Total change in flux}}{\text{total time}}$$

$$|\varepsilon|_{av} = \frac{4\pi \times 10^{-7} \times 25 \times 10^{-4}}{0.3 \times 10^{-3}} \times (500)^2 \times 2.5 = 6.5V$$

2. **Ans.** 0.75 T

$$Q = \int_{t_i}^{t_f} Idt = \frac{1}{R} \int_{t_i}^{t_f} \varepsilon dt = -\frac{N}{R} \int_{\phi_i}^{\phi_f} d\phi = \frac{N}{R} (\phi_i - \phi_f)$$

For $N = 25, R = 0.50 \Omega, Q = 7.5 \times 10^{-3} C$

$$\phi_f = 0, A = 2.0 \times 10^{-4} m^2, \phi_i = 1.5 \times 10^{-4} Wb$$

$$b = \frac{\phi_i}{A} = 0.75 T$$

3. **Ans.** 2

$$q = \frac{\Delta\phi}{R}$$

$$\Rightarrow \Delta\phi = qR = \text{Area of } i-t \text{ graph} \times R$$

$$= \frac{1}{2} (4) (0.1) \times 10 = 0.2 \times 10 = 2 \text{ Weber}$$

4. **Ans.** 32

$$\varepsilon = (\vec{v} \times \vec{B}) \cdot \vec{\ell}_{eff}$$

$$\varepsilon = [2\hat{i} \times (3\hat{j} + 4\hat{k})] \cdot [3\hat{i} + 4\hat{j}]$$

$$|\varepsilon| = 32 \text{ volt}$$

5. **Ans.** $\lambda V_y B_0$

$$E = [B\ell v]$$

6. **Ans.** 2

$$R_{eq} = 4, F = \frac{B^2 \ell^2 v}{R} = 2N$$

7. **Ans.** 4

$$e = B\ell v$$

$$v = \frac{dx}{dt} = -2 \times 120\pi \sin 120\pi t$$

$$\varepsilon = -\frac{1.2}{\pi} \times 1.5 \times \frac{2}{100} \times 120\pi \sin \left(120\pi \times \frac{1}{80} \right)$$

$$= \frac{240\pi}{100\pi} \times 1.8 = 4.32V$$

$$\approx 4 \text{ volts}$$

8. **Ans.** $1.7 \times 10^{-5} V$


$$e = -\frac{d\phi}{dt} = \frac{-d}{dt}(MI)$$

$$e = -I \frac{d}{dt} \left[\frac{\mu_0 a}{2\pi} \log_e \left(\frac{a}{r} + 1 \right) \right]$$

$$e = \frac{\mu_0 I_a^2}{2\pi} \times \frac{1}{r(r+a)} \times V$$

$$e = 1.7 \times 10^{-5} V$$

9. **Ans.**

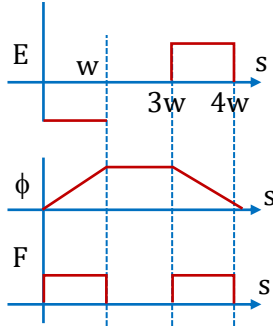

Initially while entering flux increase and then constant and then reduces to zero while coming out.

10. **Ans.** 5

$$\Delta q = \frac{Bab}{R} = 7.5 \cdot 10^{-4}$$

$$\phi_i = Bab$$

$$\phi_f = 0$$

$$\therefore \Delta q = \frac{\phi_i - \phi_f + L \int_0^0 d\ell}{R} = \frac{\phi_i - \phi_f}{R}$$

11. **Ans.** (a) zero, (b) $vB(bc)$, positive at c, (c) zero (d) $vB(bc)$, positive at a
Motional emf = BLV

12. **Ans.** $V = 1 \text{ ms}^{-1}$, $R_1 = 0.5 \Omega$, $R_2 = 0.30 \Omega$

At terminal velocity, $F_{\text{net}} = 0$

$$BiL = mg \Rightarrow i = \frac{mg}{BL} = \frac{10}{3} A$$

$$i_1 + i_2 = i$$

$$i_1^2 R_1 = 0.76$$

$$i_2^2 R_2 = 1.2$$

$$\frac{V^2}{R_1} = 0.76, \frac{V^2}{R_2} = 1.2 \Rightarrow \frac{R_1}{R_2} = \frac{1.2}{0.76} = \frac{30}{19}$$

$$i_1 = i \left(\frac{R_2}{R_1 + R_2} \right) = \frac{10}{3} \left[\frac{1}{\frac{30}{19} + 1} \right] \approx 1.3 A$$


$$i_2 = i \left(\frac{R_1}{R_1 + R_2} \right) = 2 A$$

$$R_1 = 0.45 \Omega$$

$$R_2 = 0.3 \Omega$$

$$i_2 = \frac{B\ell V}{R_2} \Rightarrow U = \frac{i_2 R_2}{BL} = \frac{2 \times 0.3}{0.6 \times 1} = 1 \text{ m/s}$$

Terminal velocity = 1 m/s

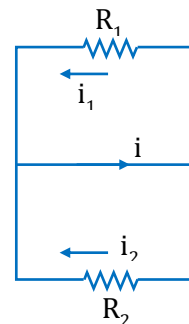

...(i)

...(ii)

...(iii)

13. **Ans.** $\left(\frac{1}{2} \frac{dB}{dt} \sqrt{R^2 - \frac{l^2}{4}} \right)$

$$E = \frac{-d\phi}{dt}$$

Let E be induced electric field due to time-changing magnetic flux.

$$E \times 2\pi R = \frac{d\phi}{dt} = (\pi R^2) \frac{dB}{dt}$$


$$\text{Potential difference} = \int_{\frac{l}{2}}^{l/2} -E dl$$

$$E = \frac{R}{2} \frac{dB}{dt}$$

$$\Delta V = \frac{R}{2} \frac{dB}{dt} \cos \theta \left[\frac{l}{2} - \left(-\frac{l}{2} \right) \right] = \frac{R}{2} \frac{dB}{dt} \cos \theta \times l$$

$$\Delta V = \frac{R}{2} \times \frac{dB}{dt} \times \frac{b}{R} \times l = \frac{1}{2} \times \frac{dB}{dt} \times \sqrt{R^2 - \left(\frac{l}{2} \right)^2}$$

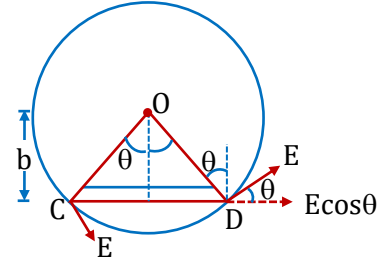Direction will be from D to C as per Lenz's law.



14. **Ans.** $\left(\frac{\mu_0 i a^2 \pi}{2 R b} \right)$

$$\varepsilon = \frac{d\phi}{dt}$$

$$iR = \frac{d\phi}{dt}$$

$$\frac{dq}{dt} R = \frac{d\phi}{dt}$$

$$dq = \frac{d\phi}{R}$$

$$\phi_1 = 0$$

$$\phi_2 = B \times A = \left(\frac{\mu_0 i}{2b} \right) \pi a^2$$

$$\phi_2 = \frac{\mu_0 i \pi a^2}{2b}$$

$$d\phi = \phi_2 - \phi_1 = \frac{\mu_0 i \pi a^2}{2b}$$

$$dq = \frac{\mu_0 i \pi a^2}{2 R b}$$

15. **Ans.** 4.6

$$i = \frac{V}{R} (1 - e^{-Rt/L})$$

$$i = \frac{2}{200} [1 - e^{-Rt/L}]$$

Energy stored in magnetic field,

$$E = \frac{1}{2} Li^2$$

$$\frac{dE}{dt} = Li \frac{di}{dt}$$

$$= 2 \left[\frac{2}{200} (1 - e^{-Rt/L}) \right] \times \left[\frac{2}{200} \times \frac{200}{2} e^{-Rt/L} \right]$$

$$= 4.6 \text{ mW}$$

16. Ans. 10

$$\phi = BA \cos \theta = \frac{\mu_0 I}{2\pi} \frac{\pi R^2}{8R^3} \times \frac{\pi r^2}{2} \times \cos 53^\circ = \frac{3\mu_0 \pi r^2}{160R}$$

$$\therefore M = \frac{\phi}{I} = \frac{3}{160} \frac{\mu_0 \pi r^2}{R}$$

17. Ans. 7

Magnetic field at a distance x along axis of a circular coil is given by $B(x) = \frac{\mu_0 i R^2}{2(R^2 + x^2)^{3/2}}$

Flux linked with N coils of square loop inclined at $\theta = 45^\circ$ with vertical is given by

$$\phi(x) = \left[\frac{\mu_0 i R^2}{2(R^2 + x^2)^{3/2}} \right] N(a^2)(\cos 45^\circ)$$

$$\text{As } P = Mi \text{ So } M = \frac{\mu_0 R^2 (2)}{2[R^2 + (\sqrt{3}R)^2]^{3/2}} \left(\frac{a^2}{\sqrt{2}} \right) = \frac{\mu_0 a^2}{2^{7/2} R} \text{ thus } p = 7$$

18. Ans. 2

$$V_L = L \frac{di}{dt}$$

$$di = \frac{V_L}{L} \cdot dt$$

$$L(i_f - i_0) = \text{area under } (V_L - t) \text{ graph}$$

$$4(i_f - i_0) = \frac{1}{2} \times 8 \times 2$$

$$i_f = 2A$$

19. Ans. 80

According to question, $V_L = 2V_R$

$$\text{So } iX_L = 2iR$$

$$\Rightarrow \omega L = 2R$$

$$\text{Frequency } f = \frac{\omega}{2\pi} = \frac{2R}{2\pi L} = \frac{8000}{2\pi} = 1273.88 /s$$

20. Ans. 5

$$\frac{1}{2} = \frac{R}{\sqrt{R^2 + X_C^2}}$$

$$\frac{\sqrt{3}}{2} = \frac{R+10}{\sqrt{(R+10)^2 + X_C^2}}$$

Solving these two equations

$$R = 5\Omega$$

21. Ans. $\frac{20}{\pi^2} \cong 2H$

For power factor to be unity

$$X_L = X_C \quad (\text{Resonance})$$

$$\omega L = \frac{1}{\omega C}$$

$$L = \frac{1}{\omega^2 C} = \frac{1}{(2\pi \times 50)^2 \times 5 \times 10^{-6}}$$

$$= \frac{20}{\pi^2} \approx 2H.$$

22. Ans. $0.2 \text{ mH}, \frac{1}{32} \mu F, 8 \times 10^5 \text{ rad/s}$

$$\omega^R = 4 \times 10^5 \text{ rad/sec}$$

$\therefore$ The circuit is in resonance

$$\therefore V_{\text{rms}} = V_R = 60 \text{ V}$$

$$i_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{60}{120} = \frac{1}{2} \text{ A}$$

$$\text{So, } 40 = i_{\text{rms}} X_L \text{ and } 40 = i_{\text{rms}} X_C$$

$$\begin{aligned} \Rightarrow \omega L = 80 & \quad \Rightarrow \frac{1}{\omega C} = 80 \\ \Rightarrow L = \frac{80}{4 \times 10^5} & \quad \Rightarrow C = \frac{1}{80 \times 4 \times 10^5} \\ \Rightarrow L = 0.2 \text{ mH} & \quad \Rightarrow C = \frac{1}{32} \mu F \end{aligned}$$

If the current lags the voltage by 45° then



$$\tan 45^\circ = \frac{V_L - V_C}{V_R}$$

$$1 = \frac{V_L - V_C}{R} \Rightarrow X_L - X_C = R$$

$$\Rightarrow \omega L - \frac{1}{\omega L} = R$$


Putting the values of L, C and R we get
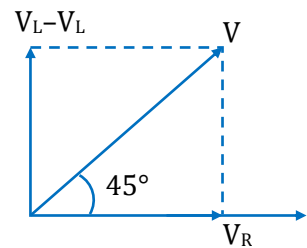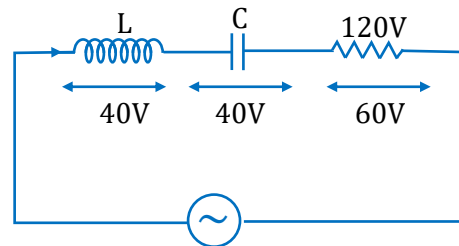
$$\omega = 8 \times 10^5 \text{ rad/sec.}$$



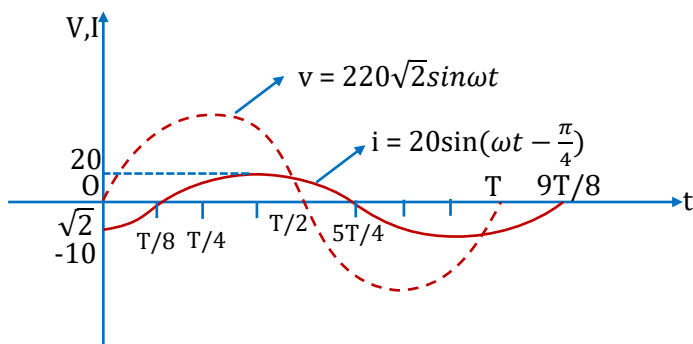23. Ans. 20 A, $\pi/4$,

$$\therefore \text{Steady state current } i = 20 \sin \pi \left(100t - \frac{1}{4} \right)$$



24. Ans. 4

$$1.25 R^2 = R^2 + \left(\frac{1}{\omega C} \right)^2$$

$$0.25 R^2 = \left(\frac{1}{\omega C} \right)^2 ; 0.5 R = \frac{1}{500 \times C} ; C = \frac{1}{250 R} ; RC = \frac{1}{250} \text{ sec}$$

$$\tau = 4 \text{ millisecond}; \tau = 4$$

25. Ans. 77 Ω , 97.6 Ω , 7.7 V, 9.76 V

For i to become maximum, the circuit must be in resonance so angular frequency of the source will be

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4.9 \times 10^{-3} \times 1 \times 10^{-6}}}$$

$$\Rightarrow \omega = \frac{1}{7} \times 10^5 \text{ rad/sec.}$$

So the impedance of P and Q,

$$\Rightarrow Z_P = \sqrt{X_C^2 + R_1^2}$$

$$= \sqrt{\left(\frac{1}{\omega C} \right)^2 + R_1^2}$$


$$= \sqrt{\left(\frac{1}{\frac{1}{7} \times 10^5 \times 10^{-6}} \right)^2 + (32)^2}$$

$$\boxed{Z_P \approx 77 \Omega}$$

$$\text{and } Z_Q = \sqrt{X_L^2 + R_2^2}$$

$$= \sqrt{(\omega L)^2 + R_2^2}$$
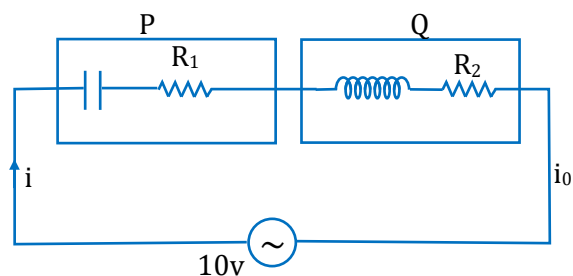
$$= \sqrt{\left(\frac{1}{7} \times 10^5 \times 4.9 \times 10^{-3} \right)^2 + (68)^2}$$



$$\begin{aligned}
 \text{and } Z_Q &= \sqrt{X_L^2 + R_2^2} \\
 &= \sqrt{(\omega L)^2 + R_2^2} \\
 &= \sqrt{\left(\frac{1}{7} \times 10^5 \times 4.9 \times 10^{-3}\right)^2 + (68)^2}
 \end{aligned}$$

Voltage across P and Q

$$\begin{aligned}
 V_p &= i Z_p & V_Q &= i Z_Q \\
 &= \frac{V}{R_1 + R_2} Z_p & &= \frac{V}{R_1 + R_2} Z_Q \\
 &= \frac{10}{100} \times 77 & \boxed{V_Q = 9.76V} \\
 V_p &= 7.7V
 \end{aligned}$$

26. **Ans.** $\frac{F_0 A \omega}{2} \sin \phi$

$$P_{av} = \langle F \cdot V \rangle = A \omega (\omega t - \phi)$$

$$P_{av} = \langle (F_0 \cos \omega t_0) A \omega \sin(\omega t - \phi) \rangle$$

$$= \langle F_0 A \omega \cos \omega t (\sin \omega t \cos \phi - \cos \omega t \sin \phi) \rangle$$

$$= -F_0 A \omega \left(-\frac{\sin \phi}{2} \right) = \frac{F_0 A \omega}{2} \sin \phi$$

EXERCISE - JEE (Main) PYQ


1. **Ans. (1)**

$$V_R + V_L = 0$$

$$\frac{V_R}{V_L} = -1$$

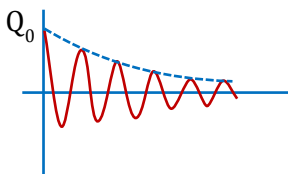2. **Ans. (3)**


As damping is happening, amplitude of charge would vary as



The oscillations decay exponentially and will be proportional to $e^{-\gamma t}$ where γ depends inversely on L .

So as inductance increases decay becomes slower

∴ For

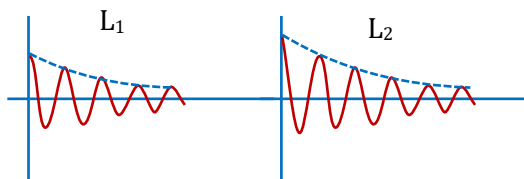

3. **Ans. (1)**

$$I = 10A$$

$$V = 80V$$

$$R = 8\Omega$$

$$10 = \frac{220}{\sqrt{8^2 + X_L^2}}$$

$$X_L^2 + 64 = 484$$

$$X_L = \sqrt{420}$$

$$2\pi \times 50L = \sqrt{420}$$

$$L = \frac{\sqrt{420}}{100\pi}$$

$$L = 0.065 H$$

4. **Ans. (1)**

$$q = \frac{\Delta\phi}{R}$$

$\Delta\phi$ = change in flux

$$q = \int I dt$$

= Area of current-time graph

$$= \frac{1}{2} \times 10 \times 0.5 = 2.5 \text{ coulomb}$$

$$q = \frac{\Delta\phi}{R}$$

$$\Delta\phi = 2.5 \times 100 = 250 \text{ wb}$$

5. **Ans. (4)**

$$\text{Quality factor} = \frac{\omega_0 L}{R}$$

6. **Ans. (4)**

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_s I_s}{V_p I_p}$$

$$\Rightarrow 0.9 = \frac{23 \times I_s}{230 \times 5}$$

$$\Rightarrow I_s = 45A$$

7. **Ans. (2)**

Number of turns of the coil per unit length of the frame is constant i.e.



$$n = \frac{N}{3a} = \text{constant} \Rightarrow N \propto a$$

$$\text{Self inductance} = \mu_0 n^2 A \ell$$

$$= \mu_0 n^2 A (3a \times n)$$

$$\Rightarrow \text{Self inductance} \propto a$$

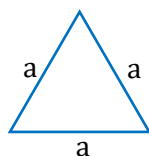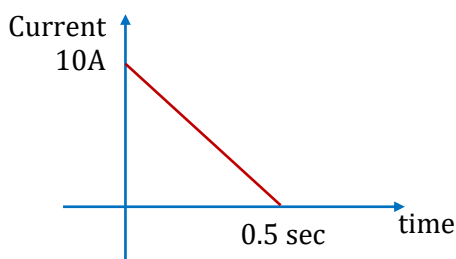So, if $a' = 3a$ then self inductance will become 3 times.



8. **Ans. (2)**

$$T_0 = 2\pi\sqrt{\frac{m}{k}}$$

$$= \frac{2\pi}{\sqrt{10}}$$

$$A = A_0 e^{-t/\gamma}$$

$$\therefore \text{For } A = \frac{A_0}{e}, t = \gamma$$

$$t = \gamma = \frac{2m}{b} = \frac{2m}{\frac{B^2 \ell^2}{R}} = 10^4 \text{ s}$$

$$\therefore \text{No. of oscillation } \frac{t}{T_0} = \frac{10^4}{2\pi/\sqrt{10}} \approx 5000.$$

9. **Ans. (2)**

$$A = A_0 e^{-0.1t} = \frac{A_0}{2}$$

$$\ln 2 = 0.1t$$

$$t = 10 \ln 2 = 6.93 \approx 7 \text{ sec.}$$

10. **Ans. (3)**

$$f = 750 \text{ Hz}, V_{rms} = 20 \text{ V}$$

$$R = 100 \text{ W}, L = 0.1803 \text{ H}$$

$$C = 10 \text{ mF}, S = 2 \text{ J/}^\circ\text{C}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

$$= \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC}\right)^2}$$

Putting values

$$|Z| = 834 \Omega$$

$$\text{In AC power } P = V_{rms} i_{rms} \cos \phi$$

$$\text{We know that } \cos \phi = \frac{R}{|Z|} \text{ and } i_{rms} = \frac{V_{rms}}{|Z|}$$

$$\text{So, } P = \frac{V_{rms}^2 R}{(|Z|)^2} = \left(\frac{20}{834}\right)^2 \times 100 = 0.0575 \text{ J/s}$$

$$H = Pt = S\Delta\theta$$

$$t = \frac{2(10)}{0.0575} = 348 \text{ sec}$$

11. Ans. (3)

$$U_{\max} = \frac{1}{2} L I_{\max}^2$$

$$i = I_{\max} (1 - e^{-Rt/L})$$

For U to be $\frac{U_{\max}}{n}$; i has to be $\frac{I_{\max}}{\sqrt{n}}$


$$\frac{I_{\max}}{\sqrt{n}} = I_{\max} (1 - e^{-Rt/L})$$

$$\Rightarrow e^{-Rt/L} = 1 - \frac{1}{\sqrt{n}} = \frac{\sqrt{n}-1}{\sqrt{n}}$$

$$\Rightarrow -\frac{Rt}{L} = \ln\left(\frac{\sqrt{n}-1}{\sqrt{n}}\right)$$

$$\Rightarrow t = \frac{L}{R} \ln\left(\frac{\sqrt{n}}{\sqrt{n}-1}\right)$$

12. Ans. (3)

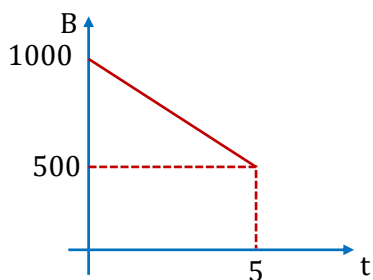

$$\frac{dB}{dt} = 100$$


$$A = 16 \times 4 - 4 \times 2 = 56 \text{ cm}^2$$

$$\epsilon = \frac{dB}{dt} A = 100 \times 10^{-4} \times 56 \times 10^{-4}$$

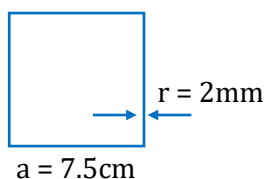13. Ans. (1)

$$q_i = \frac{d(Ba^2)}{dt} = a^2 \frac{dB}{dt}$$

$$i = \frac{q}{R} = \frac{a^2 dB/dt}{\frac{\rho l}{\pi r^2}} = \frac{a^2 dB/dt}{\frac{\rho(30)}{\pi r^2}}$$



14. Ans. (2)

$$B = \frac{\mu_0 i}{2\pi r}$$

$$d\phi = \frac{\mu_0 i}{2\pi r} \ell dr$$

$$\Rightarrow \frac{d\phi}{dt} = \frac{\mu_0 i \ell}{2\pi r} \cdot \frac{dr}{dt}$$

$$\Rightarrow e = \frac{\mu_0}{2\pi} \cdot \frac{iv\ell}{r}$$

$$i = \frac{e}{R} = \frac{\mu_0}{2\pi} \cdot \frac{iv\ell}{Rr}$$

15. Ans. (1)

By kVL

$$-L \frac{di}{dt} - \frac{q}{C} - iR = 0$$

$$L \frac{d^2 q}{dt^2} + \frac{1}{C} q + R \frac{dq}{dt} = 0$$


For damped oscillator

Net force = $-kx - bv = ma$

$$\frac{md^2 x}{dt^2} + kx + \frac{bdx}{dt} = 0$$

By comparing; Equivalence is
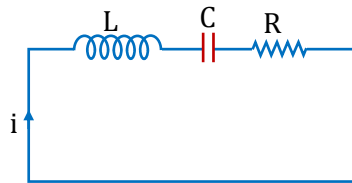
$$L \rightarrow m; C \rightarrow \frac{1}{k}; R \rightarrow b$$



16. Ans. (4)

$$U = \frac{1}{2} Li^2 = 64 \Rightarrow L = 2$$

$$i^2 R = 640$$

$$R = \frac{640}{(8)^2} = 10$$


$$\tau = \frac{L}{R} = \frac{1}{5} = 0.2$$

17. Ans. (1)

$$\cos\phi = \frac{R}{\sqrt{R^2 + 3R^2}} = \frac{1}{\sqrt{10}}, \cos\phi' = \frac{R}{\sqrt{R^2 + R^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{\cos\phi'}{\cos\phi} = \frac{\sqrt{10}}{\sqrt{2}} = \frac{\sqrt{5}}{1}$$

$$\therefore x = 1$$

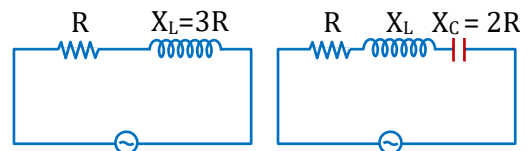

18. Ans. (3)

if $R = 0, P = 0$

19. **Ans. (1)**

Considering sinusoidal AC.

$$\text{Phase at maximum value} = \frac{\pi}{2}$$

$$\text{Phase at rms value} = \frac{3\pi}{4}$$

$$\text{Thus phase change} = \frac{3\pi}{4} - \frac{\pi}{2} = \frac{\pi}{4}$$

$$\begin{aligned}\text{Now } \omega &= 2\pi f \\ &= 2\pi \times 50 \\ &= 100\pi\end{aligned}$$

$$\text{Time taken } t = \frac{\theta}{\omega} = \frac{\pi/4}{100\pi} = \frac{1}{400} \text{ s}$$

$$t = 2.5 \times 10^{-3} = 2.5 \text{ ms}$$

20. **Ans. (242)**

$$f = 50 \text{ Hz}$$

$$\begin{aligned}X_L &= 2\pi fL \\ &= 2\pi(50)(200 \times 10^{-3}) \\ &= 20\pi \Omega\end{aligned}$$

$$\begin{aligned}i_0 &= \frac{V_0}{X_L} \Rightarrow \frac{V_{rms}\sqrt{2}}{X_L} \\ &= \frac{(220)\sqrt{2}}{20\pi} = \frac{11\sqrt{2}}{\pi}\end{aligned}$$

$$\boxed{i_0 = \frac{\sqrt{242}}{\pi}}$$

21. **Ans. (44)**

$$N = 600, A = 70 \times 10^{-4} \text{ m}^2, B = 0.4 \text{ T}$$

$$\omega = \frac{500 \times 2\pi}{60} = \frac{100\pi}{6} \text{ rad/s}$$

$$E = NAB\omega \sin\omega t \quad \omega t \text{ is angle b/w } \vec{A} \text{ \& } \vec{B}$$

$$= 600 \times 70 \times 10^{-4} \times 0.4 \times \frac{100\pi}{6} \times \frac{1}{2}$$

$$= 44 \text{ V}$$

22. **Ans. (9)**

Maximum energy stored in capacitor is same as maximum energy stored in inductor.

$$\frac{1}{2} Li_{\max}^2 = \frac{1}{2} \frac{Q_{\max}^2}{C}$$

$$i_{\max} = \sqrt{\frac{1}{LC}} Q_{\max}$$

$$= \frac{2.7 \times 10^{-6}}{\sqrt{75 \times 10^{-3} \times 1.2 \times 10^{-6}}} = 9 \text{ mA}$$

23. Ans. (40)

To maximize the average rate at which energy supplied i.e. power will be maximum.

So in LCR circuit power will be maximum at the condition of resonance and in resonance condition

$$X_L = X_C$$

24. Ans. (4)

$$\text{Quality factor} = \frac{X_L}{R} = \frac{\omega L}{R}$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 6.25 \times 10^{-6}}} = \frac{10^3}{2.5} = 400 / \text{sec}$$

$$\text{Q-factor} = \frac{400 \times 1}{100} = 4$$

EXERCISE - JEE (Advanced) PYQ

1. Ans. (B)

$$\text{Induce electric field} = \frac{R}{2} \frac{dB}{dt} = \frac{BR}{2}$$


$$\text{Torque on charge} = \frac{QBR^2}{2} (-\hat{k})$$

$$\text{By } \vec{\tau} = \frac{d\vec{L}}{dt} \Rightarrow \int d\vec{L} = \int_0^1 \vec{\tau} dt$$

$$\Delta \vec{L} = \frac{QBR^2}{2} (-\hat{k})$$

$$\text{Change in magnetic dipole moment} = \gamma \Delta \vec{L}$$

$$= \frac{\gamma QBR^2}{2} (-\hat{k})$$

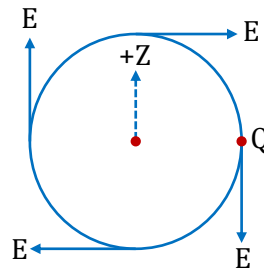

2. Ans. (B)

$$\text{Magnitude of induced electric field} = \frac{R}{2} \frac{dB}{dt} = \frac{BR}{2}$$

3. Ans. (CD)

$$\text{Current } I = I_0 \cos(\omega t)$$

$$\frac{dq}{dt} = I_0 \cos(\omega t)$$


$$\Rightarrow q = \frac{I_0}{\omega} \sin(\omega t)$$

$$\Rightarrow q = \frac{1}{500} \sin(\omega t)$$

$$\Rightarrow q = (2 \times 10^{-3}) \sin(\omega t)$$

$$\text{So, maximum charge} = 2 \times 10^{-3} \text{ C} \quad \left[\text{Immediately before, } t = \frac{7\pi}{6\omega} \right]$$
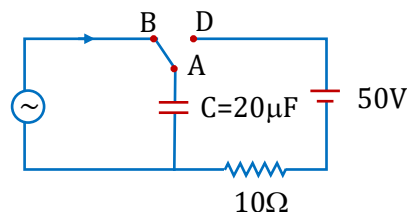
$$\text{Current in left part just before, } t = \frac{7\pi}{6\omega}$$



$$I = I_0 \cos\left(\omega \times \frac{7\pi}{6\omega}\right) = -\frac{I_0\sqrt{3}}{2}$$

Since current is negative hence current will be anticlockwise.

Immediately after, $t = \frac{7\pi}{6\omega}$

$$q = (2 \times 10^{-3}) \sin\left(\omega \times \frac{7\pi}{6\omega}\right) = -1 \times 10^{-3} \text{ C}$$

Current in 10Ω resistance,

$$I = \frac{100}{10} = 10 \text{ A}$$

At steady state, potential difference of capacitor is same as of battery,

So, final charge is

$$Q_f = C\varepsilon = (20 \mu\text{F}) (50 \text{ V}) = +1 \times 10^{-3} \text{ C}$$

$$\text{Change in charge} = +10^{-3} - (-10^{-3}) = 2 \times 10^{-3} \text{ C}$$


4. **Ans. (BD)**

by direction of induced electric field, current in wire is in same direction of current along the hypotenuse.

$$\text{Flux through triangle if wire have current, } i = \int_0^{0.1} \left(\frac{\mu_0 i}{2\pi x} \right) (2x dx) = \frac{\mu_0 i}{10\pi}$$

$$\Rightarrow \text{Mutual inductance} = \frac{\mu_0}{10\pi}$$
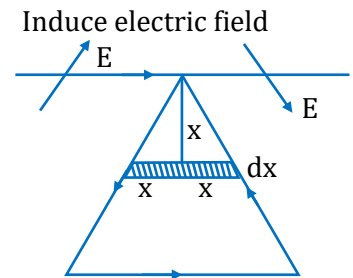
$$\text{Induced emf in wire} = \frac{\mu_0}{10\pi} \frac{di}{dt} = \frac{\mu_0}{10\pi} \times 10 = \frac{\mu_0}{\pi}$$



5. **Ans. (CD)**

When loop was entering ($x < L$)

$$\phi = BLx$$

$$e = -\frac{d\phi}{dt} = -BL \frac{dx}{dt}$$

$$|e| = BLV$$

$$i = \frac{e}{R} = \frac{BLV}{R} \text{ (ACW)}$$


$$F = iLB \text{ (Left direction)} = \frac{B^2 L^2 V}{R} \text{ (in left direction)}$$

$$\Rightarrow a = \frac{F}{m} = -\frac{B^2 L^2 V}{mR} \quad \left(a = V \frac{dV}{dx} \right)$$

$$V \frac{dV}{dx} = -\frac{B^2 L^2 V}{mR} \Rightarrow \int_{V_0}^V dV = -\frac{B^2 L^2}{mR} \int_0^x dx$$

$$\Rightarrow V = V_0 - \frac{B^2 L^2}{mR} x \text{ (straight line of negative slope for } x < L)$$
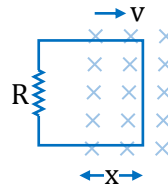
$$I = \frac{BL}{R} V \Rightarrow (I \text{ vs } x \text{ will also be straight line of negative slope for } x < L)$$



$$L \leq x \leq 3L$$


$$\frac{d\phi}{dt} = 0$$

$$e = 0 \quad i = 0$$

$$F = 0$$

$$x > 4L$$

$$e = BLv$$

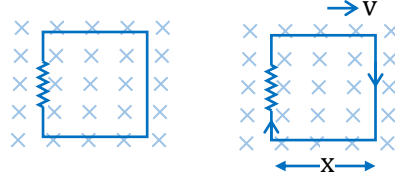

Force also will be in left direction.

$$i = \frac{BLv}{R} \text{ (clockwise)} \quad a = -\frac{B^2 L^2 v}{mR} = -v \frac{dV}{dx}$$

$$F = \frac{B^2 L^2 v}{R} \quad \int_L^x -\frac{B^2 L^2}{mR} dx = \int_{V_i}^{V_f} dV$$

$$\Rightarrow -\frac{B^2 L^2}{mR} (x-L) = V_f - V_i$$

$$V_f = V_i - \frac{B^2 L^2}{mR} (x-L) \text{ (straight line of negative slope)}$$

$$I = \frac{BLv}{R} \rightarrow \text{(Clockwise) (straight line of negative slope)}$$

6. **Ans. (8)**

$$I_{\min} = \frac{\varepsilon}{R} = \frac{5}{12} A \text{ (Initially at } t = 0)$$

$$I_{\max} = \frac{\varepsilon}{R_{eq}} = \varepsilon \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{R} \right) \text{ (Finally in steady state)}$$

$$= 5 \left(\frac{1}{3} + \frac{1}{4} + \frac{1}{12} \right)$$

$$= \frac{10}{3} A$$

$$\frac{I_{\max}}{I_{\min}} = 8$$

7. **Ans. (AB)**

$$(A) \quad \tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R} = 0$$


$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = 10^6 \text{ rad/s}$$

$$(B) \quad i_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}$$

$$\omega \approx 0, i_0 \approx 0$$

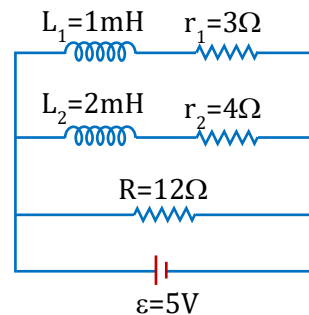For $\omega \gg \omega_0$, circuit behaves as inductor.



8. **Ans. (CD)**

Potential difference between X and Y = $V_X - V_Y$


Potential difference between Y and Z = $V_Y - V_Z$

Phasor of the voltages :

$$\therefore V_X - V_Y = \sqrt{3}V_0$$

$$V_{XY}^{rms} = \frac{\sqrt{3}V_0}{\sqrt{2}}$$
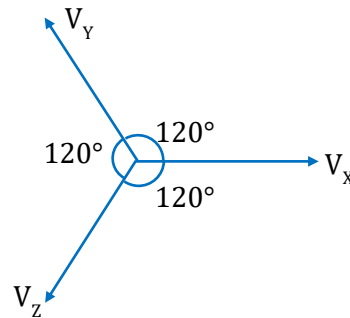
$$\text{Similarly, } V_{YZ}^{rms} = \frac{\sqrt{3}V_0}{\sqrt{2}}$$



Also, difference is independent of choice of two terminals.


9. **Ans. (AD)**

$$f = |B||A|\cos\theta$$

$$= BA \cos(\omega t)$$

$$\varepsilon = -\frac{d\phi}{dt} = BA\omega \sin(\omega t)$$
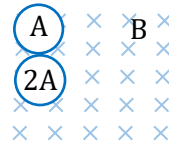
$$\text{so, } \varepsilon \text{ and } \frac{d\phi}{dt} \propto \sin(\omega t)$$



$$\text{so, maximum when, } \omega t = \theta = \frac{\pi}{2}.$$

Net emf will be difference of emfs in both loops because their polarities are opposite.

$$\begin{aligned} \varepsilon_{\text{Net}} &= \varepsilon_{2A} - \varepsilon_A = B(2A)\omega \sin \omega t - B(A)\omega \sin(\omega t) \\ &= B(2A - A)\omega \sin \omega t = BA\omega \sin \omega t \end{aligned}$$

10. **Ans. (ABC)**


Since inductors are connected in parallel

$$V_{L_1} = V_{L_2}$$

$$L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt}$$

$$L_1 I_1 = L_2 I_2$$

$$\frac{I_1}{I_2} = \frac{L_2}{L_1}$$

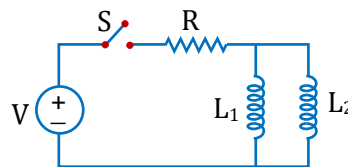

Current through resistor at any time t is given by

$$I = V/R (1 - e^{-\frac{RT}{L}}), \text{ where } L = \frac{L_1 L_2}{L_1 + L_2}$$

$$\text{After long time } I = \frac{V}{R}$$

$$I_1 + I_2 = I \quad \dots(i)$$

$$L_1 I_1 = L_2 I_2 \quad \dots(ii)$$

From (i) & (ii) we get

$$I_1 = \frac{V}{R} \frac{L_2}{L_1 + L_2}, \quad I_2 = \frac{V}{R} \frac{L_1}{L_1 + L_2}$$

(D) value of current is zero at $t = 0$

Value of current is V/R at $t = \infty$

Hence option (D) is incorrect.

11. Ans. (BD)

$$i_{\max} = (i_2 - i_1)_{\max}$$

$$\Delta i = (i_2 - i_1) = \frac{V}{R} \left[1 - e^{-\left(\frac{R}{2L}\right)t} \right] - \frac{V}{R} \left[1 - e^{-\left(\frac{R}{L}\right)t} \right]$$

$$\Rightarrow \frac{V}{R} \left[e^{-\left(\frac{R}{L}\right)t} - e^{-\left(\frac{R}{2L}\right)t} \right]$$

$$\text{For, } (\Delta i)_{\max} = \frac{d(\Delta i)}{dt} = 0$$

$$\Rightarrow \frac{V}{R} \left[-\frac{R}{L} e^{-\left(\frac{R}{L}\right)t} - \left(-\frac{R}{2L}\right) e^{-\left(\frac{R}{2L}\right)t} \right] = 0$$

$$e^{-\left(\frac{R}{L}\right)t} = \frac{1}{2} e^{-\left(\frac{R}{2L}\right)t}$$


$$e^{-\left(\frac{R}{2L}\right)t} = \frac{1}{2}$$

$$\left(\frac{R}{2L}\right)t = \ln 2$$

$$t = \frac{2L}{R} \ln 2 \rightarrow \text{time when } i \text{ is maximum.}$$

$$i_{\max} = \frac{V}{R} \left[e^{-\frac{R}{L} \left(\frac{2L}{R} \ln 2\right)} - e^{-\left(\frac{R}{2L}\right) \left(\frac{2L}{R} \ln 2\right)} \right]$$

$$|i_{\max}| = \frac{V}{R} \left[\frac{1}{4} - \frac{1}{2} \right] = \frac{1}{4} \frac{V}{R}$$

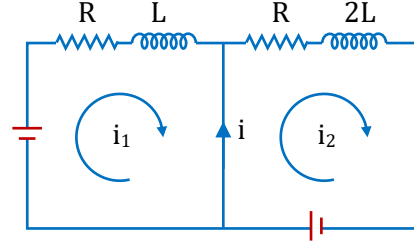

12. Ans. (ABD)

$$y = x^2$$

$$B = B_0 \left[1 + \left(\frac{y}{L} \right)^\beta \right] \hat{k}$$

$$\int d\phi = \int_0^L V_0 B_0 \left(1 + \frac{y^\beta}{L^\beta} \right) \cdot dy$$

$$\Delta\phi = V_0 B_0 \left[L + \frac{L^{\beta+1}}{(\beta+1)L^\beta} \right]$$


$$\Delta\phi = V_0 B_0 \left[L + \frac{L}{\beta+1} \right]$$

$$\therefore |\Delta\phi| = B_0 V_0 \left(1 + \frac{1}{\beta+1} \right) \cdot L$$

$$|\Delta\phi| \propto L$$

$\therefore$ Option 'B' is also correct

If, $\beta = 0$

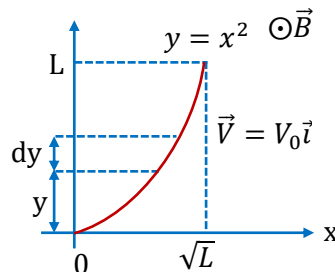

$$\Delta\phi = V_0 B_0 [L + L]$$

$$\Delta\phi = 2V_0 B_0 L$$

⇒ Option (C) is incorrect

If $b = 2$


$$\Delta\phi = V_0 B_0 \left[L + \frac{L}{3} \right]$$

$$\Delta\phi = \frac{4}{3} V_0 B_0 L \text{ option (D) is correct}$$

$\Delta\phi$ will be same if the wire is replaced by the straight wire of length $\sqrt{2}L$ and $y = x$

∴ range of y remains same

∴ Option 1 is correct.

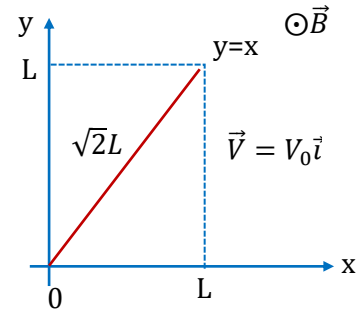

13. **Ans. (0.63)**

Since velocity of PQ is constant. So emf developed across it remains constant.

$\varepsilon = Blv$, where ℓ = length of wire PQ

Current at any time t is given by

$$i = \frac{\varepsilon}{R} \left(1 - e^{-\frac{Rt}{L}} \right)$$

$$i = \frac{B\ell v}{R} \left(1 - e^{-\frac{Rt}{L}} \right)$$

$$= 1 \times \left(\frac{10}{100} \right) \times \left(\frac{1}{100} \right) \times \frac{1}{1} \left(1 - e^{-\frac{-1 \times 10^{-3}}{1 \times 10^{-3}}} \right)$$

$$= \frac{1}{1000} \times (1 - e^{-1}) = \frac{1}{1000} \times (1 - 0.37)$$

$$i = 0.63 \times 10^{-3} A \Rightarrow x = 0.63$$

14. **Ans. (B)**

When the magnet is moved, it creates a state where the plate moves through the magnetic flux, due to which an electromotive force is generated in the plate and eddy currents are induced. These currents are such that it opposes the relative motion $\Rightarrow$ disc will rotate in the direction of rotation of magnet.

Note : This apparatus is called Arago's disk.

Answer is (B).

15. **Ans. (B)**

Torque experienced by circular loop = $\vec{M} \times \vec{B}$

where, $\vec{M}$ is magnetic moment

$\vec{B}$ is magnetic field

$$\therefore \tau = i\pi R^2 N B_0 \text{ [at the instant shown } q = \pi/2]$$

$$\therefore \vec{\tau} dt = d\vec{L} = i\pi R^2 N B_0 dt = Q\pi R^2 N B_0 [idt = Q]$$

Answer is (B).

16. Ans. (55)

Mutual inductance is producing flux in same direction as self inductance.

$$\therefore U = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2$$

$$\Rightarrow U = \frac{1}{2} \times (10 \times 10^{-3}) 1^2 + \frac{1}{2} \times (20 \times 10^{-3}) \times 2^2 + (5 \times 10^{-3}) \times 1 \times 2$$

$$= 55 \text{ mJ}$$

17. Ans. (AC)

EMF developed across the emf of semi-circular rod

$$= \int_1^4 \frac{\mu_0 i}{2\pi r} v dr = \frac{\mu_0 i v}{2\pi} \ln 4 = \frac{\mu_0 i v}{\pi} \ln 2$$

Form given value,

$$E = \frac{4\pi \times 10^{-7} \times 2 \times 3 \times 0.7}{\pi} = 24 \times 7 \times 10^{-8}$$

$$i_{\max} = \frac{E}{R} = \frac{24 \times 7 \times 10^{-8}}{1.4} = 1.2 \times 10^{-6} \text{ A}$$

$$Q_{\max} = C_0 E = 24 \times 7 \times 10^{-8} \times 5 \times 10^{-6} = 8.4 \times 10^{-12} \text{ C}$$

18. Ans. (100.00)**19. Ans. (60.00)**

Solution for Question No. 18 and 19

$$\sqrt{V_C^2 + V_R^2} = \varepsilon_{\text{rms}}$$

$$\Rightarrow V_C^2 + 100^2 = 200^2$$

$$V_C = 100\sqrt{3} \text{ V} \quad \dots(i)$$

$$\tan \phi = \frac{V_C}{V_R} = \frac{100\sqrt{3}}{100}$$

$$\therefore \phi = 60^\circ \quad \dots(ii)$$

$$P = I_{\text{rms}} \varepsilon_{\text{rms}} \cos \phi = \frac{\varepsilon_{\text{rms}}^2}{Z} \frac{1}{2}$$

$$500 = \frac{(200)^2}{Z} \frac{1}{2}$$

$$\therefore Z = 40 \Omega \quad \dots(iii)$$


$$\cos \phi = \frac{R}{Z} \Rightarrow \frac{1}{2} = \frac{R}{40}$$

$$\therefore R = 20$$

$$\text{and } x_C = \sqrt{Z^2 - R^2} = \sqrt{40^2 - 20^2} = 20\sqrt{3} \Omega$$

$$\Rightarrow \frac{1}{\omega C} = 20\sqrt{3} \Omega$$

$$\therefore C = 100$$

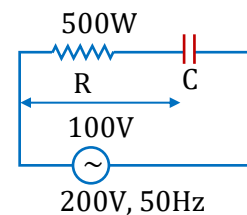

20. Ans. (A)

21. Ans. (C)

Solution for Question No. 20 and 21

$$\phi = Li = \frac{\mu_0 m}{2\pi r^3} \times \pi a^2$$

$$\Rightarrow i = \frac{\mu_0 m \pi a^2}{2\pi r^3 L}$$

$$\Rightarrow i \propto \frac{m}{r^3}$$

$$m' = \pi a^2 i = \frac{\mu_0 m \pi^2 a^4}{2\pi r^3 L}$$

$$F = \frac{k m_1 m_2}{r^4}$$

$$F = \frac{k m^2 \pi^2 a^4}{2\pi r^7 L}$$

$$W = \int F dr \propto \int \frac{m^2 dr}{r^7}$$

22. Ans. (B)

$$V = 45 \sin \omega t, L = 50 \text{ mH}$$

$$\omega_0 = 10^5 \text{ rad/s} = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{L\omega_0^2} = \frac{1}{5 \times 10^{-2} \times 10^{10}}$$

$$= 2 \times 10^{-9} \text{ F}$$

$$I_0 = \frac{45}{R}$$

$$\omega = 8 \times 10^4 \text{ rad/s} = 0.8 \omega_0$$

$$I = 0.05 I_0 = \frac{I_0}{20} \Rightarrow Z = 20R$$

$$X_L = 8 \times 10^4 \times 5 \times 10^{-2} \Omega = 4k\Omega$$

$$X_C = \frac{1}{8 \times 10^4 \times 2 \times 10^{-9}} = \frac{1}{16} \times 10^5 \Omega = \frac{25}{4} k\Omega$$

$$Z^2 = R^2 + (X_C - X_L)^2$$

$$400R^2 = R^2 + \left(\frac{9}{4} k\Omega\right)^2$$

$$R = \frac{\frac{9}{4} k\Omega}{\sqrt{399}} \approx \frac{9}{80} k\Omega = \frac{900}{8} \Omega$$

$$I_0 = \frac{V_0}{R} = \frac{45 \times 8}{900} = \frac{8}{20} A \approx 0.4 A = 400 \text{ mA}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{8}{900} \sqrt{\frac{5 \times 10^{-2}}{2 \times 10^{-9}}} = \frac{8}{900} \sqrt{25 \times 10^6}$$

$$Q = \frac{8}{900} \times 5000 = 44.4$$

$$Q = \frac{\omega_0}{\Delta\omega} \Rightarrow \Delta\omega = \frac{\omega_0}{Q} = \frac{10^5}{44.4} = 2250.0$$

$$P_{\max} = I_0^2 R = \frac{45^2}{R^2} \times R = \frac{45^2}{R} = \frac{45^2}{900} \times 8 = 18.4 \text{ W}$$

23. Ans. (D)

From force equation

$$mg - Bi\ell = \frac{mdv}{dt}$$

$$mg - \frac{B^2\ell^2}{R} \times \ell = \frac{mdv}{dt}$$

$$\frac{mgR}{B^2\ell^2} - v = \frac{mR}{B^2\ell^2} \frac{dv}{dt}$$

$$\frac{B^2\ell^2}{mR} \int_{t=0}^t dt = \int_0^v \frac{dv}{\left(\frac{mgR}{B^2\ell^2} - v\right)}$$

$$\text{Now, } \frac{mgR}{B^2\ell^2} = \frac{20 \times 10^{-3} \times 10 \times 10}{16 \times \frac{1}{16}} = 2$$

$$\text{and } \frac{B^2\ell^2}{mR} = \frac{16 \times \frac{1}{16}}{20 \times 10^{-3} \times 10} = \frac{1}{0.2} = 5$$

$$\therefore 5t = [-\ln(2 - v)]_0^v$$

$$-5t = \ln \left[\frac{2-v}{2} \right]$$

$$\therefore v = 2(1 - e^{-5t})$$

$$\text{At } t = 0.2 \text{ sec} \quad v = 2(1 - e^{-5 \times 0.2})$$

$$v = 2(1 - 0.4)$$

$$v = 1.2 \text{ m/s}$$

(P) Now at $t = 0.2 \text{ sec}$

The magnitude of the induced emf = $E = Bv\ell$

$$= 4 \times 1.2 \times \frac{1}{4} = 1.2 \text{ Volt}$$

(Q) At $t = 0.2 \text{ sec}$, the magnitude of magnetic force = $BI\ell \sin \theta$

$$= B \times \frac{B\ell v}{R} \times \ell \times \sin 90^\circ$$

$$= \frac{4 \times 4 \times \frac{1}{4} \times 1.2 \times \frac{1}{4}}{10} = 0.12 \text{ Newton}$$

(R) At $t = 0.2 \text{ sec}$, the power dissipated as heat

$$P = i^2 R = \frac{v^2}{R} = \frac{1.2 \times 1.2}{10}$$

$$P = 0.144 \text{ watt}$$

(S) Magnitude of terminal velocity

At terminal velocity, the net force become zero

$$\therefore mg = Bi\ell$$

$$mg = B \times \frac{B\ell v_t}{R} \times \ell$$

$$\therefore v_T = \frac{mgR}{B^2\ell^2} = \frac{20 \times 10^{-3} \times 10 \times 10}{16 \times \frac{1}{16}}$$

$$v_T = 2 \text{ m/s}$$

Hence, Answer is (D)

JEE (Main) Practice Paper

SECTION-A

1. **Ans. (1)**

If ' i ' is increased then flux through coil ' B ' also increases. Then according to Lenz' law induced current in coil ' B ' is such that it opposes the initial changing magnetic field Hence repulsion occurs.

2. **Ans. (4)**

$$\text{Flux} = \phi = B.A = BA \cos \theta$$


$$\text{Time period} = T = \frac{2\pi}{\omega}$$

When coil Rotate through 90° , $\phi = 0$

$$\text{Average induced EMF} = \varepsilon = \frac{\Delta\phi}{\Delta t} = \frac{BA}{T/4} = \frac{2\omega BA}{\pi}$$

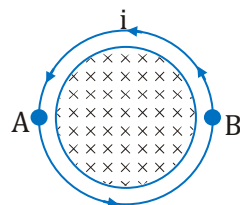
3. **Ans. (1)**

As B increases then according to Lenz law current (i) induced as shown in fig.



Now P & Q short circuited

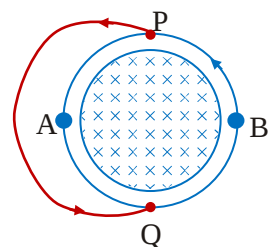Current choose Low resistance path so Balb A goes out & Balb B gets brighter.



4. **Ans. (4)**

$$Q_2 = \frac{(2\omega_1)L}{R} \text{ (as frequency is doubled)} = 2Q, \text{ where } Q_1 = \frac{L\omega_1}{R} \Rightarrow Q \text{ is doubled}$$

$$I_1 = \frac{V}{\sqrt{(L\omega_1)^2 + R^2}} \approx \frac{V}{L\omega_1} \text{ (as } L\omega \gg R \text{ for high } Q \text{ coils)} \text{ Similarly, } I_2 \approx \frac{V}{L(2\omega_1)} \Rightarrow I_2 = \frac{I_1}{2}$$

$$P_2 = I_2 R^2 = \left(\frac{I_1}{2}\right)^2 R^2 = \frac{I_1^2 R^2}{4} = \frac{P_1}{4} \Rightarrow P \text{ decreases 4 times.}$$


5. **Ans. (4)**

$$E - \frac{L di}{dt} = 0$$

$$t = \frac{Li}{E}$$

6. **Ans. (4)**


When switch was is closed

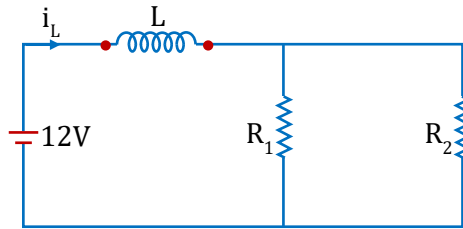

$$i_L = \frac{12}{R_1 || R_2}$$

$$= \frac{12 \times 12}{32} = \frac{9}{2} A$$

Just after switch is opened we know current in inductor does not change instantaneously.

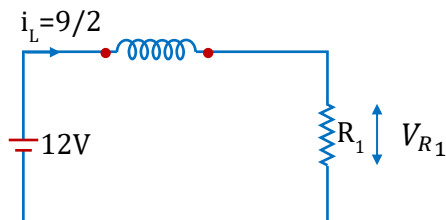Voltage across R_1 is $V_{R_1} = \frac{9}{2} R_1 = 18$ volt.

So voltage across inductor = 6 volt & B is at higher potential.

7. **Ans. (1)**

Field and flux will be outside in ring. So, a clockwise current will be induced as per Lenz law.

8. **Ans. (4)**

When DC applied

$$100 = 1 (R) \Rightarrow R = 100 \Omega$$

When AC applied

$$100 = 0.5 (Z) \Rightarrow Z = 200 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} \Rightarrow 200 = \sqrt{100^2 + X_L^2}$$

$$X_L = \sqrt{200^2 - 100^2}$$

$$\Rightarrow X_L = 100\sqrt{3} \Omega$$

$$L\omega = 100\sqrt{3} \Omega$$


$$\Rightarrow L = \frac{100\sqrt{3}}{100\pi} = \frac{\sqrt{3}}{\pi} = 0.55 H$$

9. **Ans. (4)**

$$\varepsilon = (\vec{v} \times \vec{B}) \cdot d\vec{\ell}$$

$$\varepsilon = \int_{L/2}^L r\omega B dr$$


$$= \frac{3B\omega L^2}{8}$$

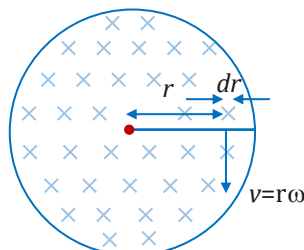

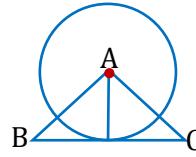10. **Ans. (4)**

$$\int_{AB} \vec{E} \cdot d\vec{\ell} + \int_{BC} \vec{E} \cdot d\vec{\ell} + \int_{CA} \vec{E} \cdot d\vec{\ell} = \frac{\pi R^2}{4} \alpha$$

$$0 + \Delta\varepsilon + 0 = \frac{\pi R^2 \alpha}{4}$$



11. **Ans. (2)**

Induced current (i) is in anticlockwise direction.

So e^- moves tangentially right (clockwise).

12. **Ans. (2)**

For ring to be in equilibrium,

$$\mu mgr \geq Q \frac{\pi r^2 R}{2\pi r} r$$

13. **Ans. (4)**

$$|\varepsilon| = N \frac{d\phi}{dt}$$

$$\phi = BA \cos \theta = BA \cos \omega t$$

$$|\varepsilon| = NBA \omega \sin \omega t$$

Hence, it does not depend on Resistance of coil.

14. **Ans. (2)**

Theoretical.

15. **Ans. (2)**

If $\vec{B}$ is in $\hat{i}$ direction then flux changes in yz plane

$$\text{Therefore, } E = \left| \frac{d\phi}{dt} \right| = \frac{\pi R^2}{4} \times \frac{dB}{dt} = 2.36 \times 10^{-5} V$$

Used Lenz law from C to B.

16. **Ans. (2)**

$$\text{Rate of loss of mechanical energy} \propto \frac{b}{m}$$

$$\text{Hence } \left(\frac{b}{m} \right)_{\text{minimum}} \Rightarrow \text{Smallest loss of mechanical energy}$$

17. **Ans. (4)**

Refer class notes.

18. **Ans. (1)**

$$\text{At Resonance } X_L = X_C \quad \{X_L = L\omega, X_C = \frac{1}{C\omega}\}$$

$$\text{When } \omega \downarrow X_L \downarrow X_C \uparrow$$

So nature of circuit will be capacitive.

19. Ans. (1)

$$I_{rms} = \sqrt{\langle (I_0 + I_1 \sin \omega t)^2 \rangle} = \sqrt{\langle I_0^2 + 2I_0 I_1 \sin \omega t + I_1^2 \sin^2 \omega t \rangle} = \sqrt{I_0^2 + 0.5 I_1^2}$$

(Here ' $\langle \rangle$ ' represent mean)

Average value of $\sin \omega t = 0$ and $\sin^2 \omega t = 0.5$.

20. Ans. (1)

It is oscillating LCR AC circuit

$$L \frac{di}{dt} + \frac{q}{C} + iR = \frac{B\pi a^2 \omega}{2} \sin \omega t$$

$$i_{rms} = \frac{i_{\max}}{\sqrt{2}} = \frac{E_{\max}}{\sqrt{2}R} = \frac{B\pi a^2 \omega}{2\sqrt{2}R}$$

$$= \frac{B\pi a^2}{2R\sqrt{2LC}}$$

maximum energy stored in cap.

$$= \frac{q_{\max}^2}{2C} = \frac{C^2 V_{\max}^2}{2} = \frac{1}{2} C V_{\max}^2$$

$$= \frac{1}{2} C (I_{rms} X_c)^2 = \frac{B^2 \pi^2 a^4}{8R^2 C}$$

maximum power by external agent

$$P = I_{rms} V_{rms}$$

$$= \frac{B^2 \pi^2 a^4}{8LCR}$$

SECTION-B**1. Ans. (2)**

$$|\varepsilon| = (\vec{v} \times \vec{B}) \cdot d\vec{\ell}$$

$$= \left[(2\hat{i} + 3\hat{j} + \hat{k}) \times (\hat{i} + 2\hat{j}) \right] \cdot (2\hat{k})$$

$$= 2 \text{ volt.}$$

2. Ans. (16)

$$P = \frac{\left(\frac{B\omega r^2}{2} \right)^2}{R} = \frac{\left(\frac{20 \times 2 \times 2^2 \times 10^{-4}}{2} \right)^2}{4} = 16 \mu W$$

3. **Ans. (2)**

$$E = \frac{d\phi}{dt} = BA\omega N \sin \omega t$$

$$E_{\max} = BA\omega N = 20V$$

$$I = E/R = 2A$$

4. **Ans. (6)**

At half power frequencies,

$$Z = R\sqrt{2} \Rightarrow |X_L - X_C| = R$$

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2 \Rightarrow \omega^2 L^2 + \frac{1}{\omega^2 C^2} - \frac{2L}{C} = R^2$$

$$\omega^4 L^2 C^2 - \omega^2 \left(\frac{2L}{C} + R^2\right) C^2 + 1 = 0$$

The product of roots is $\omega_1^2 \omega_2^2 = \frac{1}{L^2 C^2} = \omega_1 \omega_2 = \frac{1}{LC} = \omega_0^2$

$$\Rightarrow \omega_0 = \sqrt{\omega_1 \omega_2} = 60 \text{ rad/s} \Rightarrow \omega_0/10 = 6$$

5. **Ans. (3)**

$$\text{Time constant} = \frac{L}{R} = \frac{1}{2}$$

So, EMF will be half at $t = \frac{1}{2} \ln 2$

$$E \Rightarrow \frac{6}{2} = 3V$$

6. **Ans. (125)**

At $t = 0$, $L = \infty \Omega$, $i_1 = 1A$

At $t = \infty$, $L = 0\Omega$, $i_2 = 1.25 A$

7. **Ans. (400)**

$$\tan 60^\circ = \frac{X_L}{R} \quad \& \quad \tan 60^\circ = \frac{X_C}{R}$$

$$X_L = 100\sqrt{3} \Rightarrow X_C = 100\sqrt{3}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 100\Omega$$

$$\text{Power} = V_{\text{RMS}} I_{\text{RMS}} \cos \theta$$

$$= (200) \left(\frac{200}{100}\right) \times 1$$

$$= 400 \text{ watt}$$

8. **Ans. (5)**

$$e = \frac{d\phi}{dt} = \frac{d}{dt} (\pi r^2 B) = 2\pi r B \frac{dr}{dt}$$

$$\Rightarrow r = \frac{e}{\left(2\pi B \frac{dr}{dt}\right)}$$

$$\Rightarrow r = \frac{10^{-6}}{2\pi \times 10^{-3} \times 10^{-2}} = \frac{5}{\pi} \text{ cm}$$

9. **Ans. (6)**

$$V_L^2 + R_R^2 = 150^2 \Rightarrow V_L^2 = 150^2 - 120^2 \Rightarrow V_L = 90 \text{ V}$$

$$\text{Also } V_C^2 + V_R^2 = 130^2 \Rightarrow V_C = 50 \text{ V}$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{120^2 + 40^2} = 40\sqrt{10} = x$$

$$\text{Power factor } \cos \phi = \frac{R}{Z} = \frac{V_R}{V} = \frac{120}{40\sqrt{10}} = \frac{3}{\sqrt{10}} = y$$

10. **Ans. (10)**Suppose the left of the loop has co-ordinate x dx = displacement of loop in time dt dA = area of the element of width $dx = Ldx$ $d\phi$ = flux associated with $dA = \vec{B} \cdot d\vec{A} = BL dx$

$$\phi = \text{flux through the loop} = \int_x^{x+L} (\alpha x) L dx$$

$$= \frac{\alpha L}{2} [(x+L)^2 - x^2] = \frac{\alpha L(2x+L)(L)}{2}$$

$$\varepsilon = \text{induced emf} = \left| -\frac{d\phi}{dt} \right| = \alpha L^2 V = (0.2)(0.2)^2 (10) = 80 \times 10^{-3} \text{ V} \quad \dots (i)$$

As the square moves, the flux increases and so the induced current must produce a field that is out of the page in the interior of the square *i.e.* induced current should flow in anticlockwise direction inside the square.

$$i = \text{induced current} = \frac{80 \times 10^{-2}}{80 \times 10^{-2}} = 1 \text{ A}$$

JEE (Advanced) Practice Paper1. **Ans. (A)**

As field in inerts increasing therefore B induce will be outwards therefore induce current will be form B to A and from D to C .

Therefore B to A and D to C .

2. **Ans. (D)**

For L - R circuit

$$\cos \theta = \left(\frac{R_1}{R_1^2 + X_L^2} \right) = 0.6$$

For C - R circuit

$$\cos \theta_2 = \left(\frac{R_2}{R_2^2 + X_C^2} \right) = 0.5$$

Now when L, C, R of two circuits are joined

$$\cos \theta = \left(\frac{R_1 + R_2}{\sqrt{(R_1 + R_2)^2 + (X_L - X_C)^2}} \right)$$

$$\cos \theta = 1 \text{ (given)}$$

$$\therefore X_C = X_L = X$$

$$\tan \theta_1 = \left(\frac{X_L}{R_1} \right)$$

$$\tan \theta_2 = \left(\frac{X_L}{R_2} \right)$$

$$\frac{\tan \theta_1}{\tan \theta_2} = \frac{X_L}{R_1} \cdot \frac{R_2}{X_C} = \left(\frac{R_2}{R_1} \right)$$

$$\tan \theta_1 = \frac{4}{3}$$

$$\tan \theta_2 = \sqrt{3}$$

$$\therefore \frac{R_1}{R_2} = \frac{3\sqrt{3}}{4}$$

3. **Ans. (A)**

The direction of induced electric field is circular and hence potential drop across wire OA and OB is zero. Hence all induced emf will be in the wire AB .

$$e = -A \frac{dB}{dt} = - \left(-\frac{\pi \times 1^2}{6} \times \frac{6}{\pi} \times 2 \cos 2t \right) = 2 \cos 2t$$

$$\therefore e_{\max} = 2 \text{ volt}$$

4. **Ans. (C)**

$$i_1 = \frac{V_0}{Z_1} ; i_2 = \frac{V_0}{Z_2}$$

$$\text{We have, } Z = \sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}, \text{ thus } \omega \uparrow, Z \downarrow \Rightarrow i \text{ increases}$$

5. **Ans. (C)**

$$\text{Here } \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 10^{-3} \times 50 \times 10^{-6}}} = 2000 \text{ rad/s}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}} \text{ so, resonance condition}$$

$$\Rightarrow I = \frac{V}{R} = \frac{20/\sqrt{2}}{6+4} = \sqrt{2} = 1.4 \text{ A}$$

$$\Rightarrow \text{Reading of ammeter} = 1.4 \text{ A.}$$

$$\Rightarrow \text{Reading of voltmeter} = 4\sqrt{2} \text{ V} = 5.6 \text{ V}$$

6. **Ans. (ABCD)**

For (A) Expression of voltage of time 't': $V = V_m \sin(\omega t + \phi)$

$$\text{At } t = 0: 100 = 200 \sin \phi \Rightarrow \phi = \frac{\pi}{6} \text{ rad; current lags voltage by } \frac{\pi}{6} \text{ rad}$$

$$\text{For (B)} \quad R = Z \cos \phi = \frac{200 \text{ V}}{400 \text{ mA}} \cos \frac{\pi}{6} = 250\sqrt{3} \Omega$$

$$\text{For (C)} \quad X = Z \sin \phi = 250 \Omega$$

$$\text{For (D)} \quad P_{av} = \frac{V_m I_m}{2} \cos \phi = 20\sqrt{3} \text{ W}$$

7. **Ans. (ABC)**

$$I_1 = \frac{V_{rms}}{Z_1} = \frac{40}{100\sqrt{2}} = \frac{\sqrt{2}}{5} \text{ A at } 45^\circ \text{ leading}$$


$$I_2 = \frac{V_{rms}}{Z_2} = \frac{40}{50\sqrt{2}} = \frac{2\sqrt{2}}{5} \text{ A at } 45^\circ \text{ lagging}$$

So, I_1 is 90° ahead of I_2

$$I_{res} = \sqrt{I_1^2 + I_2^2} = \frac{2}{\sqrt{10}} \text{ A}$$

$$V_{R_1} = I_1 R_1 = \frac{\sqrt{2}}{5} \times 100 = 20\sqrt{2} \text{ V}$$
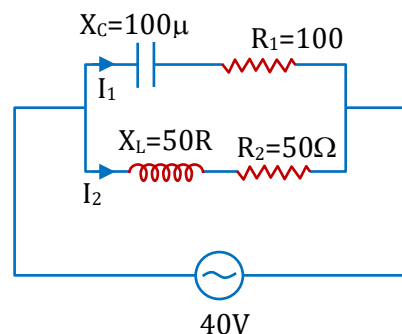
$$V_{R_2} = I_2 R_2 = \frac{2\sqrt{2}}{5} \times 50 = 20\sqrt{2} \text{ V}$$



8. **Ans. (B)**

$$\tan \phi_L = \frac{X_L}{R} ; \tan \phi_C = \frac{X_C}{R}$$

$$\tan \phi_L = \omega \sqrt{LC} ; \tan \phi_C = \frac{1}{\omega \sqrt{LC}} \quad \left[\because R = \sqrt{\frac{L}{C}} \right]$$

We know that

$$\tan(A+B) = \frac{\tan A + \tan B}{1 - \tan A \tan B}$$

$$\text{Here, } \tan(\phi_L + \phi_C) = \frac{\tan \phi_L + \tan \phi_C}{1 - \tan \phi_L \tan \phi_C} = \infty$$

$$\Rightarrow \phi_L + \phi_C = 90^\circ$$

$$\text{So, } I = \sqrt{I_L^2 + I_C^2}$$

$$I^2 = \frac{V_{rms}^2}{R^2 + \omega^2 L^2} + \frac{V_{rms}^2}{R^2 + \frac{1}{\omega^2 C^2}}$$

$$I^2 = \frac{V_{rms}^2}{\frac{L}{C} + \omega^2 L^2} + \frac{V_{rms}^2}{\frac{L}{C} + \frac{1}{\omega^2 C^2}}$$

$$= \frac{V_{rms}^2 C}{L} \left(\frac{1}{1 + \omega^2 LC} + \frac{1}{1 + \frac{1}{\omega^2 LC}} \right)$$

$$= \frac{V_{rms}^2}{R^2}$$

$$\text{So, } I = \frac{V_{rms}}{R}$$

and Impedance of circuit is independent of ω .

9. **Ans. (AC)**

I_2 is in phase with voltage of source; I_1 leads the voltage by $\frac{\pi}{2}$

I is the resultant of I_1 and I_2 .

10. **Ans. (B)**

For unity power factor, box must contain inductor.



11. Ans. (A)

$$\frac{R}{Z} = \frac{1}{\sqrt{2}} \Rightarrow Z = \sqrt{2}R$$

$$\text{Also, } R = X_L = X_C$$

$$\text{So, } Z = \frac{\sqrt{2}}{\omega C}$$

12. Ans. (A)

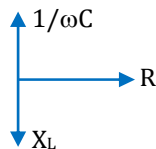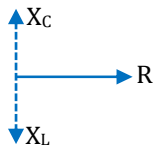

$$Z = \sqrt{X_L^2 + R^2} = R\sqrt{2} \quad X_L = X_C = 1/\omega C$$

$$\text{So, } X_L = X_C = R \quad \text{So, the circuit is in resonance.}$$

$$\text{So, } Z = \sqrt{2} \cdot \frac{1}{\omega C}$$

13. Ans. (16)

$$\vec{A} = 4\hat{k} \text{ for } x\text{-}y \text{ plane}$$

$$\phi = \vec{B} \cdot \vec{A} = B_0(2\hat{i} + 3\hat{j} + 4\hat{k}) \cdot 4\hat{k} = 16 B_0$$

14. Ans. (8)

KCL of junction :

$$i_1 + i_2 - i_L + i_C = 0$$

$$i_C = i_L - (i_1 + i_2)$$

$$\frac{dq}{dt} = i_L - (i_1 + i_2)$$

$$C \left(\frac{dV_C}{dt} \right) = i_L - (i_1 + i_2)$$

$$2(-6e^{-2t}) = i_L - (10e^{-2t} + 4)$$

$$i_L = -2e^{-2t} + 4$$

$$V_L = -L \frac{di}{dt} = -4[4e^{-2t} + 0] = -16e^{-2t}$$

$$a = -16, b = 2$$

$$\left| \frac{a}{b} \right| = 8$$


15. Ans. (0.05)

$$\Delta t = \frac{2Q}{\omega} \ell n \eta = 0.05 \text{ sec}$$

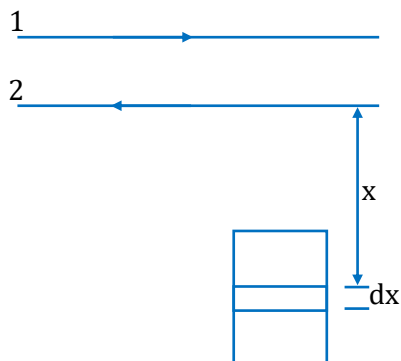16. Ans. (2)

$$d\phi = \int_d^{2d} \left(\frac{\mu_0 i}{2\pi x} \right) dx - \int_{2d}^{3d} \left(\frac{\mu_0 i}{2\pi x} \right) dx = \frac{\mu_0 i d}{2\pi} \left\{ \ell n 2 - \ell n \left(\frac{3}{2} \right) \right\}$$

$$\phi = \frac{\mu_0 i d}{2\pi} \ell n \left(\frac{4}{3} \right)$$



$$\varepsilon = -\frac{d\phi}{dt} = -\frac{\mu_0 d}{2\pi} \ell n \left(\frac{4}{3} \right) \frac{dI}{dt}$$

17. Ans. (6)

$$\text{Apply KVL, } E - IR - L \frac{dI}{dt} - \frac{q}{C} = 0$$