

19. $V_{old} = AL$

$$V = AL \quad R = \frac{\rho L}{A}$$

New

$$L' = L + \frac{L}{5} = \frac{6}{5} L$$

$$V = A'L' = AL$$

$$A' = \frac{5A}{6}$$

$$R' = \frac{\rho L'}{A'} = \frac{36}{25} R$$

$$\% \text{ change} = \frac{R' - R}{R} \times 100 = 44\%$$

20. Volume remains same $\Rightarrow AL = A'(2L)$


$$A' = \frac{A}{2}; R_i = \frac{\rho L}{A}$$

$$R_f = \frac{\rho(2L)}{(A/2)} = 4R_i$$

$$\% \text{ change} = \frac{4R_i - R_i}{R_i} \times 100 = 300\%$$

21. Increase and decrease respectively.

22.

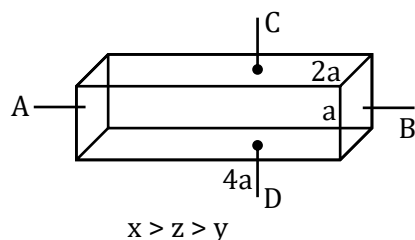

$$\left(R = \rho \frac{\ell}{A} \right), A = \text{Area of crosssection.}$$

23. The value ρ does not depend on geometry but increases with increase in temperature

24. $R = R_0 (1 + \alpha \Delta T)$

$$1 = R_0 [1 + \alpha(27)]$$

$$2 = R_0 [1 + \alpha(T)] \Rightarrow \frac{1}{2} = \frac{1 + \alpha \times 27}{1 + \alpha \times T} \text{ solve it.}$$

25. For I - V slope = $\frac{I}{V} \propto \frac{1}{R} \propto \frac{1}{T}$ curve

Slope $\downarrow$ $R \uparrow$ $T \uparrow$

$$\therefore R_2 > R_1 \therefore T_2 > T_1$$

26. $\frac{2R}{2+R} = \frac{6}{5}$

$$10R = 12 + 6R; R = 3 \Omega$$

27. $R = R_0 (1 + \alpha \Delta t)$

$$3R_0 = R_0 (1 + 4 \times 10^{-3} T)$$

$$2 = 4 \times 10^{-3} T \Rightarrow T = \frac{1000}{2} = 500^\circ \text{C}$$

28. For conductor, $T \downarrow \rho \downarrow$

For semiconductor, $T \downarrow \rho \uparrow$



29. $R_1 = R_{01} (1 + \alpha \Delta T)$

$$R_2 = R_{02} (1 - \beta \Delta T)$$


$$R_{\text{series}} = R_1 + R_2 = R_{01} + (R_{01}\alpha - R_{02}\beta)\Delta T + R_{02}$$

Not depend on temperature
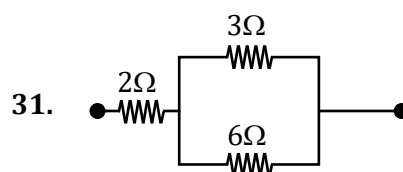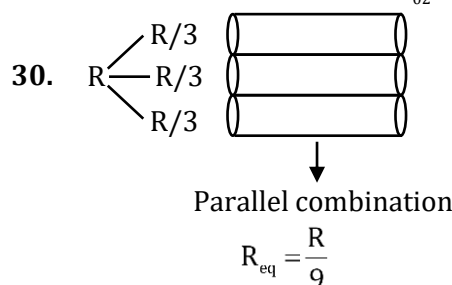
$$R_{01}\alpha - R_{02}\beta = 0 \Rightarrow \frac{R_{01}}{R_{02}} = \frac{\beta}{\alpha}$$



32. Redraw circuit

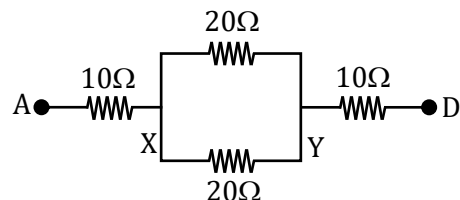


$$R_{AD} = 30 \Omega$$

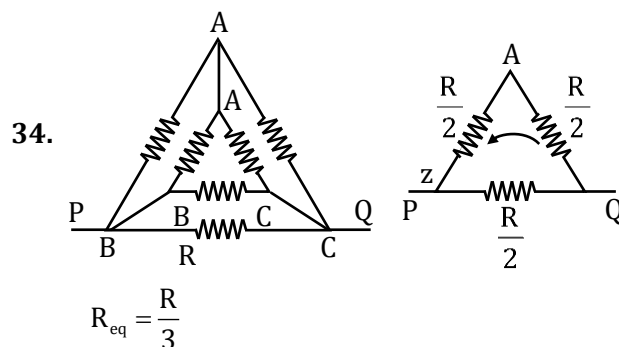
33. $\frac{(R+3) \cdot 10}{(R+3)+10} + 3 = R$ (given)

$$\text{solve it } (10R + 30) = (R - 3)(R + 13)$$


$$10R + 30 = R^2 - 39 + 10R \text{ or } R = \sqrt{69} \Omega$$



35. After folding symmetry


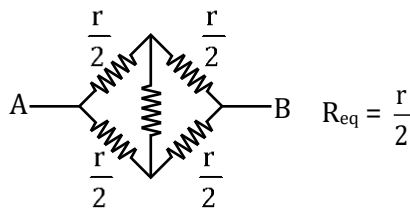


36. It is balance Wheat Stone Bridge

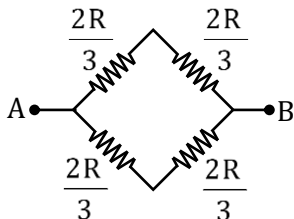

$$R_{AB} = \frac{2R}{3} \Omega$$

37. Redrawing the circuit

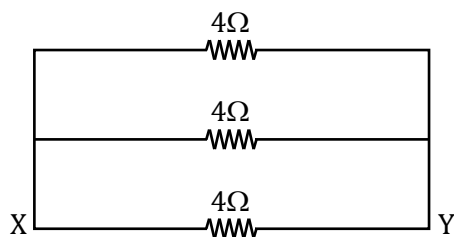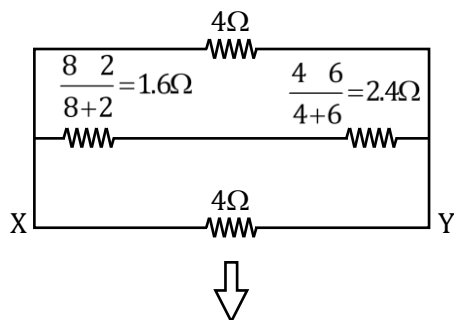

$$R_{eq} = \frac{4}{3}$$



38. When they are connected in parallel

$$\text{Then } R = \frac{r}{n} \Rightarrow r = nR$$

When they are connected in series

$$\text{Then } R_{eq} = nr = n \times nR = n^2 R$$


39.

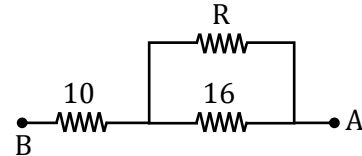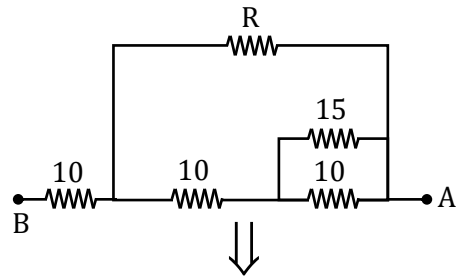

$$\frac{16R}{16+R} + 10 = 18$$


40. $R_{AB} = 20\Omega$ Multiple W.S.B.

41.

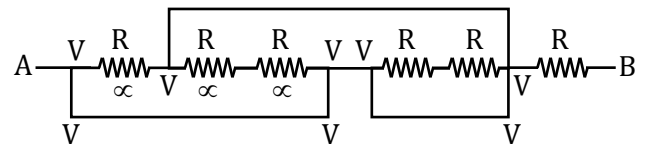

$$R_{eq} = R$$

42. $R_{eq} = 6\Omega$

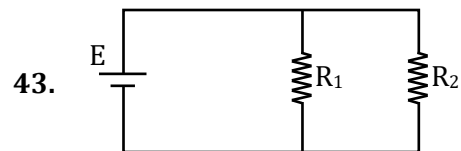

43.

$$\frac{R_1 R_2}{R_1 + R_2} = 6\Omega \Rightarrow R_1 \text{ could be } = 8\Omega$$

44. $I_{in} = I_{out}$

$$10 + 1 + 2 = I \Rightarrow I = 13A$$


45. $V_x + 2 \times 1 - 3 \times 1 = V_y$

$$V_x - V_y = +1 \text{ volt}$$

$$46. I = \frac{V}{R_{eq}} = \frac{9}{\frac{9}{5}} = 5 \text{ A}$$

$$47. i = 0.25 = \frac{12}{R+6} \Rightarrow R + 6 = 48 \Rightarrow R = 42 \Omega$$
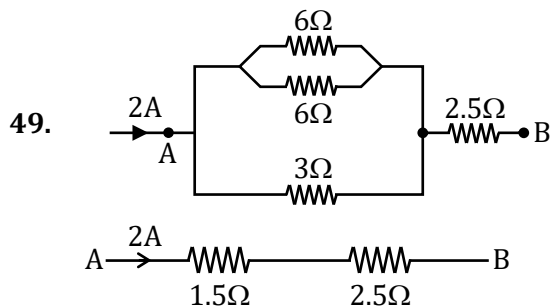
$$48. i = 2 \text{ A} = \frac{6}{2+R} \Rightarrow R = 1\Omega$$



$$R_{eq} = 4\Omega \quad V_{eq} = 8V$$

50. In loop AHDCBA


$$-30 I_1 - 45 - I_3 - 40 I_3 = 0$$

$$-30 I_1 - 41 I_3 - 45 = 0$$

In loop AHDCBA

$$-30 I_1 + 20 I_2 + 1 I_2 - 80 = 0$$

$$-30 I_1 + 21 I_2 - 80 = 0$$

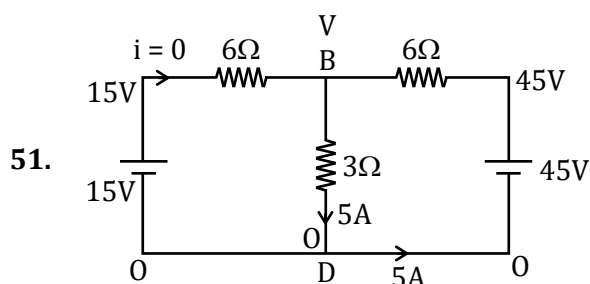


$$\frac{V-15}{6} + \frac{V}{3} + \frac{V-45}{6}$$

$$V - 15 + 2V + V - 45 = 0$$

$$4V = 60$$

$$V = 15V$$
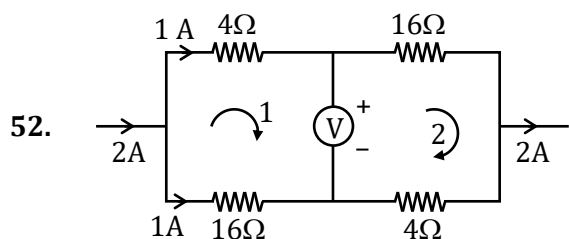
$$\therefore i_{BD} = \frac{V}{3} = \frac{15}{3} A = 5A$$




By KVL in loop (1)


$$-4 \times 1 - V + 16 \times 1 = 0$$

$$V = 12 \text{ Volts}$$

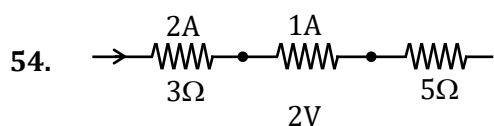
53. $V_{JG} = \frac{32}{32+34} \times 60 = 20V$



55. $i = \frac{3E}{7R}$

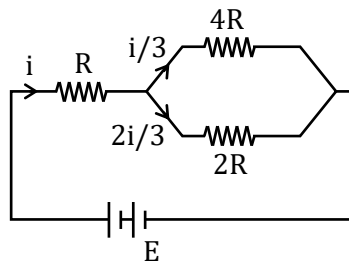

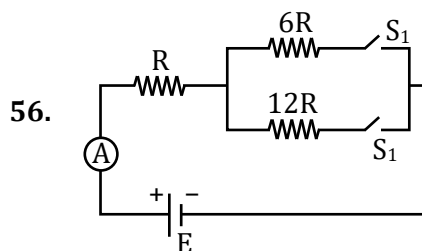
$$V = (2R) \frac{2}{3} \left(\frac{3E}{7R} \right) = \frac{4}{7} E$$



$$I_1 = \frac{E}{7R} \quad I_2 = \frac{E}{13R} \quad I_3 = \frac{E}{5R}$$

$$I_3 > I_1 > I_2$$

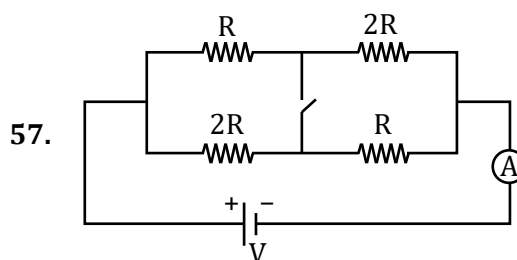


when key open when key closed

$$R_{eq} = \frac{3R}{2}$$


$$R_{eq} = \frac{4R}{3}$$

$$i_0 = \frac{2V}{3R}$$


$$i_c = \frac{3V}{4R}$$

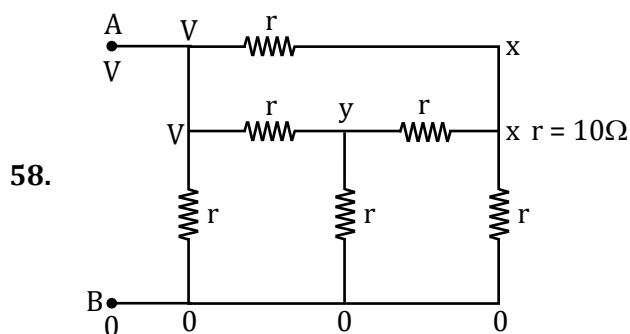

Balanced Wheat Stone Bridge

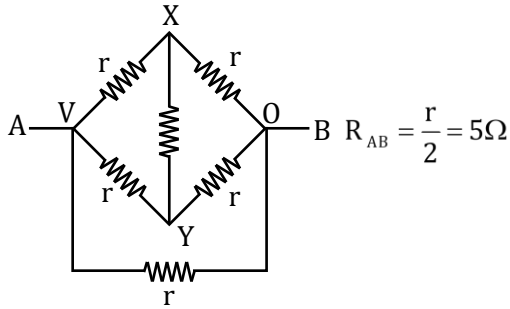


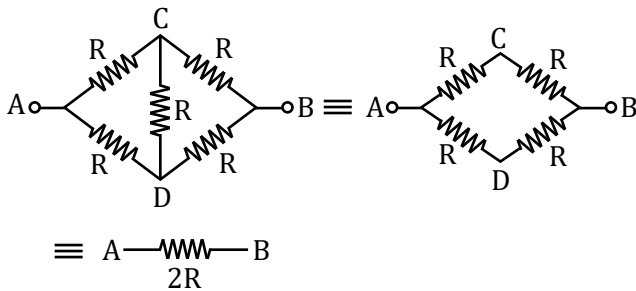59. Given circuit can be reduced to
Balanced Wheat Stone Bridge



$$\text{Required current} = \frac{V}{2R}$$


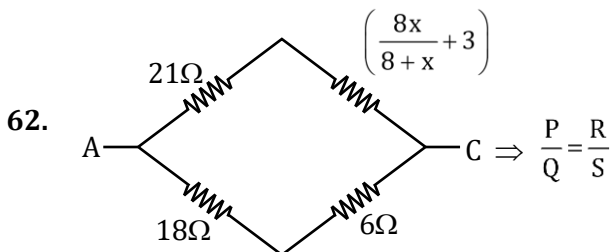
60. Option (3) is correct.
61. Wheatstone bridge is in balance condition



63. For balance wheat stone bridge

$$\frac{16}{4} = \frac{x}{1/2}; x = 2\Omega.$$


64. $R_{eq} = 10\Omega$

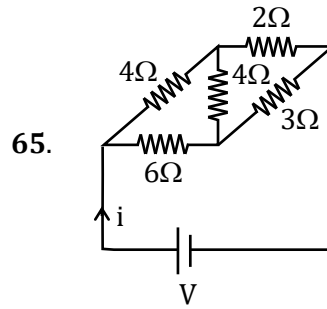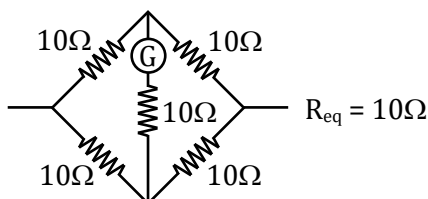

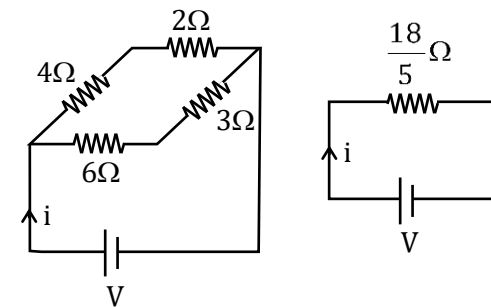65.

$$\text{Here } \frac{4}{6} = \frac{2}{3} \Rightarrow \text{Balanced Wheat Stone Bridge}$$

Therefore given circuit can be reduced to



$$\Rightarrow i = \frac{5V}{18}$$

66. $V = E - Ir = 4 - \frac{10}{20} \times 8 = 0V (\because I = \frac{10}{20} = \frac{1}{2} A)$


67. When battery is connected to external resistance

$$\frac{4}{2+r} = 1 \Rightarrow r = 2\Omega$$

When terminals of battery are connected directly

$$i = 4/2 = 2A$$


68. All

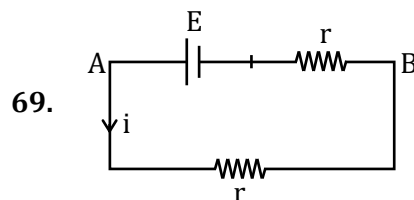

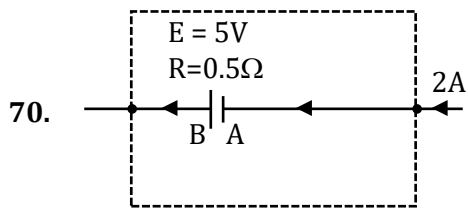69.


$$V_{AB} = 3 \Rightarrow i = 3/r$$

$$E - ir = 3 \Rightarrow E = 3 + ir = 3 + 3 = 6V$$



$$V_A + 5 - 2 \times 0.5 = V_B$$
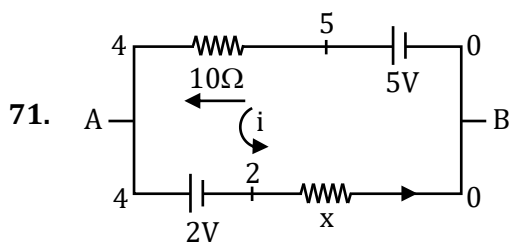
$$10 + 5 - 1 = V_B \Rightarrow V_B = 14V$$



$$i = \frac{5-4}{10} = 0.1A$$

$$x \times 0.1 = 2 \Rightarrow x = 20\Omega$$



72. emf is basically work

73. $\therefore I = \frac{E}{2+r}$, terminal potential $\frac{E}{2} = E - Ir$

$$\Rightarrow \frac{E}{2} = E - \frac{E}{2+r} r$$

$$\Rightarrow 2 + r = 2r$$

$$\Rightarrow r = 2\Omega$$

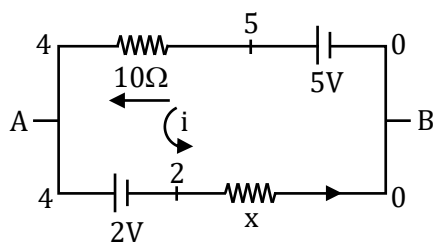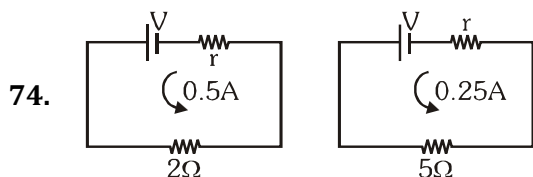

$$V = 0.5(2+r) \quad \dots(i)$$

$$V = 0.25(5+r) \quad \dots(ii)$$


for (i) & (ii)

$$0.5(2+r) = 0.25(5+r)$$

$$4 + 2r = 5 + r$$

$$r = 1$$

$$V = 0.5 \times 3 = 1.5V$$

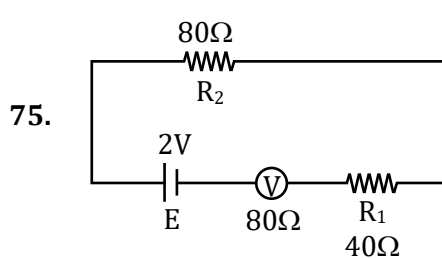

$$i = \frac{2}{200} = 0.01 A$$

$$V = 0.8 V$$

76. $0.9 = \frac{V}{2+r}$

$$0.3 = \frac{V}{7+r}$$

$$1.8 + 0.9r = 2.1 + 0.3r$$

$$0.6r = 0.3$$

$$r = \frac{1}{2} \Omega$$

77. for maximum power $R_{\text{internal}} = R_{\text{ext.}}$

78. $R = \frac{V_0^2}{P_0}$; $P = \frac{V^2}{R} = \frac{V^2}{V_0^2} P_0 = \left(\frac{V}{V_0}\right)^2 P_0$


79. $P = \frac{V^2}{R_{\text{eq.}}} \Rightarrow R_{\text{eq.}} \downarrow P \uparrow$

80. $P = i^2 R$ Current is same, so $P \propto R$.

In the first case it is $3r$, in second case it is $(2/3)r$, in III case it is $\frac{r}{3}$ & in IV case the net

resistance is $\frac{3r}{2}$

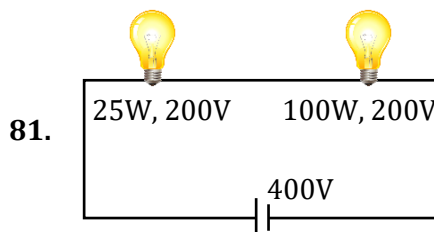
$$R_{\text{III}} < R_{\text{II}} < R_{\text{IV}} < R_1 \therefore P_{\text{III}} < P_{\text{II}} < P_{\text{IV}} < P_1$$



$$R = \frac{V_{\text{rated}}^2}{P_{\text{rated}}}; R_1 = \frac{(200)^2}{25}; R_2 = \frac{(200)^2}{100}$$

$$R_1 > R_2; V_1 > V_2$$

thats why 25 W bulb fuse first

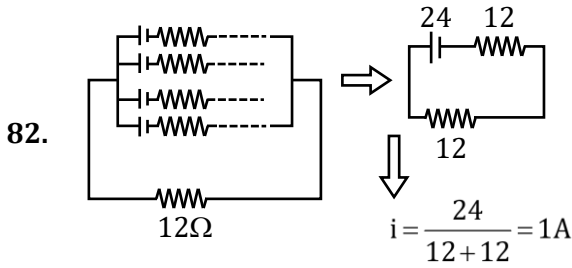

$$\text{For } I_{\max} = \frac{nr}{m} = R \quad \dots(1)$$

n = number of column


m = number of row

$$nm = 48 \quad \dots(2)$$

from eq (1) and (2)

$$n = 12$$

$$m = 4$$

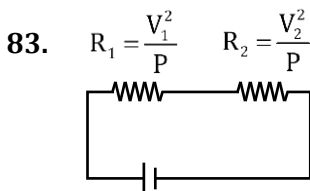


$$i = \frac{\varepsilon}{\left(\frac{V_1^2}{P} + \frac{V_2^2}{P}\right)}; \text{Brightness} \propto \text{power} = (i^2 R)$$

$$P_i = \frac{\varepsilon^2 V_1^2}{(V_1^2 + V_2^2)}$$

84. $P = \frac{V^2}{R_{\text{eq}}}; R_{\text{eq}} \downarrow P \uparrow$

85. For maximum power internal resistance should be equal to external resistance ($R_{\text{int}} = R_{\text{ext}}$)

$$R = \frac{r}{2}$$

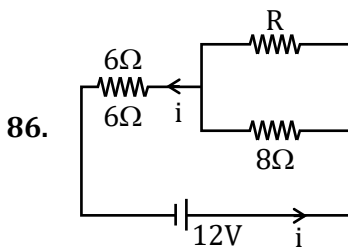

$$i^2 6 = 6 \Rightarrow i = \sqrt{\frac{6}{6}} = 1A$$


$$\left(6 + \frac{8R}{8+R}\right) = 6$$

$$\frac{8R}{8+R} = 6; 4R = 24 + 3R \Rightarrow R = 24 \Omega$$


87. $\max \rightarrow R = 1 \Rightarrow P = i^2 R = 4W$

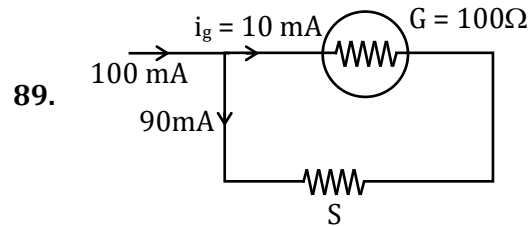88. Net resistance of system will decrease.

$\therefore$ Reading of A will increase & reading of V will decrease.


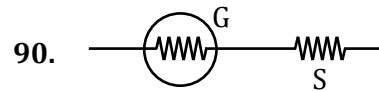
$$100 \times 10 = 90 S \Rightarrow S = \frac{100}{9} \Omega$$



$$V = G i_g$$

$$nV = (G + S)i_g \Rightarrow n = \left(\frac{G+S}{G}\right) \Rightarrow S = (n-1)G$$


91. Initially

$$\frac{R_1}{R_2} = \frac{x}{(1-x)} = \frac{10}{30} \Rightarrow x = 25 \text{ cm}$$

Finally after interchange

$$\frac{y}{1-y} = \frac{30}{10} \Rightarrow y = 75 \text{ cm}$$

shifting = 50 cm

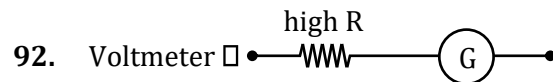


93. If radius of wire is doubled then resistance becomes 1/4 times but ratio of AC : CB remains same.

94. $V = I(R + R_A) \Rightarrow 12 = 0.1(R + 20)$

$$\Rightarrow R = \frac{12}{0.1} - 20 \quad R = 100 \Omega$$

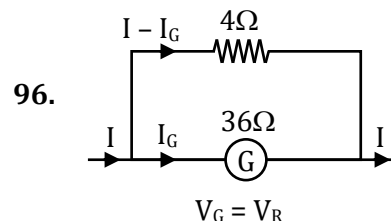95. $R = (n-1)G$


$$\text{Here } n = \frac{10}{1} = 10 \Rightarrow R = (10-1)G = 9G$$



$$V_G = V_R$$

$$\Rightarrow 4(I - I_G) = 36I_G$$
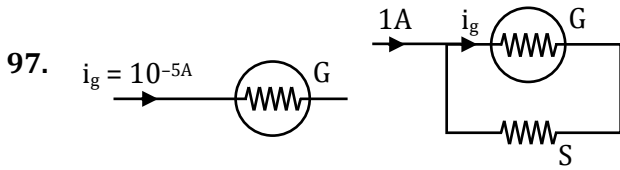
$$\Rightarrow 10I_G = I \Rightarrow \frac{I_G}{I} = \frac{1}{10}$$




$$V = 10^{-3} \text{ V} \quad G i_g = S (1 - i_g)$$

$$10^{-3} = S (1 - 10^{-5})$$

$$S \approx 10^{-3} \Omega$$

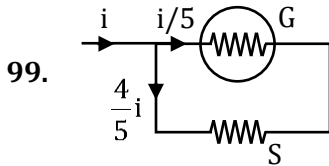98. High resistance $\Rightarrow$ Good voltmeter




$$\frac{i}{5} G = \frac{4i}{5} S; S = \frac{G}{4}$$

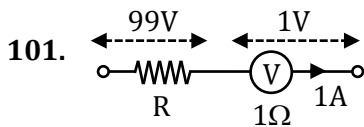
100. $\frac{R_1 + 10}{R_2} = \frac{50}{50} = 1 \Rightarrow R_1 + 10 = R_2 \quad \dots (i)$

$$\frac{R_1}{R_2} = \frac{40}{60} \Rightarrow 3R_1 = 2R_2 \quad \dots (ii)$$

$$R_1 + 10 = \frac{3}{2} R_1 \Rightarrow R_1 = 20 \Omega$$


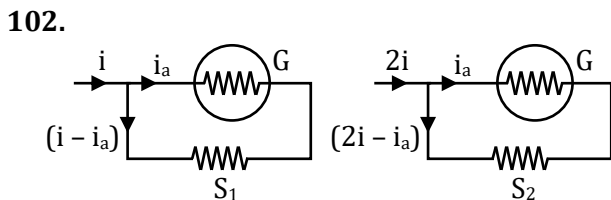
$$99 = 1 \times R \Rightarrow R = 99 \Omega$$



$$G i_a = S_1 (i - i_a) \quad \dots (i)$$

$$G i_a = (2i - i_a) S_2 \quad \dots (ii)$$


$$\text{Equation (i)} = \text{(ii)}$$

$$S_1 (i - i_a) = S_2 (2i - i_a) \Rightarrow \frac{S_1}{S_2} = \left(\frac{2i - i_a}{i - i_a} \right)$$

Exercise-II (Previous Year Questions)

1. Resistance = $(0.5 \Omega/\text{km}) (150 \text{ km}) = 75 \Omega$
 Total voltage drop = $(8 \text{ V/km}) (150 \text{ km}) = 1200 \text{ V}$
 Power loss = $\frac{(\Delta V)^2}{R} = \frac{(1200)^2}{75} \text{ W}$
 $= 19200 \text{ W} = 19.2 \text{ kW}$

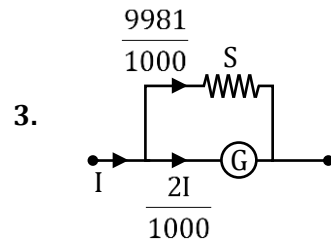2. $\frac{5}{R} = \frac{\ell_1}{100 - \ell_1}$ and $\frac{5}{R/2} = \frac{1.6 \ell_1}{100 - 1.6 \ell_1}$
 $\Rightarrow R = 15 \Omega$




$$\left(\frac{2I}{1000} \right) G = \left(\frac{998I}{1000} \right) S$$

$$\Rightarrow S = \frac{G}{499}$$


Total resistance of Ammeter
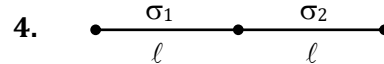
$$R = \frac{SG}{S + G} = \frac{\left(\frac{G}{499} \right) G}{\left(\frac{G}{499} \right) + G} = \frac{G}{500}$$



$$R_{eq} = R_1 + R_2$$

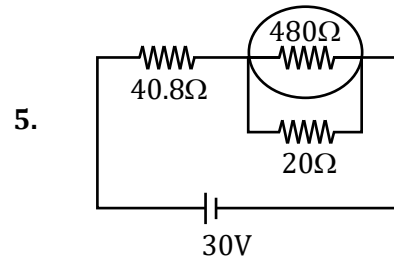
$$\Rightarrow \frac{2\ell}{\sigma_{eq} A} = \frac{\ell}{\sigma_1 A} + \frac{\ell}{\sigma_2 A} \Rightarrow \sigma_{eq} = \frac{2\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$$



$$R_{eff} = 40.8 + \frac{480 \times 20}{480 + 20} = 40.8 + 19.2 = 60 \Omega$$

$$I = \frac{V_{eff}}{R_{eff}} = 0.5 \text{ A}$$

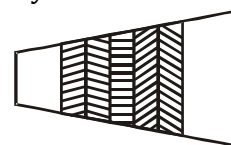6. Metallic conductor can be considered as the combination of various conductors connected in series combination. In series combination the current always remains constant.




7. Effective resistance of B & C = $\frac{(1.5R)(3R)}{1.5R + 3R} = R$

In series sequence $V \propto R$

so voltage across 'A' = voltage across B & C


Now B & C are parallel so $V_B = V_C$

$$\Rightarrow V_A = V_B = V_C$$

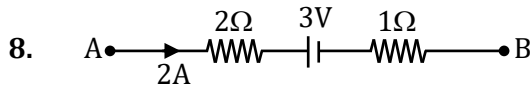

$$V_B = V_A - (2 \times 2) - 3 - (2 \times 1)$$

$$\Rightarrow V_A - V_B = 9V$$

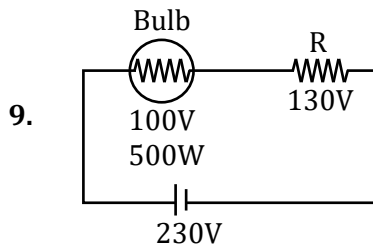

$$\text{Current through bulb} = \frac{P}{V} = \frac{500W}{100V} = 5A$$

$$\text{Therefore } R = \frac{130V}{5A} = 26\Omega$$

10. $R = \frac{\rho \ell}{A} = \frac{\rho \ell^2}{\text{volume}} \Rightarrow R \propto \ell^2$

$$\Rightarrow R_2 = n^2 R_1$$

11. $I = \frac{E}{nR + R} \quad \dots (1)$

$$10I = \frac{E}{\frac{R}{n} + R} = \frac{nE}{R + nR} \quad \dots (2)$$

From (1) & (2),


$$n \frac{E}{R + nR} = 10 \left(\frac{E}{nR + R} \right) \Rightarrow n = 10$$

12. $I = \frac{nE}{nr} = \frac{E}{r} = \text{constant}$

13. $\frac{\theta}{i} = \frac{50}{10^{-3}} = 5000, \frac{\theta}{V} = 20$

$$\frac{\theta/i}{\theta/V} = \frac{5000}{10} = 250 \Rightarrow \frac{V}{i} = R = 250\Omega$$

14.

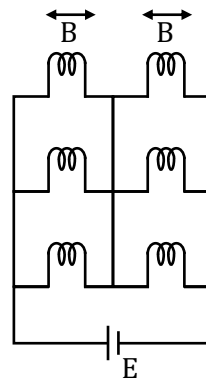


Case-I

$$R_{eq1} = 2R/3$$

$$P_{eq1} = \frac{E^2}{2R/3} = \frac{3P}{2}$$

$$\therefore P_{eq1} : P_{eq2} = 9:4$$

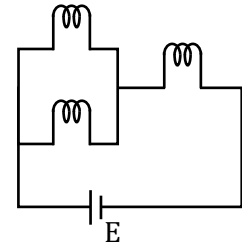


Case-II


$$R_{eq2} = R/2 + R = \frac{3R}{2}$$

$$P_{eq2} = \frac{E^2}{3R/2} = \frac{2P}{3}$$

15. Fuse is used for protection.

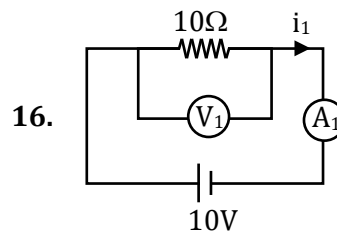

Circuit 1

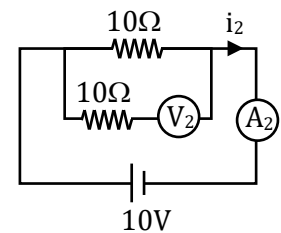

Circuit 2


10Ω is in series with ideal voltmeter. Therefore it will not affect the circuit (Circuit-2)

$$i_1 = \frac{10}{10} = 1A$$

$$V_1 = 10V$$

$$i_2 = \frac{10}{10} = 1A$$

$$V_2 = 10V$$

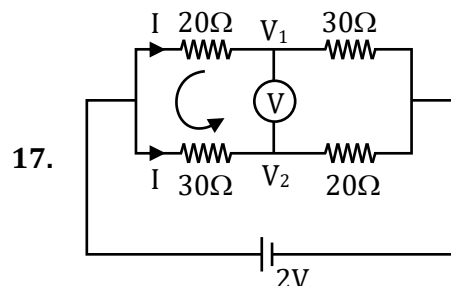


$$(V_1 - V_2) = \frac{30}{25} - \frac{20}{25} = \frac{10}{25} = \frac{2}{5} = 0.4V$$

18. Interchanging cell and galvanometer do not effect balance condition.

19. $\mu = \frac{v_d}{E} = \frac{7.5 \times 10^{-4}}{3 \times 10^{-10}} = 2.5 \times 10^6 \text{ m}^2/\text{V-s}$

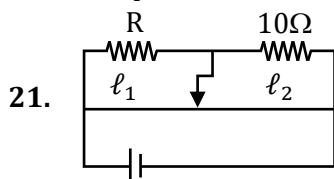20. For some metals like copper, resistivity is nearly proportional to temperature although a non linear region always exists at very low temperature.



$$\frac{R}{10} = \frac{l_1}{l_2} \Rightarrow \frac{R}{10} = \frac{3}{2} \Rightarrow R = 15\Omega$$

Length of 15Ω resistance wire is 1.5 m


$$\therefore \text{length of } 1\Omega \text{ resistance wire} = \frac{1.5}{15} = 0.1 \text{ m}$$

22. $I = \frac{2+4}{4+1+1} = \frac{6V}{6\Omega} = 1 \text{ A}$

23. By KVL

$$-I_2 R_2 - E_2 + E_3 + I_3 R_1 = 0$$

$$I_2 R_2 + E_2 - E_3 - I_3 R_1 = 0$$

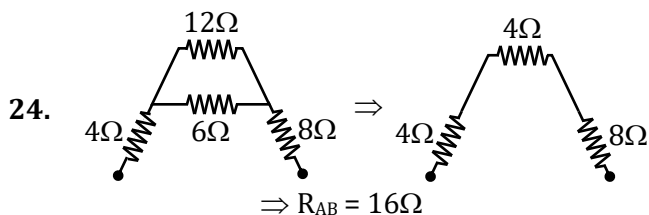

25. Resistance of conductor, $R = \frac{\rho \ell}{A} \Rightarrow A = \frac{\rho \ell}{R}$

$$\Rightarrow \frac{A_1}{A_2} = \frac{\rho_1}{\rho_2} \times \frac{\ell_1}{\ell_2} \times \left(\frac{R_2}{R_1} \right) = 1$$

[$\because R_1 = R_2, \ell_1 = \ell_2$ and for same material $\rho_1 = \rho_2$]

26. (A) $v_d = \left(\frac{eE}{m} \right) \tau$

(B) $J = \sigma E = E/\rho \Rightarrow \rho = E/J$

(C) $\rho = \frac{E}{nev_d}$

$$v_d = \frac{E}{nep}$$

$$\frac{eE}{m} \tau = \frac{E}{nep}$$


$$\tau = \frac{m}{ne^2 \rho}$$

(D) $I = neAv_d$

$$\frac{i}{A} = nev_d$$

$$J = nev_d$$

27. $R_1 = \frac{R}{4} = 0.25\Omega$

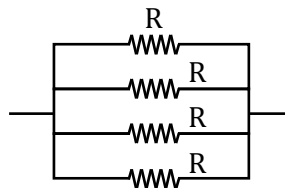

$$R = 1\Omega$$

$$R_{\text{series}} = 4R = 4(1) = 4\Omega$$

28. $V = ir$


$$i = \frac{V}{r}$$

$$i \propto \frac{1}{r} \quad [V \text{ is same for } r_2 \text{ \& } r_3]$$

$$\frac{i_2}{i_3} = \frac{r_3}{r_2}$$

$$i_3 = \frac{r_2}{r_2 + r_3} i_1$$
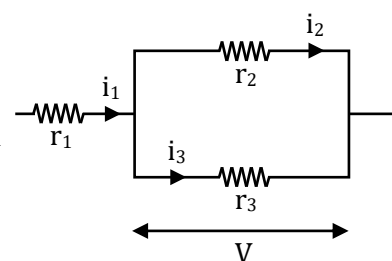
$$\frac{i_3}{i_1} = \frac{r_2}{r_2 + r_3}$$




29. $V = \frac{1}{4\pi\epsilon_0} \cdot \frac{Q}{R}$

$$\frac{1}{4\pi\epsilon_0} = \text{constant}$$

$Q = \text{same (Given)}$

$$\therefore V \propto \frac{1}{R}$$

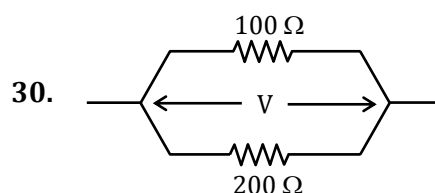$\therefore$ Potential is more on smaller sphere.



As both resistors are in parallel combination so potential drop (V) across both are same.

$$P = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{R}$$

$$\frac{P_1}{P_2} = \frac{R_2}{R_1} = \frac{200}{100} = \frac{2}{1} = 2 : 1$$

31. For conductors α is (+)ve

For semiconductors & Insulators α is (-)ve

32. Radius of wire $= \frac{10^{-2}}{\sqrt{\pi}}$

Cross sectional area $A = \pi r^2 = 10^{-4} \text{ m}^2$

$$j = \frac{i}{A} = \left(\frac{V}{R} \right) \cdot \frac{1}{A} = \frac{E\ell}{RA} \quad R = \frac{\rho\ell}{A}$$


$$j = \frac{10 \times 10}{10 \times 10^{-4}} = 10^5 \text{ A/m}^2$$

or

$$J = \sigma E \Rightarrow \frac{E}{\rho} = \frac{E\ell}{RA} = \frac{10 \times 10 \times \pi}{10 \times 10^{-4} \times \pi}$$

$$\Rightarrow 10^5 \text{ A/m}^2$$

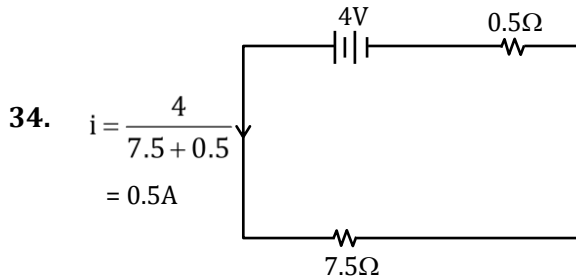33. Resistance of P & Q should be approx. equal as it decreases error in experiment.




$$\text{TPD} = 4 - 0.5 \times 0.5$$

$$= 4 - 0.25$$

$$\text{TPD} = 3.75 \text{ volt}$$

35. If effective resistance is x ,

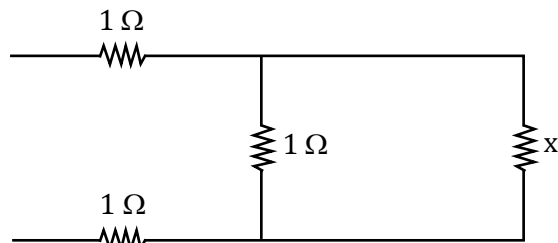

$$\Rightarrow x = 1 + \frac{x \times 1}{x + 1} + 1$$

$$\Rightarrow (x - 2) = \frac{x}{x + 1}$$

$$\Rightarrow x^2 - x - 2 = x$$



$$\Rightarrow x^2 - 2x - 2 = 0$$

$$\text{So, } x = \frac{2 \pm \sqrt{12}}{2} = 1 \pm \sqrt{3} \Omega$$

$$\text{neglecting negative value, } x = 1 + \sqrt{3} \Omega$$

36. Conductance $= \frac{1}{\text{Resistance}}$

37.

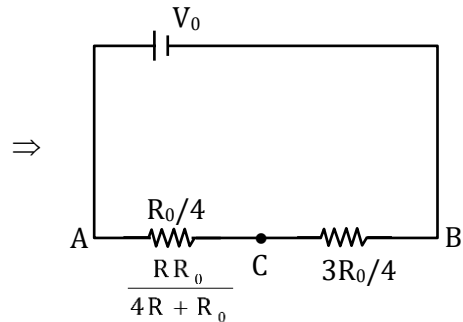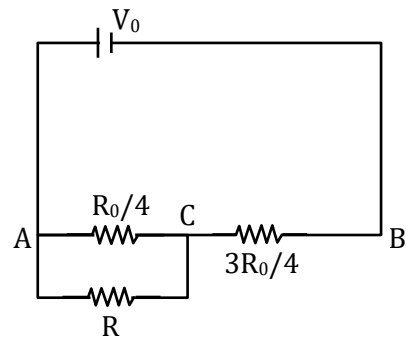


In series, potential divides in direct ratio of resistance,

$$\text{So, } V_{AC} = \frac{R_{AC}}{R_{AC} + R_{CB}} V_0$$

$$= \frac{\frac{RR_0}{4R + R_0}}{\frac{RR_0}{4R + R_0} + \frac{3R_0}{4}} \times V_0 = \frac{4RV_0}{16R + 3R_0}$$

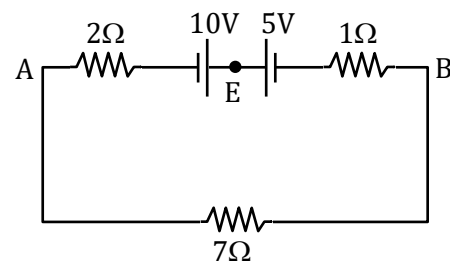
38. $i = \frac{10 - 5}{10} = \frac{5}{10} \text{ A}$



$$= 0.5 \text{ A}$$

from A to B through E.

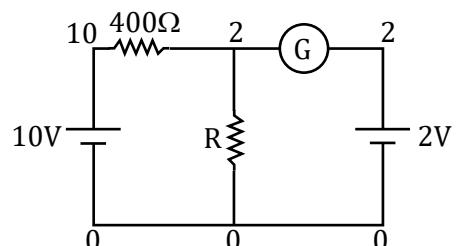39. For no reading galvanometer. Potential across it is same.



$$i_{400\Omega} \Rightarrow \frac{10-2}{400} = \frac{8}{400} = \frac{1}{50} = i_R$$

$$i_R \Rightarrow \frac{V_R}{R} \Rightarrow \frac{2}{R} = \frac{1}{50} \Rightarrow R = 100\Omega$$

$$40. R_T = R_0 [1 + \alpha(T - T_0)]$$

$$6.8 = 2[1 + \alpha(80 - \alpha)]$$

$$\alpha = \frac{2.4}{80} = 0.03/^\circ\text{C} = 3 \times 10^{-2}/^\circ\text{C}$$

$$41. I_s = \frac{E}{10R} \quad \dots (1)$$

$$I_p = \frac{E}{R/10} = \frac{10E}{R} \quad \dots (2)$$

$$n = \frac{I_p}{I_s} = 100 \Rightarrow n = 100$$

$$42. R = \frac{\rho L}{A} \text{ If diameter becomes thrice then cross}$$

Section area will become 9 times so

$$R \propto \frac{1}{A} \text{ Resistance will become } \frac{1}{9} \text{ times}$$


$$R' = \frac{81\Omega}{9} = 9\Omega$$

$$43. I = neAv_d$$

$$V_d = \frac{I}{neA} = \frac{10}{10^{22} \times 1.6 \times 10^{-19} \times \pi \times 10^{-6}}$$

$$V_d = \frac{6.25}{\pi} \times 10^3 \text{ ms}^{-1}$$

44.

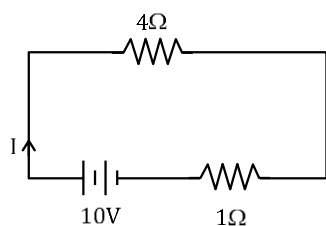

$$I = \frac{E}{R+r} = \frac{10}{4+1} = 2\text{A}$$

$$V_T = E - Ir$$


$$= 10 - 2(1)$$

$$= 8\text{V}$$

$$45. \text{ Wire resistance} = 100\Omega$$

Divided into 10 equal parts

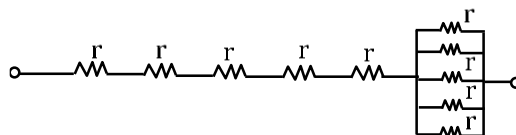
$$\text{so each part resistance } r = \frac{100}{10} = 10\Omega$$



$$\text{Req.} = 5(10) + \frac{10}{5}$$

$$= 52\Omega$$

46.

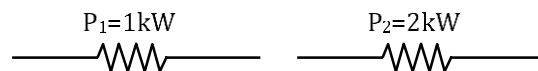

$$\text{In series } P_s = \frac{P_1 P_2}{P_1 + P_2} = \frac{1 \times 2}{1 + 2} = \frac{2}{3} \text{ kW}$$

$$\text{In parallel } P_p = P_1 + P_2 = 1 + 2 = 3 \text{ kW}$$

$$\Rightarrow \frac{P_s}{P_p} = \frac{\frac{2}{3}}{3} = \frac{2}{9}$$

$$47. \text{ Using } i = neAv_d$$

$$100 \times 10^{-3} = n \times \pi \left(\frac{d}{2} \right)^2 v' \quad \dots (1)$$

$$200 \times 10^{-3} = n \times \pi \left[\frac{d/2}{2} \right]^2 \times e \times v' \quad \dots (2)$$


On Solving ; $v' = 8v$

$$48. \ell \rightarrow 10\Omega$$

$$\therefore R \propto \ell^2$$


$$\therefore \text{ for } 2\ell \text{ length } R = 40\Omega$$

Now

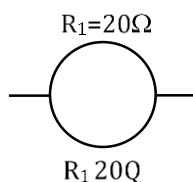

$$R_{\text{eff}} = \frac{R_1}{2} = 10\Omega$$

49.

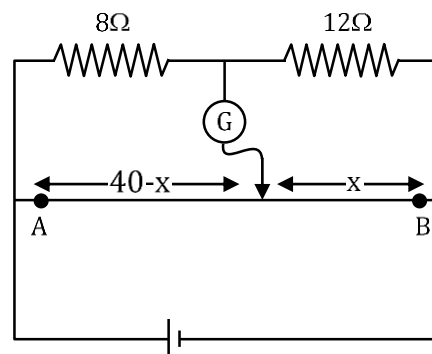

$$8(x) = 12(40 - x)$$

$$2x = 120 - 3x \Rightarrow 5x = 120 \Rightarrow x = 24 \text{ cm}$$


Exercise-III (Analytical Questions)

- 1.
- $\therefore V_1$
- and
- V_2
- are in series

$$\therefore V \propto R$$

$$\therefore V_1 \neq V_2 \text{ (as } R_1 \neq R_2 \text{)}$$
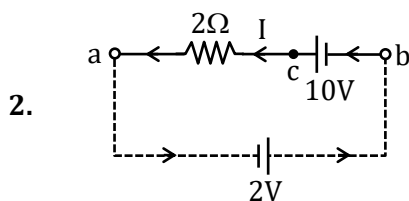
$$V_1 + V_2 = V_3 \text{ (as } V \text{ is same in parallel)}$$



$$I = \frac{12}{2} = 6A$$

Apply KVL from a to c

$$V_a + 6 \times 2 = V_c$$

$$V_a - V_c = -12 \text{ Volt}$$

- 3.
- $E = 10V, I_{\max} = \frac{E}{r} = 2 \text{ Amp.}$


$$r = \frac{E}{2} \Rightarrow r = \frac{10}{2} = 5\Omega$$

- 4.
- $\frac{V^2}{R} t = \text{constant}$

$$\therefore t \propto R$$

$$\text{In series } t_s = t_1 + t_2$$
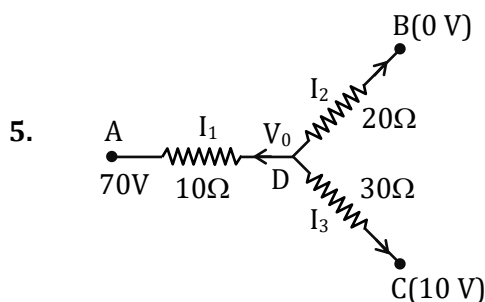
$$\text{In parallel } t_p = \frac{t_1 t_2}{t_1 + t_2}$$



$$I_1 + I_2 + I_3 = 0$$


$$\frac{V_0 - 70}{10} + \frac{V_0 - 0}{20} + \frac{V_0 - 10}{30} = 0$$

$$\Rightarrow V_0 = 40 \text{ volt}$$

$$I_1 = 3A$$

$$I_2 = 2A$$

$$I_3 = 1A$$

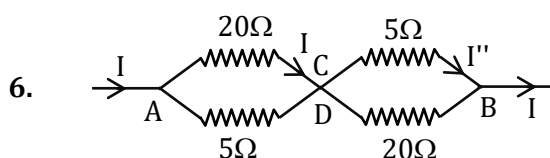


$$I' = \frac{5}{25} I = \frac{I}{5}$$

$$R_{eq} = 4 + 4 = 8\Omega$$

$$I'' = \frac{20}{25} I = \frac{4I}{5}$$

$$\text{Also } = V_C = V_D$$
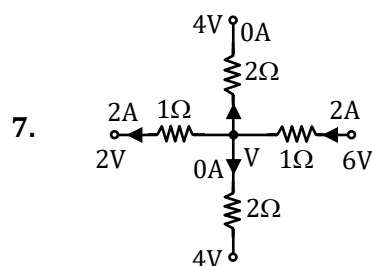
$$\text{Current in DC} = \frac{4I}{5} - \frac{I}{5} = 3I/5$$



$$\frac{V-2}{1} + \frac{V-6}{1} + \frac{V-4}{2} + \frac{V-4}{2} = 0$$

$$2V - 4 + 2V - 12 + V - 4 + V - 4 = 0$$


$$6V = 24$$

$$V = 4$$

$$2A, -2A, 0A, 0A$$

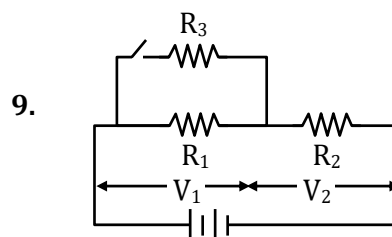- 8.
- $i = \text{constant}$

$$\text{as area } \uparrow \Rightarrow R/\ell \downarrow \text{ \& } E \downarrow \Rightarrow \frac{V}{L} \downarrow \text{ \& } J = \frac{i}{A} \downarrow$$




After closing the switch $V_1 \downarrow$ and $V_2 \uparrow$
 $\Rightarrow i$ through $R_1 \downarrow$ and i through $R_2 \uparrow$.

- 10.
- $V = \frac{\text{Work}}{q} = \frac{[ML^2T^{-2}]}{[AT]} = [ML^2T^{-3}A^{-1}]$

$$R = \frac{V}{i} = [ML^2T^{-3}A^{-2}]$$

$$\rho = \frac{RA}{\ell} = [ML^3T^{-3}A^{-2}]$$
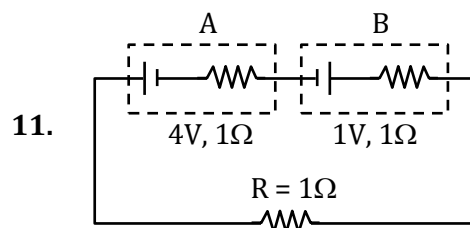
$$\sigma = \frac{1}{\rho} = [M^{-1}L^{-3}T^3A^2]$$



$$i = \frac{4-1}{1+1+1} = 1A$$

Now TPD of A = $4 - 1 \times 1 = 3V$

TPD of B = $1 + 1 \times 1 = 2V$

Power consumed by R = $1^2 \times 1 = 1W$

P.D. of R = $1 \times 1 = 1V$

12. Increase in temperature causes atoms to vibrate more, which increases the number of collisions electrons suffer and decrease the drift velocity.

OR $\vec{v}_d = \mu E = \left(\frac{e\tau}{m}\right)\vec{E} \quad \& \quad \sigma = \frac{ne^2\tau}{m}$

$$v_d \propto \tau, \sigma \propto \tau \text{ (temp. } \uparrow; \tau \downarrow)$$

13. $S(i - i_0) = i_0 G$

$$\Rightarrow i = i_0 \left(1 + \frac{G}{S}\right)$$

$\therefore$ As $S \uparrow$ $i \downarrow$

$\therefore$ Value of shunt is more in mili ammeter.

$$R_{\text{net}} = \frac{GS}{S+G} = \frac{G}{1+\frac{G}{S}}$$

$\therefore S \uparrow \Rightarrow R_{\text{net}} \uparrow$

$$\Rightarrow R_{\text{mili ammeter}} > R_{\text{ammeter}}$$

14. A current carrying wire is not charged.

15. In balanced condition, current through galvanometer is zero and does not affect main current.

16. For rating, $P = \frac{V^2}{R} \therefore P \uparrow \Rightarrow R \downarrow$

17. * For maximum power $R = r$

* $P = I^2 R \propto I^2$ (if $R = \text{constant}$)

18. At higher currents, joule's heating will be larger, increasing the temperature sharply. Since,

$R = R_0 (1 + \alpha \Delta T)$, resistance varies and $V \propto I$ doesn't hold anymore.


19. For meter bridge experiment, unknown resistance $S = \frac{100-\ell}{\ell} R$

20. $\Delta KE = q(\Delta V)$

21. As i changes (in same resistor); n remain constant

by $i = JA$; J become double

by $i = nAeV_d$; V_d become double

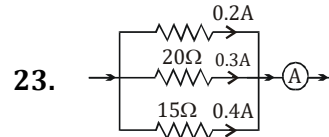

$$0.2R_1 = 20 \times 0.3 = 15 \times 0.4$$

26. For (A) :

$$\vec{E} = -\frac{\partial V}{\partial x} \hat{i} - \frac{\partial V}{\partial y} \hat{j} - \frac{\partial V}{\partial z} \hat{k} = \frac{1}{x^2} \hat{i} + \frac{1}{y^2} \hat{j} + \frac{1}{z^2} \hat{k}$$


$$\Rightarrow |\vec{E}| = |\hat{i} + \hat{j} + \hat{k}| = \sqrt{3} \text{ N/C}$$

For (B) :

$$I = \frac{dQ}{dt} = 4 - 4t, \text{ current will be zero at } t = 1s$$

Total heat produced
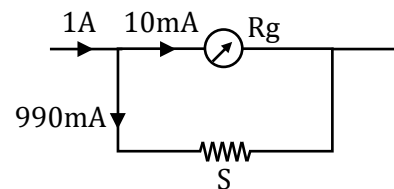
$$\int_0^1 I^2 R dt = \int_0^1 (4 - 4t)^2 (6) dt = (16 \times 6) \left[\frac{(1-t)^2}{-3} \right]_0^1 = 32J$$



For(C) $(10 \text{ mA}) (R_g) = (990 \text{ mA}) (s)$

$$\Rightarrow s = \frac{0.99}{99} = 0.01\Omega$$

For(D) $U = -\vec{p} \cdot \vec{E}$ Here $\vec{p} = \pm qd \hat{i}$

$$|\vec{P}| = (10 \times 10^{-3}) (8 \times 10^{-2}) = \pm (8 \times 10^{-4}) \hat{i} \text{ C-m}$$

$$U = -pE \cos \theta$$

$$U = (8 \times 10^{-4}) (500)$$

$$U = 0.4 \text{ J}$$