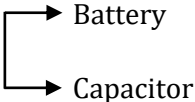
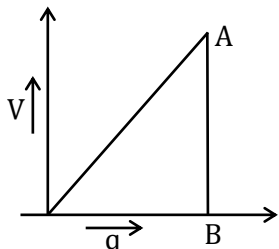


Capacitor


SOLUTIONS

Exercise-I (Conceptual Questions)

1. $C \rightarrow$ Depends material & dimensions only
2. $Q = CV$
 $C \rightarrow$ does not depend on Q and V
 $Q \uparrow \quad \quad \quad V \uparrow$
3. Charge on capacitor = Charge of positive plate or negative plate. Net charge on capacitor = 0
4. $C = 4\pi\epsilon_0 R$ and $V = \frac{4}{3}\pi R^3$
 $A = 4\pi R^2$
 $R = \left(\frac{3V}{A}\right)$
 $\therefore C = 12\pi\epsilon_0 \left(\frac{V}{A}\right)$
5. Current
6. Energy Source 
7. $C = 4\pi\epsilon_0 R\epsilon_r$ $\left[\because 2\pi R = 2 \Rightarrow R = \frac{1}{\pi} \right]$
 $C = \frac{4\pi\epsilon_0\epsilon_r}{\pi}$
 $C \approx 2800 \text{ pF}$
8. Energy supplied by the battery is
 $U = CV^2 = Q^2/C = QV$
 $= (10^{-6})(300)$
 $= 3 \times 10^{-4} \text{ J}$
9. It does not depend on the resistance
 $\frac{1}{2}CV^2 = \frac{1}{2} \times 2 \times 10^{-4} \times (200)^2 = 4 \text{ J}$
10. $V = \frac{Q}{C}$
11. 
Area = $\frac{1}{2} qV$ = Energy stored in capacitor.

12. 

$$\text{Work} = CV^2 \Rightarrow U = \frac{1}{2} CV^2$$

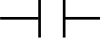13. 


$$C = \frac{\epsilon_0 A}{d}$$

14. $C = \frac{\epsilon_0 A}{d}$

$$Q = CV = \frac{\epsilon_0 AV}{d}$$

$$= \frac{8.85 \times 10^{-12} \times 400 \times 10^{-4} \times 200}{2 \times 10^{-3}}$$

$$= 3.54 \times 10^{-8} \text{ C}$$

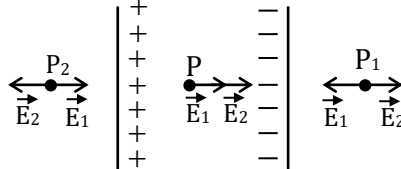15. 

$$\text{at P, } E = \frac{q}{2A\epsilon_0}$$

$$\text{at P}_1 \text{ \& P}_2 \quad E = 0$$

16. $r = 20 \text{ mm}$ for sphere

$$A = \pi r^2 \quad C' = 4\pi\epsilon_0 R$$

$$C = \frac{\epsilon_0 A}{d} \Rightarrow C = C'$$

$$\frac{\epsilon_0 A}{d} = 4\pi\epsilon_0 R \Rightarrow d = \frac{\epsilon_0 r^2}{4\epsilon_0 R} = 1 \times 10^{-4} \text{ m}$$

$$= 0.1 \text{ mm}$$

17. Use $U = \frac{1}{2} \epsilon_0 E^2$

18. Q-same

$$U' \propto \frac{1}{C} \quad C' = KC$$

$$U' = \frac{CU_0}{C'} = \frac{U_0}{K}$$

19. Q remains same.

$$U = \frac{Q^2}{2C}$$

$$\therefore C' = KC = 6C$$

$$\& U' = \frac{U}{K} = \frac{U}{6}$$

$$20. \quad C = \frac{\epsilon_0 A}{d - t + \frac{t}{K}}$$

21. $Q = CV$;
when a slab of dielectric medium is placed
capacitance is increased

$Q \propto C$ so charge is also increased

22. Charge does not change. It remains constant.

$$23. \quad U = \frac{1}{2} CV^2$$

$\therefore$ when a dielectric is inserted then $C \uparrow$ so $U \uparrow$

$$24. \quad U = \frac{Q^2}{2C} \therefore C \uparrow \therefore U \downarrow$$

$$25. \quad U = \frac{Q^2}{2C}$$

$$\therefore C = \frac{\epsilon_0 A}{d}$$

If $d \downarrow$ $C \uparrow$ $U \downarrow$

$$26. \quad E = \frac{V}{d}$$

$\therefore d \uparrow$ $E \downarrow$

$$\therefore Q = CV \text{ and } C = \frac{\epsilon_0 A}{d}$$

$\therefore d \uparrow$ $C \downarrow$ $Q \downarrow$

27. Battery $\rightarrow$ removed

$Q \rightarrow$ constant

$$V = \frac{Q}{C} \text{ if } d \uparrow C \downarrow V \uparrow$$

28. No

$$29. \quad C = \frac{\epsilon_0 A}{d}; C_1 = \frac{\epsilon_0 A}{2d} = \frac{C}{2}$$

$$C_2 = \frac{5\epsilon_0 A}{2d} = \frac{5}{2} C$$

$$C_{eq} = C_1 + C_2 = 3C$$

$$\frac{\Delta C}{C} \% = \frac{2C}{C} \times 100 = 200\%$$

$$30. \quad C_{AB} = \frac{2}{3} + 2 = \frac{8}{3} \mu F$$


$$31. \quad V_2 = V_3$$

$$Q_1 = Q_2 + Q_3$$

$$V = V_1 + V_2$$

$$32. \quad C = 1 \mu F, \quad C' = 3 \mu F$$

$$V = 500 V, \quad V' = 2000 V$$

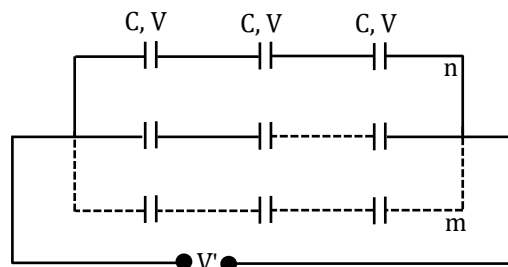

Suppose m rows of given capacitors are connected in parallel and each row now contains n capacitors then potential difference across each capacitor $V = \frac{V'}{n}$ and equivalent

$$\text{capacitance of network } C' = \frac{mC}{n}$$

on putting values,

$$\Rightarrow V = \frac{V'}{n} \Rightarrow 500 = \frac{2000}{n}$$

$$n = 4 \Rightarrow C' = \frac{mC}{n}$$

$$3 = \frac{m \times 1}{4} \Rightarrow m = 12$$

$\therefore$ total capacitors = $m \times n = 48$

33. Given circuit is balanced wheat stone bridge. Hence effective capacity is $6 \mu F$.

$$34. \quad \frac{V_1}{V_2} = \frac{C_2}{C_1} = \frac{10}{1}$$

$$V_1 = \frac{500}{11} \times 10 = \frac{5000}{11} \text{ volt}$$

35. C and C are in parallel and in series with $2C$. Therefore resultant of these three will be


$$= \frac{(C+C) \times 2C}{C+C+2C} = C$$

This equivalent system is in parallel with C .

It's equivalent capacitance = $C + C = 2C$


Now, $2C$ and $2C$ are in series and in parallel with $2C$.

$$\text{So, } C_{net} = C + 2C = 3C$$

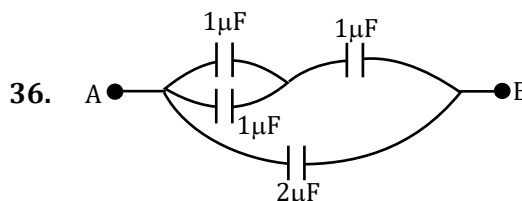

$$\text{Redraw the circuit } C_{AB} = \frac{8}{3} \mu F$$

37. Identify Wheatstone bridge (WSB)

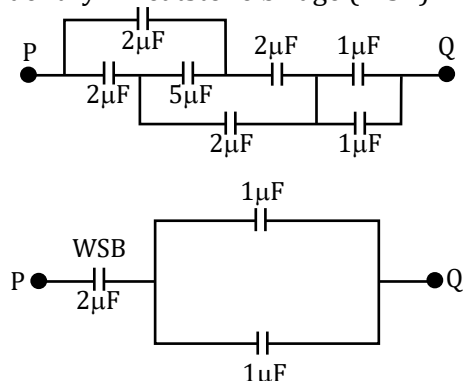

$$C_{PQ} = 1 \mu F$$

38. Let Initial charge = q
then from charge conservation


$$Q_1 + Q_2 = Q'_1 + Q'_2$$

$$q + q = C_1 V + C_2 V = V[C_1 + C_2]$$

$$V = \frac{2q}{C_1 + C_2} = \frac{2q}{4\pi\epsilon_0(R_1 + R_2)} = \frac{2kq}{(R_1 + R_2)}$$

$$\Rightarrow q = \frac{V(R_1 + R_2)}{2k}$$

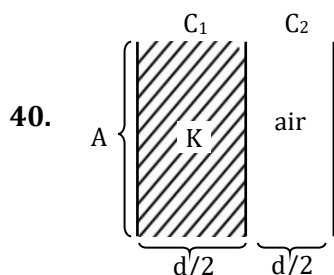39. As the potential of two spheres is same hence there will be no flow of charge.



$$C = \frac{\epsilon_0 A}{d} \Rightarrow C_1 = \frac{\epsilon_0 KA}{d/2} = \frac{2\epsilon_0 KA}{d}$$

$$C_2 = \frac{\epsilon_0 A}{d/2} = 2\left(\frac{\epsilon_0 A}{d}\right)$$

C_1 & C_2 are in series combination

$$\text{Hence } \frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{d}{2\epsilon_0 A} \left(\frac{1}{K} + \frac{1}{1} \right)$$

$$\frac{1}{C_s} = \frac{d}{2\epsilon_0 A} \left(\frac{K+1}{K} \right)$$

$$C_s = \frac{2\epsilon_0 A}{d} \left(\frac{K}{K+1} \right) \Rightarrow C_s = \frac{2CK}{K+1}$$

41. Q same $\rightarrow Q = C_1 V_{AD} = C_1 (V_1 - V_D)$

$$\text{and } Q = C_2 V_{DB} = C_2 (V_D - V_2)$$

$$C_1 (V_1 - V_D) = C_2 (V_D - V_2)$$

$$C_1 V_1 + C_2 V_2 = (C_1 + C_2) V_D$$

$$V_D = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

42. Since both capacitors are in series so charge on each capacitor will be same.

Applying KVL from A to B :-

$$V_A - V_B = \frac{Q}{C_1} - E + \frac{Q}{C_2}$$


$$\text{or } V_A - V_B + E = Q \left[\frac{1}{C_1} + \frac{1}{C_2} \right]$$

$$5 + 10 = Q \left[\frac{3}{2} \times 10^6 \right]$$

$$Q = \frac{30}{3} = 10 \mu C$$

$$V_1 = \frac{Q}{C_1} = \frac{10 \times 10^{-6}}{1 \times 10^{-6}} = 10 V$$

43. Redraw circuit

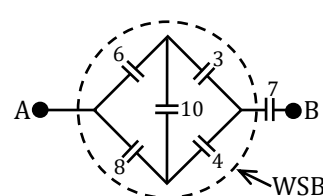

C_{net} of W.S.B.

$$= \frac{6 \times 3}{6 + 3} + \frac{8 \times 4}{8 + 4}$$

$$= 2 + \frac{32}{12} = \frac{14}{3}$$


This is in series with 7

$$\text{So, } C_{\text{eq.}} = \frac{\frac{14}{3} \times 7}{\frac{14}{3} + 7} = \frac{14}{5}$$

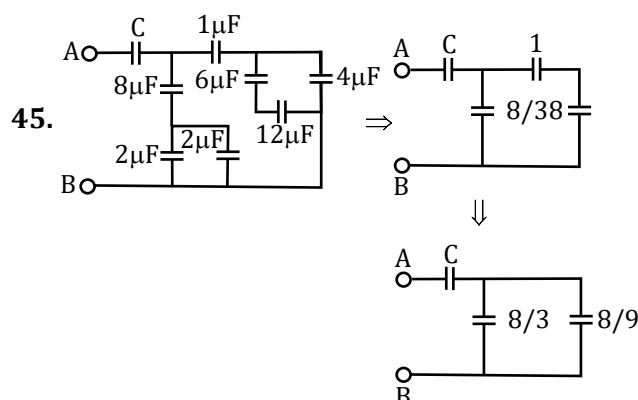44. C_{net} of C_1 and C_2 , $C_{\text{net}} = \frac{C_1 C_2}{C_1 + C_2}$ $\{C_1 < C_2\}$

So, C_{net} will be smaller than C_1

$$C_{\text{net}} < C_1 < C_2 \text{ so } \frac{C_1}{2} < C < C_1$$



$$C_{AB} = \frac{C \times \frac{32}{9}}{C + \frac{32}{9}} = 1 \Rightarrow C = \frac{32}{23} \mu F$$

46. When capacitor is fully charged. There will be no flow of current through capacitor.

$$\text{So, } I = \frac{2.5}{2+0.5} = 1 \text{ A}$$


P.D. across upper branch = $2\Omega \times 1\text{A} = 2\text{V}$

and same voltage on lower branch


$$V_C + V_{2\Omega} = 2\text{V}$$

{but voltage on $2\Omega = 0$ as no current}
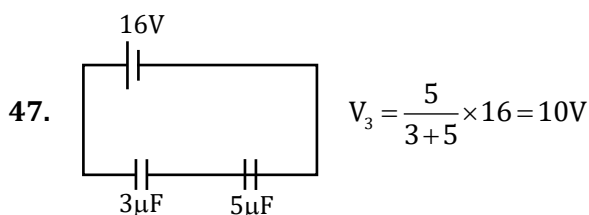
$$V_C = 2\text{V, So } Q = 2\text{V} \times 5\mu\text{F} = 10\mu\text{C}$$



48. Given circuit can be reduced as

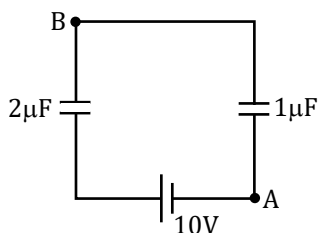

$$\text{Charge on capacitors} = \left(\frac{2}{3}\right)(10)\mu\text{C}$$

$$\text{Now } V_B - V_A = \left(\frac{20}{3}\right)(1) = \frac{20}{3}$$

$$\Rightarrow V_B = V_A + \frac{20}{3} = 10 + \frac{20}{3} = \frac{50}{3} \text{ V}$$

49. C_2 & C_3 are in parallel so $V_2 = V_3$


Let $C_1 = C$

$$C_2 = C_3 = \frac{C_1}{2} = \frac{C}{2}$$

$$\text{Equivalent of } C_2 \text{ \& } C_3 = \frac{C}{2} + \frac{C}{2} = C$$

So $V_1 = V_2 = V_3$

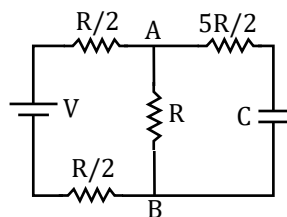50. In steady state $V_C = V_{AB} = \text{capacitor voltage} = V/2$



51. At $t \rightarrow \infty$ $V_{AB} = \frac{V}{2}$, $i_{AB} = \frac{V}{2R}$


52. Bulb light up during charging

53. $C = \frac{\epsilon_0 A}{d} = 10\mu\text{F}$

$$C_1 = \frac{k_1 \epsilon_0 A}{2d} = 10\mu\text{F}$$

$$C_2 = \frac{k_2 \epsilon_0 A}{2d} = 20\mu\text{F}$$

$$C_{eq} = C_1 + C_2 = 30\mu\text{F}$$

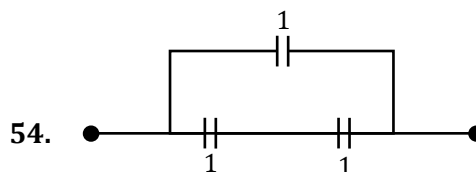


$$C_{net} = 1.5\mu\text{F}$$

55. Whenever there is transfer of charge some energy dissipates in the form of heat hence potential energy of system decreases.

If $V_1 \neq V_2$ then charge transfer takes place

$$\Rightarrow \frac{kQ_1}{R_1} \neq \frac{kQ_2}{R_2}$$

$$Q_1 R_2 \neq Q_2 R_1$$

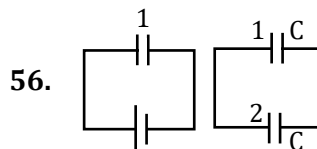

$$\text{energy stored (U)} = \frac{q^2}{2C}$$

After connecting with another capacitor

$$V_{\text{Common}} = \frac{q_1 + q_2}{C_1 + C_2} = \frac{q + 0}{C + C} = \frac{q}{2C}$$

$\therefore$ Energy on each capacitor

$$= \frac{1}{2} C V_{\text{Common}}^2 = \frac{1}{2} C \left(\frac{q}{2C} \right)^2 = \frac{1}{2} \frac{q^2}{4C} = \frac{U}{4}$$

57. $\frac{1}{C_{eq}} = \frac{1}{3} + \frac{1}{10} + \frac{1}{15}$

$$C_{eq} = 2\mu\text{F}$$


$$Q_{eq} = (2 \times 100) \mu\text{C} = 200\mu\text{C}$$

58. $V_A = \frac{C_B}{C_A + C_B} V_T = 6\text{V} \Rightarrow V_B = (10 - 6)\text{V} = 4\text{V}$

$$\Rightarrow \frac{V_A}{V_B} = \frac{3}{2}$$

$$59. U_s = \frac{1}{2} kx^2 = 500 \text{ J} \quad \left[k = \frac{F}{x} \right]$$
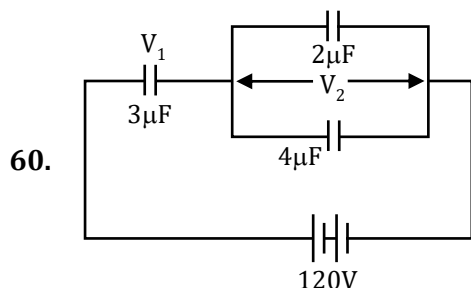
$$U_c = \frac{1}{2} CV^2 = 500 \text{ J} \Rightarrow \frac{U_s}{U_c} = \frac{1}{1}$$




$$C_{eq} = \frac{6 \times 3}{6 + 3} = 2 \mu F$$

$$\therefore Q = 120 \times 2 \mu C = 240 \mu C$$

$$V_1 = \frac{240}{3} = 80 \text{ V}$$

$$V_2 = 40 \text{ V} \Rightarrow Q_2 = 40 \times 2 = 80 \text{ C}$$

$$Q_3 = 40 \times 4 = 160 \text{ C}$$

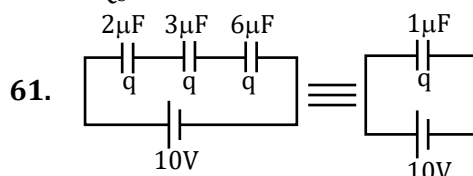

$$\frac{1}{C} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6} = \frac{6}{6} \Rightarrow C = 1 \mu C$$

$$\Rightarrow q = 10^{-6} \times 10 = 10 \mu C$$

62. After connecting V become same

$$\frac{E_a}{E_b} = \frac{b}{a}$$

$$63. C = \frac{4\pi\epsilon_0 R_1 R_2}{R_2 - R_1}$$

$$64. C = \frac{4\pi\epsilon_0 b^2}{b - a}$$

$$65. \tau = RC$$

$$66. \text{Energy density} = \frac{1}{2} \epsilon_0 \frac{V^2}{d^2}$$

$$67. V_{common} = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \{ \because V_2 = 0 \}$$

$$\Rightarrow V_{common} = \frac{C_1 V}{C_1 + C_2}$$

68. Potential same at both spheres $V_1 = V_2$

$$\therefore \frac{kQ_1}{R_1} = \frac{kQ_2}{R_2} \Rightarrow \frac{Q_1}{R_1} = \frac{Q_2}{R_2}$$

surface charge density

$$\begin{aligned} \therefore \frac{\sigma_1}{\sigma_2} &= \frac{Q_1}{4\pi R_1^2} \times \frac{4\pi R_2^2}{Q_2} \\ &= \frac{Q_1}{Q_2} \times \left(\frac{R_2}{R_1} \right)^2 = \left(\frac{R_1}{R_2} \right) \left(\frac{R_2}{R_1} \right)^2 \\ &= \frac{R_2}{R_1} = \frac{20}{10} = \frac{2}{1} \end{aligned}$$

69. $C_{eq} = 4 \mu F$ (Wheat stone bridge)

70. By charge conservation

$$V_{com} = \frac{6 \times 12 - 3 \times 12}{9} = 4 \text{ Volt}$$

$$\begin{aligned} 71. V_{com} &= \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} \\ &= \frac{0.2 \times 600 + 1 \times 0}{0.2 + 1} \\ &= 100 \text{ volt} \end{aligned}$$

$$72. U = \frac{q^2}{2C} = \frac{q^2 d}{2\epsilon_0 A}$$

$$\text{Volume} = Ad$$


$$\text{Energy Density} = \frac{U}{\text{Volume}} = \frac{q^2}{2\epsilon_0 A^2}$$

$$73. W = \frac{1}{2} CV_2^2 - \frac{1}{2} CV_1^2 = \frac{1}{2} C(900 - 225)$$

$$C = \frac{2}{675} W$$

Now in 2nd case
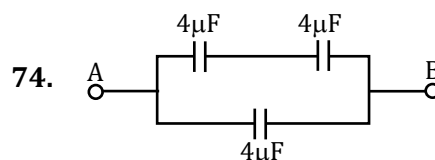
$$\begin{aligned} \frac{1}{2} C [(60)^2 - (30)^2] &= \frac{1}{2} C [3600 - 900] \\ &= \frac{1}{2} \cdot \frac{2}{675} W [2700] = 4W \end{aligned}$$



$$C_{AB} = (2 + 4) \mu F = 6 \mu F$$

$$75. \frac{Q_1}{Q_2} = \frac{C_1 V}{C_2 V} = \frac{C_1 V}{KC_1 V} \quad (\because V = \text{const.})$$

$$\Rightarrow K = \frac{Q_2}{Q_1} = \frac{100}{40} = 2.5$$

$$76. C_{net} = \frac{C}{2}, V_{net} = 2V$$

77. $C_{eq} = 2\mu F$
 $Q_{eq} = 4\mu C$
 Q on $1\mu F = 2\mu C$
 Q on $2\mu F$ each $= 2\mu C$
78. E remain same because $V = \text{constant}$
79. $P = \frac{W}{t} = \frac{\frac{1}{2}CV^2}{t} = \frac{\frac{1}{2} \times 40 \times 10^{-6} \times (3000)^2}{2 \times 10^{-3}}$
 $= 9 \times 10^4 = 90 \text{ kW}$
80. $C_S = \frac{C_1 C_2}{C_1 + C_2}$
 $C_P = C_1 + C_2$
81. $V \propto \frac{Q}{R}$ So $Q \propto R$ at constant V
 So $\frac{q_1}{q_2} = \frac{R_1}{R_2}$
82. $V_{com.} = \frac{Q}{C_1 + C_2} = \frac{Q}{4\pi\epsilon_0(R_1 + R_2)}$
 $= \frac{150 \times 10^{-6} \times 9 \times 10^9}{(10 + 20) \times 10^{-2}} = 4.5 \times 10^6 V$
83. $\frac{1}{2}C_1 V_1^2 = \frac{1}{2}C_2 V_2^2$ [Assume no energy lost]
 because total energy is transferred (given).
 $\therefore \frac{1}{2} \times 900 \times 10^{-6} \times 100^2 = \frac{1}{2} \times 100 \times 10^{-6} \times V^2$
 $\therefore V^2 = 90000 \Rightarrow V = 300 \text{ Volt}$

Exercise-II (Previous Year Questions)

1. Electric field, $E \propto \frac{1}{K}$ As $K_1 < K_2$ so $E_1 > E_2$
2. Once the capacitor is charged, its charge will be constant $Q = CV$. When dielectric slab is inserted
 $C'_{New} = KC$
 $E = \frac{Q^2}{2C} \Rightarrow E_{New} = \frac{1}{K} E_{initial}$
 $V = \frac{Q}{C}$ so $V_{new} = \frac{1}{K} V$
3. $F = \frac{Q^2}{2\epsilon_0 A}$
 $\therefore Q = CV$ and $C = \frac{\epsilon_0 A}{d} \Rightarrow \epsilon_0 A = Cd$
 So $F = \frac{C^2 V^2}{2Cd} = \frac{CV^2}{2d}$


4. Initial energy stored in capacitor $2\mu F$
 $U_i = \frac{1}{2} 2(V)^2 = V^2$
 Final voltage after switch 2 is ON
 $V_f = \frac{C_1 V_1}{C_1 + C_2} = \frac{2V}{10} = 0.2 V$
 Final energy in both the capacitors
 $U_f = \frac{1}{2} (C_1 + C_2) V_f^2 = \frac{1}{2} 10 \left(\frac{2V}{10} \right)^2 = 0.2 V^2$
 So energy dissipated $= \frac{V^2 - 0.2V^2}{V^2} \times 100 = 80\%$
5. $U_i = \frac{1}{2} CV^2$
 $U_f = \frac{1}{2} [2C] \left[\frac{V}{2} \right]^2 = \frac{1}{2} U_i$
 Decrease by a factor of 2
6. $F = QE = Q \frac{\sigma}{2\epsilon_0} = \frac{Q^2}{2A\epsilon_0}$
 $\therefore$ Electrostatic force is independent of distance between plates
7. $U_{initial} = \frac{1}{2} CV^2$,
 $\text{Loss} = \frac{C \cdot C}{2(C+C)} (V-0)^2 = \frac{1}{4} CV^2$
 $\% \text{ Loss} = \frac{\frac{1}{4} CV^2}{\frac{1}{2} CV^2} \times 100 = 50\%$
8. (A) $\frac{\sigma}{R}$ (B) $\frac{\sigma}{2R}$
 Total charge $= \sigma \times 4\pi R^2 + \sigma \times 4\pi (2R)^2$
 $= 20 \sigma \pi R^2$
 $\frac{Q_A}{Q_B} = \frac{1}{2}$
 $Q_A = \frac{20}{3} \sigma \pi R^2$ and $Q_B = \frac{40}{3} \sigma \pi R^2$
 $\sigma_A = \frac{Q_A}{\text{area}} = \frac{20 \sigma \pi R^2}{3 \cdot 4\pi R^2} = \frac{5\sigma}{3}$
 $\sigma_B = \frac{40 \sigma \pi R^2}{4\pi (2R)^2} = \frac{5\sigma}{6}$

$$9. \quad C_m = \epsilon_r C_0 \Rightarrow \epsilon_r = \frac{30}{6} = 5$$

$$\epsilon = \epsilon_0 \epsilon_r = 8.85 \times 10^{-12} \times 5 = 0.44 \times 10^{-10}$$

$$10. \quad C_0 = \frac{\epsilon_0 A}{d}$$
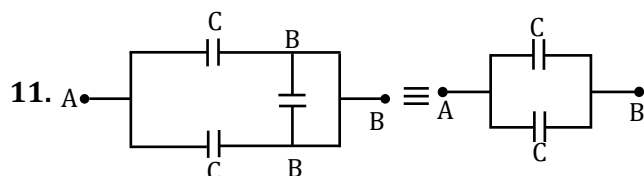
$$C_K = \frac{\epsilon_0 A}{d - t + \frac{t}{k}} = \frac{\epsilon_0 A}{d - \frac{d}{2} + \frac{d}{8}} = \frac{8 \epsilon_0 A}{5d} = \frac{8}{5} C_0$$




(one capacitor gets shorted)

$$\Rightarrow C_{eq} = C_1 + C_2$$

$$= C + C = 2C$$

$$12. \quad E = \frac{1}{2} CV^2 = \frac{1}{2} \left(\frac{\epsilon_0 A}{d} \right) (Ed)^2 = \frac{1}{2} \epsilon_0 E^2 Ad$$

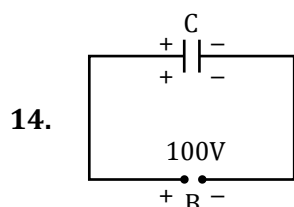
13. Polar molecules have centres of positive and negative charges separated by some distance, so they have permanent dipole moment.



$$Q_i = CV$$

$$= 900 \times 10^{-12} \times 100$$

$$Q_i = 9 \times 10^{-8} \text{ C}$$

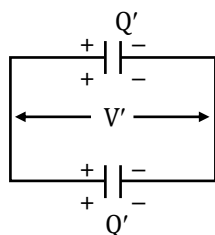

$$Q_f = 2Q'$$

From conservation of charge

$$2Q = Q_f = Q_i$$

$$Q' = \frac{Q_i}{2} = \frac{9 \times 10^{-8}}{2}$$

$$Q' = 4.5 \times 10^{-8} \text{ C}$$

$$E_{\text{store}} = 2 \times \frac{1}{2} \frac{(Q')^2}{C}$$

$$= \frac{(4.5 \times 10^{-8})^2}{900 \times 10^{-12}}$$

$$E_{\text{store}} = 2.25 \times 10^{-6} \text{ J}$$

$$15. \quad C = \frac{A \epsilon_0}{d}$$

$$C' = \frac{A/2 \epsilon_0}{2d} = \frac{A \epsilon_0}{4d} = \frac{C}{4}$$

$$16. \quad \frac{C_1 C_2}{C_1 + C_2} = 3$$



$$C_1 + C_2 = 16$$

$$C_1 C_2 = 48$$

$$C_1 = 12 \mu\text{F}$$



$$C_2 = 4 \mu\text{F}$$
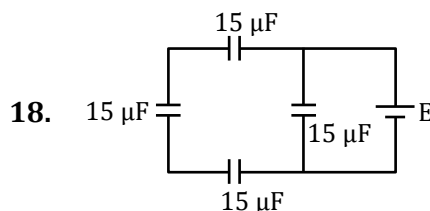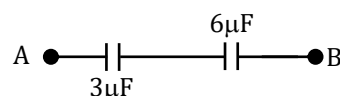
$$17. \quad C_{AB} = \frac{3 \times 6}{3 + 6} = 2 \mu\text{F}$$



$$C_{eq} = 5 + 15 = 20 \mu\text{F}$$

19. Balanced wheat stone bridge

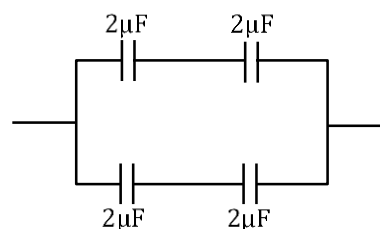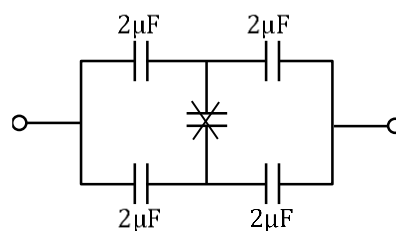

$$C_{eq} = 2 \mu\text{F}$$

20. Battery connected so $V = \text{constant}$

Now $d \downarrow \Rightarrow C \uparrow$

A: $Q = CV \propto C \Rightarrow Q \uparrow$

B: $U = \frac{1}{2} CV^2 \propto C \Rightarrow U \uparrow$

C: $C = \frac{\epsilon_0 A}{d} \Rightarrow C \uparrow$

D: $\frac{Q}{V} = C \Rightarrow C \uparrow$

E: $(Q)(V) \propto C \Rightarrow QV \uparrow$

Therefore statements A, C and E are correct.

21. $U_{\text{capacitor}} = \frac{1}{2} CV^2$

$$= \frac{1}{2} \times 12 \times 10^{-12} \times 50 \times 50$$


$$= 15 \times 10^{-9} \text{ J}$$

$$= 15 \text{ nJ}$$

22. Capacitance depends only on

- (1) Shape
- (2) Size
- (3) Medium

23.

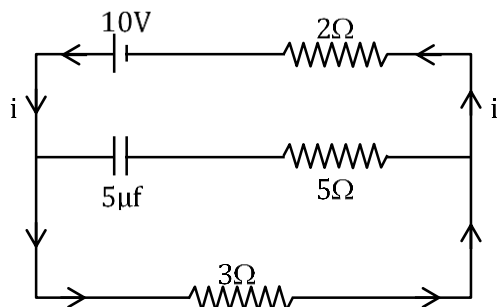

There will be no current in middle branch containing capacitor.

$$i = \frac{V}{R} = \frac{10}{2+3} = 2 \text{ A}$$

Exercise-III (Analytical Questions)

1. $\therefore$ battery is connected


$\therefore V = \text{constant}$

$$U = \frac{1}{2} CV^2, Q = CV$$

$U \propto C, Q \propto C$

4. $U = \frac{1}{2} \epsilon_0 E^2 (Ad)$

$$U \propto E^2$$

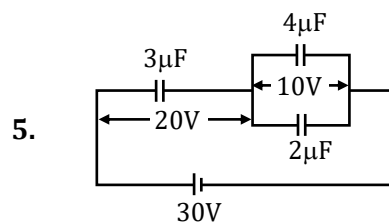

$$\therefore V \propto \frac{1}{C}$$

$$Q_{\text{Battery}} = C_{\text{eff}} V = 2 \times 20 \mu\text{C}$$

$$Q_{\text{battery}} = 60 \mu\text{C}$$

$$Q_{3\mu\text{F}} = 60 \mu\text{C}$$

$$Q_{4\mu\text{F}} = 40 \mu\text{C}$$

$$Q_{2\mu\text{F}} = 20 \mu\text{C}$$

6.
$$\begin{array}{ccc|ccc} Q & & 0 & & -2Q & \\ \hline -\frac{Q}{2} & \frac{+3Q}{2} & -\frac{3Q}{2} & \frac{+3Q}{2} & -\frac{3Q}{2} & -\frac{Q}{2} \end{array}$$


7. $U_{\text{self}} = \frac{KQ^2}{2R}$ Energy density $= \frac{1}{2} \epsilon_0 E^2$

$$F = \frac{Q^2}{2A\epsilon_0} \quad W_{\text{field}} = U_i - U_f = \frac{kQ^2}{R} - 0$$

$$W_{\text{field}} = \frac{kQ^2}{R}$$

8. Force between two point charges is independent of the presence of other charges.

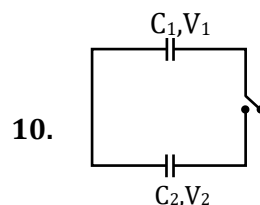9. $C = 4\pi\epsilon_0 R \Rightarrow 1 = \frac{1}{9 \times 10^9} R \Rightarrow R = 9 \times 10^9 \text{ m}$




$$V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

When two capacitors are connected then energy of system decreases. (but Not always)

11. A high capacity capacitor charged to high voltage has very high charges, that may discharge to ground through human body, when touched with bare hands.

12. $U = \frac{Q^2}{2C}$ and $C = \frac{\epsilon_0 A}{d}$ $d \uparrow C \downarrow U \uparrow$

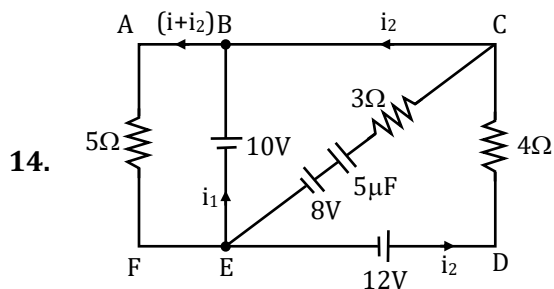13. At facing surface same magnitude and opposite nature charges are there.



When a steady state is reached, no current passes through the capacitor or the branch CE.

Considering the loop ABEFA,

$$5 \times (i_1 + i_2) = 10 \text{ or } i_1 + i_2 = 2A \quad \dots(i)$$

Considering the loop BCDEB

$$4i_2 = 12 - 10 = 2 \Rightarrow i_2 = 0.5 A$$




$$\text{So } i_1 = 2 - 0.5 = 1.5 A$$

To find the charge on capacitors, we must know potential difference across the plates.

Consider the loop CEDC :

$$-12 + 4i_2 + 3 \times 0 - V_C + 8 = 0 \Rightarrow V_C = -2V.$$

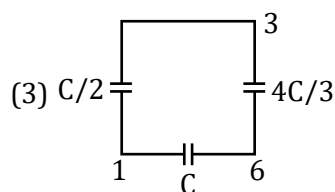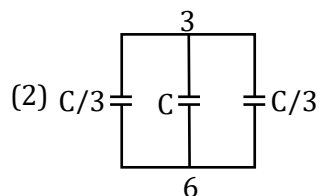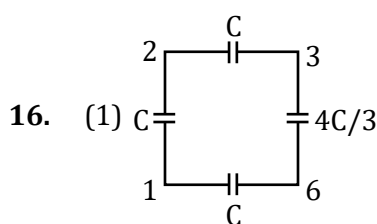
So, charge on capacitor $Q = CV = 10 \mu C$



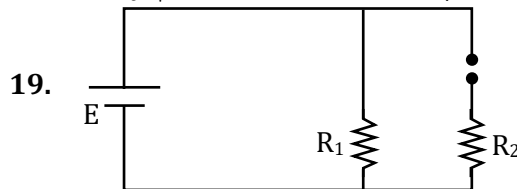18. In steady state current through battery

$$I = \frac{50}{23+3+17+7} = 1A$$


$$\Rightarrow Q_{10\mu F} = CV = 10 \times 20 = 200\mu C$$



At $t = 0$

$$I_1 = \frac{E}{R_1} = \frac{25}{5} = 5A$$

$I_2 = 0$

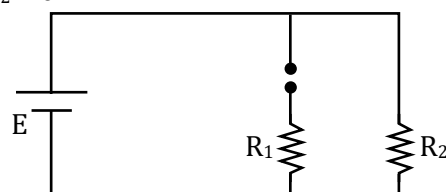

At $t = \infty$

$I_1 = 0$

$$I_2 = \frac{E}{R_2} = \frac{25}{10} = 2.5 A$$