

Alternating Current

SOLUTIONS

Exercise-I (Conceptual Questions)

- Given that,
 $H_{AC} = 3 H_{DC}$
 $I_{rms}^2 R t = 3 (I^2 R t)$
 $I_{rms}^2 = 3 I^2$
 $I_{rms} = \sqrt{3} I = \sqrt{3} \times 2$
 $I_{rms} = 3.46 \text{ A}$
- $E = E_0 \cos \omega t$
 Given, $E_0 = 10 \text{ V}$, $t = \frac{1}{600} \text{ sec.}$, $f = 50 \text{ Hz}$
 $E = 10 \cos (2\pi \times 50 \times \frac{1}{600})$
 $E = 10 \cos \frac{\pi}{6} \rightarrow E = 5\sqrt{3} \text{ V}$
- $\therefore 2\pi$ (phase difference) $\equiv T$ (Time difference)
 $1 \text{ rad (PD)} \equiv \frac{T}{2\pi}$ (Time difference)
 So, $\frac{\pi}{4}$ (PD) $\equiv \frac{T}{2\pi} \times \frac{\pi}{4}$ (Time difference)
 $= \frac{T}{8} \Rightarrow \text{time difference} = \frac{1}{50 \times 8} \text{ s}$
 or time difference = 2.5 ms.
- $I = 3 + 4 \sin \omega t$
 (i) square = $9 + 16 \sin^2 \omega t + 24 \sin \omega t$
 (ii) mean value = $9 + 16 \times \frac{1}{2} + 0 = 17$
 (iii) Root = $\sqrt{17}$
 (iv) Rms value = $\sqrt{17}$
 OR
 $I = a + b \sin \omega t$
 $\therefore I_{rms} = \sqrt{a^2 + \frac{b^2}{2}} = \sqrt{9 + \frac{16}{2}} = \sqrt{9 + 8} = \sqrt{17}$
- $i = i_1 \cos \omega t + i_2 \sin \omega t$
 Let $i_1 = a \sin \phi$, and $i_2 = a \cos \phi$
 then $i = a \sin \phi \cos \omega t + a \cos \phi \sin \omega t$
 $i = a \sin (\phi + \omega t)$
 $[\because \sin A \cos B + \sin B \cos A = \sin (A+B)]$
 So $I_{rms} = \frac{a}{\sqrt{2}}$

$$a = \sqrt{i_1^2 + i_2^2} \quad (\because a = \sqrt{i_1^2 + i_2^2})$$

OR

$$i = i_1 \cos \omega t + i_2 \sin \omega t$$

$$I_{max} = \sqrt{i_1^2 + i_2^2} \Rightarrow I_{rms} = \frac{\sqrt{i_1^2 + i_2^2}}{\sqrt{2}} = \sqrt{\frac{i_1^2 + i_2^2}{2}}$$

- $V = 120 \sin (100\pi t) \cos (100\pi t)$
 $\therefore 2 \sin \theta \cos \theta = \sin 2\theta$
 $\therefore \sin (100\pi t) \cos (100\pi t) = \frac{\sin (2 \times 100\pi t)}{2}$
 $V = 60 \sin (200\pi t)$
 compare from
 $V = V_0 \sin \omega t$
 $V_0 = 60 \text{ volt}$,
 $\omega = 200\pi$
 $2\pi f = 200\pi$
 $f = 100 \text{ Hz}$
- $V_{avg} = \frac{2V_0}{\pi} = \frac{2\sqrt{2}V_{rms}}{\pi} = \frac{2\sqrt{2} \times 220}{3.14} = 198 \text{ Volt}$
- Peak voltage in primary $V_0 = \sqrt{2} V_{rms} = 100\sqrt{2}$
 $\frac{V_s}{V_p} = \frac{N_2}{N_1} \Rightarrow V_s = \frac{N_s}{N_p} \times V_p$
 $V_s = 5 \times 100\sqrt{2} = 500\sqrt{2} \text{ Volt}$
- $X_L = 2\pi f L$
 $X_L \propto f$ (graph straight line)
 $X_C = \frac{1}{2\pi f C}$; $X_C \propto \frac{1}{f}$
 (graph rectangular hyperbola)
- $\tan \phi = \frac{X_L}{R}$
 $\tan \phi = \frac{2\pi \times 50 \times 0.21}{12}$
 $\tan \phi \approx 5.5$
 Now $\tan 60^\circ = \sqrt{3}$ and $5.5 > \sqrt{3}$
 So, angle will be greater 60° .
- $V^2 = V_R^2 + V_C^2$
 $(220)^2 = (110)^2 + V_C^2$
 $V_C = 190 \text{ Volt.}$

19. For DC. $V = IR$

$$R = \frac{V}{I} = \frac{100}{25}$$

$$R = 4\Omega \text{ (Resistance of coil)}$$

$$\text{For AC. } V = IZ$$

$$Z = \frac{V}{I} = \frac{100}{20} \quad Z = 5\Omega$$

$$Z^2 = R^2 + X^2 \quad \rightarrow \quad X^2 = Z^2 - R^2$$

$$= 5^2 - 4^2$$

$$\text{Reactance of coil } X = 3\Omega.$$

24. $I = \frac{V}{Z}$

$$Z = \omega L = 2\pi \times 50 \times 2 = 200\pi$$

$$I_1 = \frac{V}{200\pi}$$

$$\text{on frequency } 400 \text{ Hz}$$

$$Z = \omega L = 2\pi \times 400 \times 2$$

$$I_2 = \frac{V}{1600\pi}; \quad \frac{I_1}{I_2} = \frac{V}{200\pi} \times \frac{1600\pi}{V} = 8$$

$$I_2 = \frac{I_1}{8} \text{ (lagging by } 90^\circ \text{ from } V \text{ due to purely inductive circuit)}$$

OR

$X_L \propto f$, f becomes 8 times, so X_L also becomes 8 times, so current becomes $1/8$ times and lagging by 90° from V (pure inductive circuit)

$\therefore$

27. Use $X_c = \frac{1}{\omega C}$

31. $\tan \phi = \frac{X_L}{R}$

$$\tan \phi = \frac{40\pi}{100} \quad \begin{cases} X_L = \omega L \\ = 2\pi \times 50 \times 0.4 \\ = 40\pi\Omega \\ R = 100\Omega \end{cases}$$

$$\tan \phi = 0.4\pi,$$

$$\phi = \tan^{-1}(0.4\pi)$$

32. $\tan \phi = \frac{X_c}{R} = \frac{1}{\omega RC}$

$$= \frac{1}{2\pi \times 50 \times 100 \times 100 \times 10^{-6}} = \frac{1}{\pi}$$

$$\rightarrow \phi = \tan^{-1}\left(\frac{1}{\pi}\right)$$

33. $V_L = L \frac{dI}{dt} = L \frac{d}{dt} (I_0 \sin \omega t)$
 $= I_0 \omega L \cos \omega t = I_0 \omega L \sin(\omega t + \pi/2)$

35. Use $V^2 = V_R^2 + V_C^2$

39. $V_L = I \times X_L$
 $I = \frac{0.6}{2\pi \times 60 \times 10^{-3}}$

40. $\therefore X_L = X_C$

$$f = \frac{1}{2\pi\sqrt{LC}} \rightarrow X_L = 2\pi fL$$

$$X_L = 2\pi L \times \frac{1}{2\pi\sqrt{LC}} = \sqrt{\frac{L}{C}}$$

$$X_L = \sqrt{\frac{10^{-3}}{10 \times 10^{-6}}} \Rightarrow X_L = 10\Omega.$$

OR

$$\text{At resonance, } \omega = \frac{1}{\sqrt{LC}}$$

$$\omega = 10^4 \text{ Rad/sec.}$$

$$\therefore X_L = \omega L = 10^4 \times 10^{-3} = 10\Omega$$

42. Impedance of series circuit

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

If X_L and X_C are interchanged then there is no effect on Z .

47. Power dissipation = $VI \cos \phi$

$$= V \cdot \frac{V}{Z} \cdot \frac{R}{Z} = \frac{V^2 R}{Z^2}$$

$$\text{Now } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = R (\because X_L = X_C)$$

$$\text{Power dissipation} = \frac{V^2 R}{R^2} = \frac{V^2}{R}$$

$$V = \frac{V_0}{\sqrt{2}} = \frac{10}{\sqrt{2}} \Rightarrow R = 10\Omega$$

$$\text{Power dissipation} = \frac{10 \times 10}{\sqrt{2} \times \sqrt{2} \times 10} = 5 \text{ Watt.}$$

OR

At resonance

$$I_0 = \frac{10}{10} = 1 \text{ A}$$

$$I_{\text{rms}} = \frac{1}{\sqrt{2}} \text{ A}$$

$$P_{\text{av}} = V_{\text{rms}} I_{\text{rms}} = \frac{10}{\sqrt{2}} \times \frac{1}{\sqrt{2}} = 5 \text{ Watt.}$$

Alternating Current

48. At resonance, maximum power impart to circuit.

$$f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow 50 = \frac{1}{2\pi\sqrt{10 \times C}}$$

$$\rightarrow C = 10^{-6} \text{ F}$$

49. $f = \frac{1}{2\pi\sqrt{LC}}$

Now $L' = L + \frac{L}{4} = \frac{5L}{4}$

$C' = C - \frac{C}{5} = \frac{4C}{5}$

$$f' = \frac{1}{2\pi\sqrt{L'C'}} = \frac{1}{2\pi\sqrt{\frac{5L}{4} \times \frac{4C}{5}}}$$

$$f' = \frac{1}{2\pi\sqrt{LC}} = f$$

51. R Changed $\Rightarrow$ Z Changed $\Rightarrow$ I Changed

$V_L = I X_L$ (Changed)

$V_C = I X_C$ (Changed)

V_L and V_C are changed by same amount

So Voltage across LC combination ($V_L - V_C$) remains same.

52. $\tan \phi = \frac{V_L - V_C}{V_R} = \frac{1}{1} = 45^\circ$

$V_L > V_C$

So current lags by $\frac{\pi}{4}$

$$\therefore I = I_0 \cos \left(\omega t - \frac{\pi}{4} \right)$$

53. $Z = \sqrt{R^2 + X^2}$ [X = reactance]

if $\omega \uparrow$ than $X_C \downarrow$, $Z \downarrow$

So circuit contain resistance and capacitance

54. $V_L = V_C$

$\therefore X_L = X_C$ (Resonance condition)

$$i = \frac{V}{R} = \frac{100}{50} = 2 \text{ A}$$

$$V_R = iR = 2 \times 50 = 100 \text{ V}$$

56. $V^2 = V_R^2 + (V_L - V_C)^2$

59. $P_{\text{loss}} = VI \cos \phi$

$$\cos \phi = \frac{P_{\text{loss}}}{VI} = \frac{600}{5 \times 160}$$

$$\cos \phi = 0.75$$

64. $E = E_0 \sin \omega t$

$$I = I_0 \sin \left(\omega t + \frac{\pi}{2} \right) \Rightarrow \phi = \frac{\pi}{2}$$

$$\cos \phi = 0 \text{ so } P = 0$$

65. Power factor $\cos \phi = \frac{R}{Z}$

For negligible power factor $\Rightarrow$ R Low

Z high (L high)

66. Wattless power = $V I \sin \phi$,

Wattless power

$$= \frac{100}{\sqrt{2}} \times \frac{100}{\sqrt{2}} \times \sin \frac{\pi}{6} \begin{cases} V = \frac{100}{\sqrt{2}} \text{ V} \\ I = \frac{100}{\sqrt{2}} \text{ A} \\ \phi = \frac{\pi}{6} \end{cases}$$

$$= 2.5 \times 10^3 \text{ Watt}$$

69. Power factor = $\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X_L^2}}$

$$\cos \phi = \frac{1100}{\sqrt{(1100)^2 + \left(2 \times \frac{22}{7} \times 50 \times \frac{7}{2} \right)^2}}$$




$$= \frac{1100}{\sqrt{(1100)^2 + (1100)^2}}; \cos \phi = \frac{1}{\sqrt{2}}$$

Exercise-II (Previous Year Questions)

1. When capacitor is filled with mica then capacitance C increases so X_C decreases
In case (b) $X_C \downarrow$ so voltage across capacitor decreases. so $V_a > V_b$

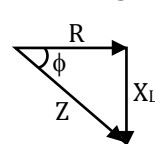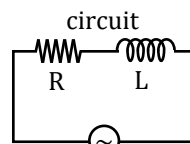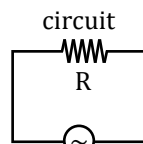2.

Pure resistor Resistor & Inductor (Phasor diagram)



AC source Impedance = Z

$$P' = V.I \cos \phi$$

$$P = \frac{V^2}{R}$$

$$P' = V \cdot \left[\frac{V}{Z} \right] \cdot \cos \phi$$

$$\Rightarrow V^2 = PR \quad P' = \frac{V^2}{Z} \cdot \frac{R}{Z}$$

(From phasor diagram)

$$P' = \frac{(PR)R}{Z^2}$$

$$P' = \left(\frac{R}{Z} \right)^2 P$$

$$\begin{aligned}
 3. \quad \frac{1}{\omega C} &= \frac{1}{340 \times 50 \times 10^{-6}} X_C = 58.8 \Omega \\
 X_L &= \omega L = 340 \times 20 \times 10^{-3} = 6.8 \Omega \\
 Z &= \sqrt{R^2 + (X_C - X_L)^2} \\
 &= \sqrt{40^2 + (58.8 - 6.8)^2} = \sqrt{4304} \Omega \\
 P &= i_{\text{rms}}^2 R = \left(\frac{V_{\text{rms}}}{Z} \right)^2 R \\
 &= \left(\frac{10/\sqrt{2}}{\sqrt{4304}} \right)^2 \times 40 = \frac{50 \times 40}{4304} = 0.47 \text{ W}
 \end{aligned}$$


So best answer (nearest answer) will be (1)

4. Input voltage, $V(t) = V_0 \sin \omega t$
 For capacitor, $I(t) = \frac{dq}{dt} = C \frac{dV}{dt} = \omega C V_0 \cos \omega t$
 $\Rightarrow$ Current $I(t)$ leads voltage $V(t)$ by 90°
 Also, Capacitor does not consume any energy over a full cycle.
5. For better tuning, Q-factor must be high.
 $\therefore Q = \frac{\omega_0 L}{R} = \frac{1}{\sqrt{LC}} \left(\frac{L}{R} \right) = \frac{1}{R} \sqrt{\frac{L}{C}}$
 R and C should be small and L should be high.
6. $\tan \phi = \frac{V_L - V_C}{V_R} = \frac{100 - 40}{80} = \frac{3}{4}$ or $\phi = 37^\circ$
 Power factor = $\cos \phi = \cos 37^\circ = \frac{4}{5}$ or 0.8
7. Here
 $X_L = \omega L = (314) (20 \times 10^{-3}) = 6.280$
 $X_C = \frac{1}{\omega C} = \frac{1}{314 \times 100 \times 10^{-6}} = 31.84 \Omega$
 $R = 50 \Omega$
 $Z = \sqrt{(X_C - X_L)^2 + R^2}$
 $= \sqrt{(31.84 - 6.28)^2 + (50)^2} = 56 \Omega$
 $\Rightarrow P = \left(\frac{V_{\text{rms}}}{Z} \right)^2 R = \left(\frac{10}{\sqrt{2} \times 56} \right)^2 \times 50$
 $= 0.79 \text{ watt}$
8. Changing polarity is termed as AC.
9. $Z = \frac{12}{0.2} = 60 \Omega$ and $R = \frac{12}{0.4} = 30 \Omega$

$$\begin{aligned}
 10. \quad I &= \frac{V}{X_C} = \frac{V}{1/C\omega} = VC\omega \\
 &= 200 \times 40 \times 10^{-6} \times 2\pi \times 50 \\
 &= 2.5 \text{ A} \\
 11. \quad \text{When L removed } \tan \phi &= \frac{X_C}{R} \\
 \text{When L removed } \tan \phi &= \frac{X_L}{R} \\
 \frac{X_C}{R} &= \frac{X_L}{R} \Rightarrow \text{Resonance} \Rightarrow Z = R \\
 \cos \phi &= \frac{R}{Z} = \frac{R}{R} = 1
 \end{aligned}$$

$$\begin{aligned}
 12. \quad \text{Impedance, } z &= \sqrt{R^2 + X_L^2} \\
 X_L \uparrow, Z \uparrow, I \downarrow
 \end{aligned}$$
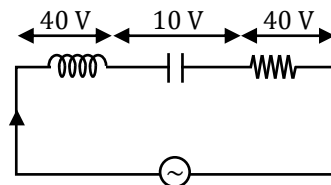
$$\begin{aligned}
 13. \quad I_0 &= 10\sqrt{2} \text{ A} \\
 I_{\text{RMS}} &= \frac{I_0}{\sqrt{2}} = 10 \text{ A}
 \end{aligned}$$



$$\begin{aligned}
 V_{\text{RMS}} &= \sqrt{V_R^2 + (V_L - V_C)^2} \\
 &= \sqrt{(40)^2 + (40 - 10)^2} \\
 &= 50 \text{ V} \\
 Z &= \frac{V_{\text{RMS}}}{I_{\text{RMS}}} = \frac{50 \text{ V}}{10 \text{ V}} = 5 \Omega
 \end{aligned}$$

$$\begin{aligned}
 14. \quad Q &= \frac{\omega}{\Delta \omega} = \frac{\omega L}{R} \Rightarrow \Delta \omega = R/L = \frac{50}{4} = 8 \text{ rad/sec} \\
 \omega_0 &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 80 \times 10^{-6}}} = 50 \text{ rad/sec.} \\
 \omega_{\text{min}} &= \omega_0 - \frac{\Delta \omega}{2} = 46 \text{ rad/sec} \\
 \omega_{\text{max}} &= \omega_0 + \frac{\Delta \omega}{2} = 54 \text{ rad/sec} \\
 19. \quad L &= 10 \times 10^{-3} \text{ H} \\
 C &= 1 \times 10^{-6} \text{ F} \\
 R &= 100 \Omega \\
 \text{At resonance } X_L &= X_C \\
 \omega L &= \frac{1}{\omega C} \\
 f &= \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10 \times 10^{-3} \times 10^{-6}}} = 1.59 \text{ KHz}
 \end{aligned}$$

Alternating Current

$$20. \quad i_c = i_d = \frac{V_0}{X_c} \sin \omega t$$

$$i_c = i_d = (V_0 \omega C) \sin \omega t$$

On decreasing frequency $i_c \downarrow$

$$21. \quad X_L = \frac{50}{L} \times 10^{-3} \times 2\pi \times 50 = 5\Omega$$

$$X_C = \frac{1}{2\pi \times 50 \times \frac{10^3}{\pi} \times 10^{-6}} = 10\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{(10)^2 + (5)^2}$$

$$= 5\sqrt{5}\Omega$$

$$22. \quad \tan \phi = \frac{X_L}{R}$$

$$X_L = \omega L = 100\pi \times \frac{1}{\pi} = 100\Omega$$

$$R = 100\Omega$$

$$\tan \phi = \frac{100}{100} = 1$$

$$\phi = 45^\circ$$

$$23. \quad Z_1 = \sqrt{X_L^2 + R^2} \quad X_L = 0 \text{ (D.C. circuit)}$$

$$Z_1 = 10\Omega$$

$$Z_2 = \sqrt{X_C^2 + R^2}$$

$$X_C = \frac{1}{2\pi \times 50 \times \frac{10^3}{\pi} \times 10^{-6}} = 10\Omega$$

$$Z_2 = \sqrt{(10)^2 + (10)^2}$$

$$= 10\sqrt{2}$$

$$Z_1 < Z_2$$

24. Power dissipated is maximum of purely resistive circuit.

$$25. \quad \omega = 2\pi \frac{\text{rad}}{\text{sec}}$$

$$E_{\max} = NBA\omega$$

$$= 100 \times 0.05 \times 1 \times 2\pi$$

$$= 10 \times \pi$$


$$= 31.4 \text{ V}$$

26. as frequency is very high

$$X_C \approx 0$$

$$X_L \rightarrow \infty$$

Effective circuit will be

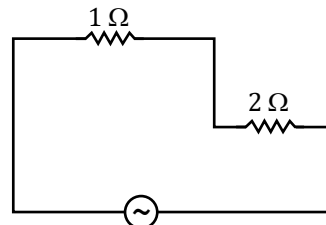

Effective impedance of circuit will be $= 3\Omega$

$$27. \quad I_{\text{Peak}} = \frac{V_{\text{Peak}}}{X_C} = V_{\text{Peak}} (\omega C)$$

$$= V_{\text{Peak}} (2\pi f C)$$

$$= (210\sqrt{2}) (2\pi \times 50 \times 10 \times 10^{-6})$$

$$= 0.93 \text{ Ampere}$$

$$28. \quad V_L = i X_L$$

$$V_L = \omega L i_0 \cos \omega t$$

$$29. \quad P = Vi$$

$$88 = 11000 i$$

$$i = 8 \times 10^{-3} \text{ A}$$

$$i = 8 \text{ mA}$$

$$30. \quad Q = Q_0 e^{\frac{-Rt}{2L}}$$

putting $Q = 0.50 Q_0$;

$$0.50 Q_0 = Q_0 e^{\frac{-Rt}{2L}}$$

$$\Rightarrow e^{\frac{Rt}{2L}} = 2$$

$$\Rightarrow \frac{Rt}{2L} = \ln(2)$$

$$\Rightarrow t = \frac{2L}{R} (\ln 2) = \frac{2 \times 12 \times 10^{-3}}{1.5} \cdot (0.693)$$

$$= 11.088 \times 10^{-3} = 11.09 \text{ ms}$$

Exercise-III (Analytical Questions)

1. At frequency lower than resonant frequency since $X_C > X_L$

$\therefore$ Current leads voltage

$\rightarrow$ At resonance, impedance is minimum.

$\rightarrow$ At resonance, phase diff. between voltage across L and current in C is $\frac{\pi}{2}$

$$\rightarrow f = \frac{1}{2\pi \sqrt{LC}}$$

2. $\tau = RC \Rightarrow R = \frac{\tau}{C}$

$$[R] = \left[\frac{1}{fC} \right]$$

$$\tau = \frac{L}{R} \Rightarrow R = \frac{L}{\tau} = (f.L)$$

$\therefore$ b & c are correct.


3. $V_1 = \sqrt{V_R^2 + V_L^2} = 100 \text{ Volt} \quad \dots(1)$


$V_C - V_L = 120 \text{ Volt} \quad \dots(2)$


$$130 = \sqrt{V_R^2 + (V_L - V_C)^2} \Rightarrow V_R = 50 \text{ Volt}$$


$V_L = 50\sqrt{3} \text{ Volt} = 86.6 \text{ Volt} \text{ \& } V_C = 206.6 \text{ Volt}$

$$\cos \phi = \frac{V_R}{130} = \frac{5}{13}$$

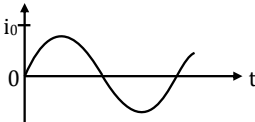
4.  $i_{\text{Avg}} = 0, i_{\text{rms}} = \frac{i_0}{\sqrt{2}}$

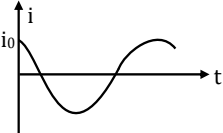 $i_{\text{avg}} = 0, i_{\text{rms}} = \frac{i_0}{\sqrt{2}}$

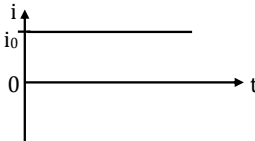
 $i_{\text{Avg}} = i_{\text{rms}} = i_0$

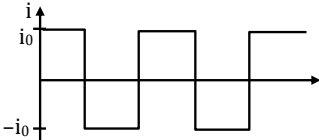 $i_{\text{Avg}} = 0, i_{\text{rms}} = i_0$


5. $Q_{\text{factor}} = \frac{1}{R} \sqrt{\frac{L}{C}}$

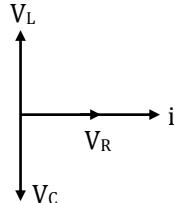6. 


7. $f_0 = \sqrt{f_1 f_2}$

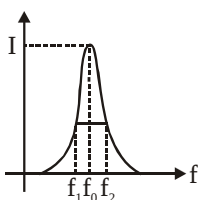

8. $z = \sqrt{R^2 + (x_L - x_C)^2}$

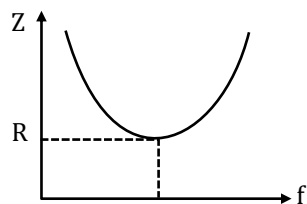

Impedance can be greater than or equal to resistance, but it can't be less than resistance of circuit.

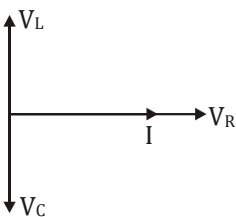9. 

At resonance

$$V_L = V_C \text{ \& } Z = R$$

there V_L & V_C are out of phase

10. For capacitor and inductor

$$\phi = 90^\circ \Rightarrow \cos \phi = 0 \Rightarrow P_{\text{avg}} = 0$$

11. **For (A)** : Current and voltage are in phase

$\Rightarrow$ only R or RLC in resonance.

For (B) : Current leads voltage by $\frac{\pi}{2} \Rightarrow$ only C

$\Rightarrow$ power factor = 0

For (C) : Current leads voltage $\Rightarrow$ RC

or RLC with $X_C > X_L$

For (D) : Current leads voltage

$\Rightarrow$ RL or RLC with $X_L > X_C$